



**VietNam National University
University of Engineering and Technology**

Modelling Combinational Circuit with VHDL


TS. Nguyễn Kiêm Hùng
Email: kiemhung@vnu.edu.vn

Laboratory for Smart Integrated Systems


Objectives

- In this lecture you will be introduced to:
 - **Key VHDL constructs used to define combinational circuits**
 - **Commonly used combinational subcircuits**

Register Transfer Level (RTL) Design

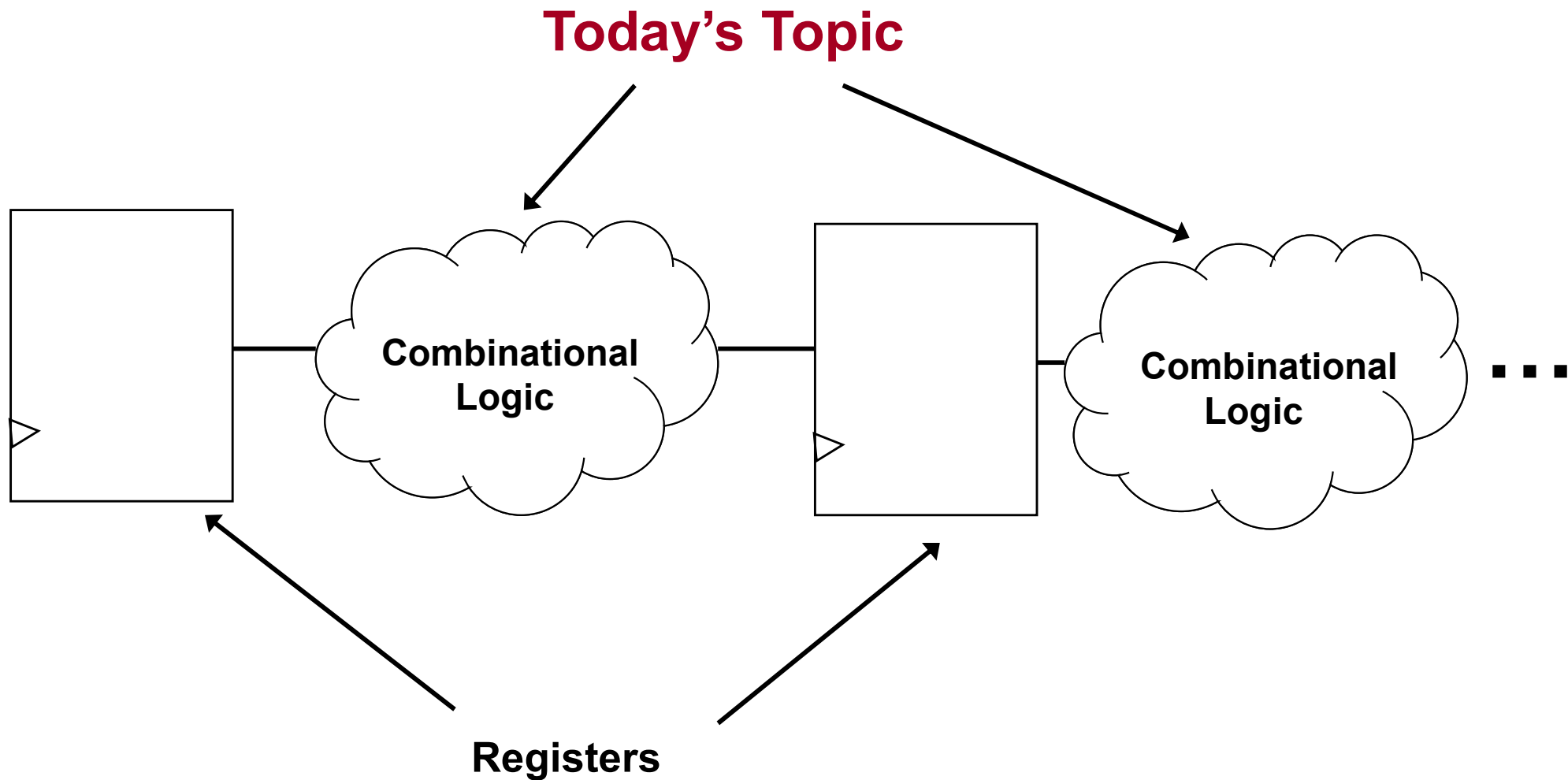


VHDL Design Styles

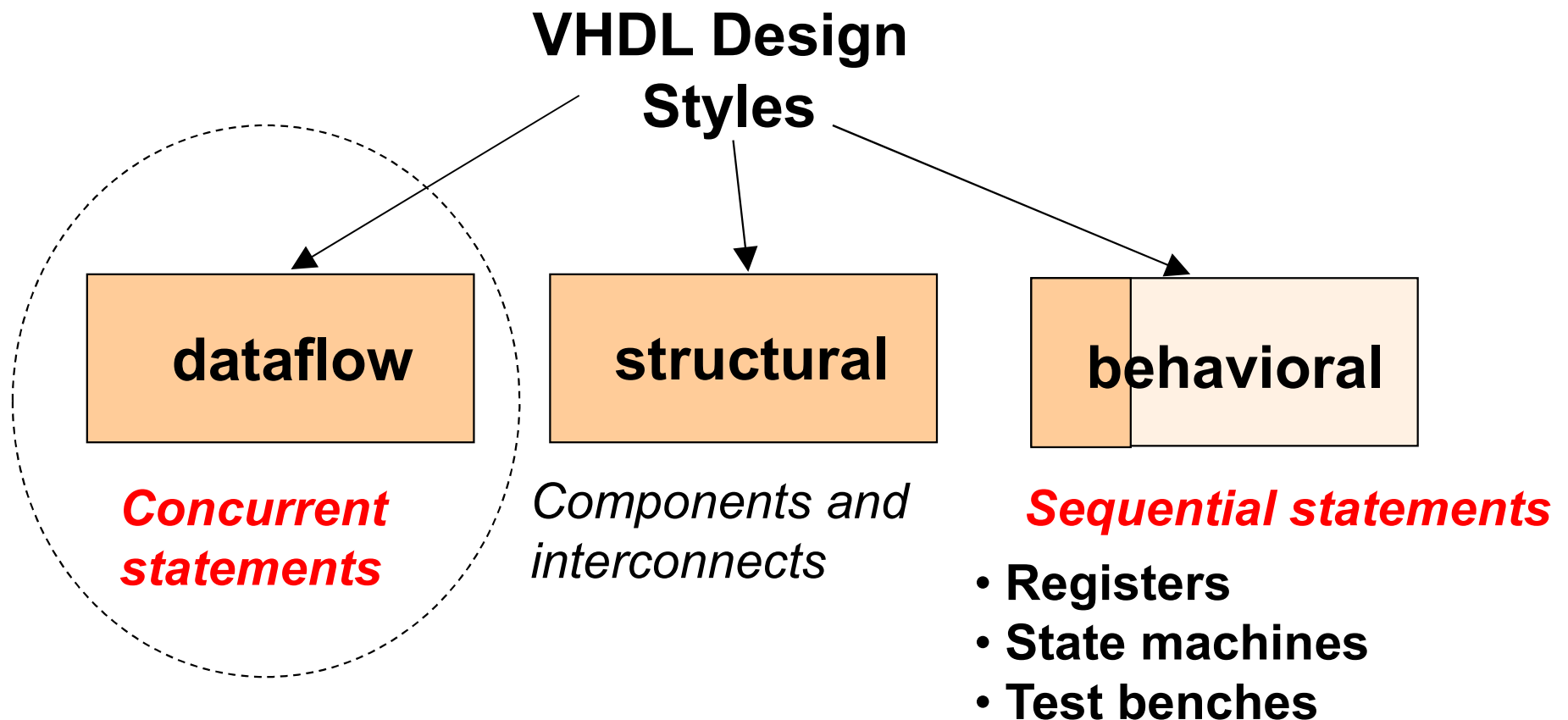

Operators

Logic Operators

- Logic operators

 


- Logic operators precedence

only in VHDL-93

Highest



Lowest

 

Concatenation

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL c, d, e, f: STD_LOGIC_VECTOR(7 DOWNTO 0);

a <= "0000";
b <= "1111";
c <= a & b;           -- c = "00001111"

d <= '0' & "0001111";  -- d <= "00001111"

e <= '0' & '0' & '0' & '0' & '1' & '1' &
    '1' & '1';         -- e <= "00001111"
f <= ('0', '0', '0', '0', '1', '1', '1', '1') ;
                                -- f <= "00001111"
```

Arithmetic Operators (1)

To use basic arithmetic operations involving `std_logic_vectors` you need to include the following library packages:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
USE ieee.std_logic_unsigned.all;
```

or

```
USE ieee.std_logic_signed.all;
```


Arithmetic Operators (2)

You can use standard +, -, *, [/] operators to perform addition and subtraction:

```
signal A : STD_LOGIC_VECTOR(3 downto 0) ;  
signal B : STD_LOGIC_VECTOR(3 downto 0) ;  
signal C : STD_LOGIC_VECTOR(3 downto 0) ;  
.....  
C <= A + B ;
```

Relational Operators

- Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

- Logic and relational operators precedence

Highest
↓
Lowest

not					
=	/=	<	<=	>	>=
and	or	nand	nor	xor	xnor

Precedence of logic and relational operators

The desired function: compare $a = bc$
(a equal to b and c or not?)

Incorrect

... when $a = b$ **and** c else ...

equivalent to

... when $(a = b)$ **and** c else ...

Correct


... when $a = (b \text{ **and** } c)$ else ...

No Implied Precedence of Logic operator

Wanted: $y = ab + cd$

Incorrect

 $y \leq a \text{ and } b \text{ or } c \text{ and } d ;$
equivalent to
 $y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d ;$
equivalent to
 $y = (ab + c)d$




Correct


$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d) ;$

Precedence of Arithmetic Operator

$S \leftarrow A + B + C + D;$

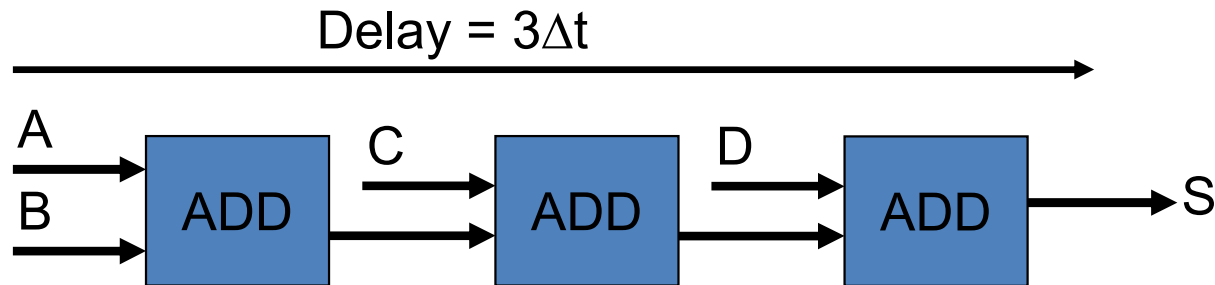

$S \leftarrow (A + B) + (C + D);$

 

Describing Combinational Logic Using Dataflow Design Style

Concurrent statements

Concurrent signal assignments are event triggered and executed as soon as an event on one of the signals occurs

- Simple signal assignment (\Leftarrow)
- Conditional signal assignment
(when-else)
- Selected signal assignment
(with-select-when)
- Generate scheme for equations
(for-generate)

Simple Signal Assignment

- **Syntax:**

[Label:] Target_signal <= expression;

- **Example:**

```
Sum <= (A xor B) xor Cin;
```

```
Carry <= (A and B);
```

```
Z <= (not X) or Y;
```


Simple Signal Assignment : Example

Full Adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth Table


$x_i y_i$ c_i	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$x_i y_i$ c_i	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 

(c) Circuit

Simple Signal Assignment : Example (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY fulladder IS  
    PORT ( x      : IN          STD_LOGIC ;  
           y      : IN          STD_LOGIC ;  
           cin     : IN          STD_LOGIC ;  
           s       : OUT         STD_LOGIC ;  
           cout    : OUT         STD_LOGIC ) ;  
END fulladder ;
```

Simple Signal Assignment : Example (2)

```
ARCHITECTURE fulladd_dataflow OF fulladder IS  
BEGIN
```

```
    U1: s <= (x XOR y) XOR cin ;
```

```
    U2: cout <= (x AND y) OR (cin AND x) OR (cin AND y) ;
```

```
END fulladd_dataflow ;
```

Simple Signal Assignment : Example (3)


```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE IEEE.std_logic_unsigned.all;  
  
...
```

```
ARCHITECTURE fulladd_dataflow OF fulladd IS  
-- define internal SUM signal  
signal SUM: STD_LOGIC_VECTOR(1 downto 0);  
BEGIN  
    U0: SUM <= ('0' & x) + ('0' & y) + ('0' & cin);  
    U1: COUT <= SUM(1);  
    U2: S <= SUM(0);  
END fulladd_dataflow ;
```

QUIZ

**How to build a structural model of 4-bit adder
by using the described Full Adder?**

Structural Model of 4-bit Adder

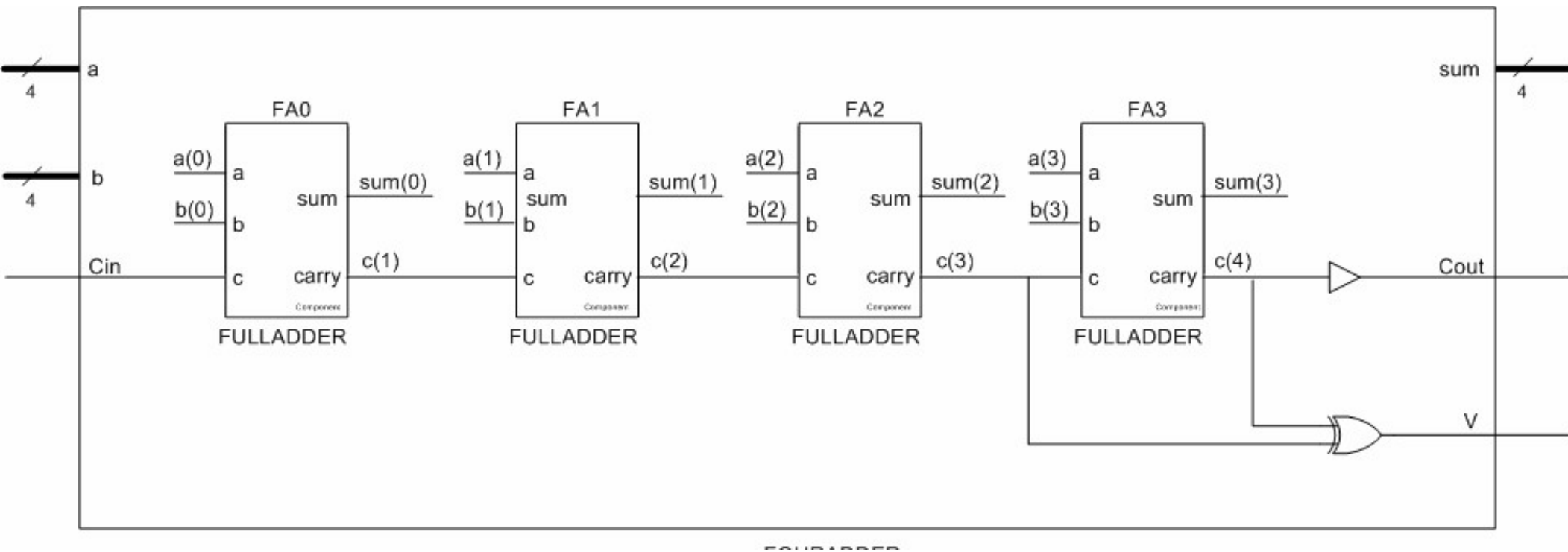

Structural Model of 4-bit Adder

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY ADDER_4BIT IS  
    PORT ( x      : IN      STD_LOGIC_VECTOR (3 downto 0);  
          y      : IN      STD_LOGIC_VECTOR (3 downto 0);  
          cin    : IN      STD_LOGIC ;  
          sum    : OUT     STD_LOGIC_VECTOR (3 downto 0);  
          v, cout: OUT     STD_LOGIC ) ;  
END ADDER_4BIT ;
```

Structural Model of 4-bit Adder

```
ARCHITECTURE adder_4bit_structure OF adder_4bit IS  
  signal c: std_logic_vector (4 downto 0);  
  -- component declaration  
  component FULLADDER  
    port (x, y, cin: in std_logic;  
          s, cout: out std_logic);  
  end component;  
BEGIN  
  FA0: FULLADDER  
    port map (x(0), y(0), cin, sum(0), c(1));  
  FA1: FULLADDER  
    port map (x(1), y(1), C(1), sum(1), c(2));  
  FA2: FULLADDER  
    port map (x(2), y(2), C(2), sum(2), c(3));  
  FA3: FULLADDER  
    port map (x(3), y(3), C(3), sum(3), c(4));  
  Cout <= c(4);  
  V <= c(3) xor c(4);  
END adder_4bit_structure ;
```


Assigning Signal Values Using OTHERS

- **Syntax:**

$S \leq (OTHERS \Rightarrow value) ;$

-- set each bit of the destination operand to Value

- **Example:**


$S \leq (OTHERS \Rightarrow '0') ;$

$S \leq (0 \Rightarrow '1', OTHERS \Rightarrow '0') ;$

Conditional Signal Assignment


When - Else
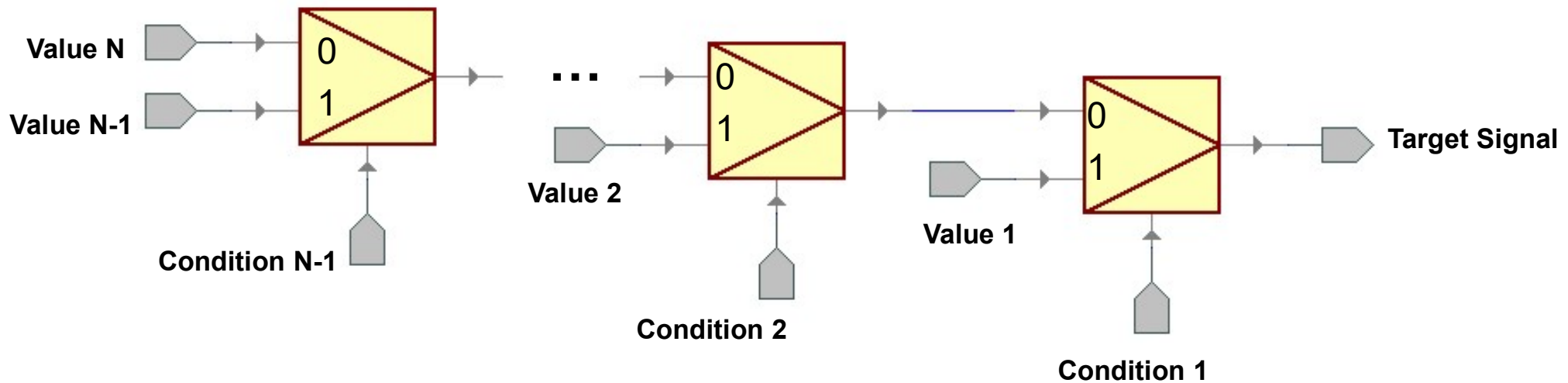
```
[label:]  
target_signal <= value1 WHEN condition1 ELSE  
                    value2 WHEN condition2 ELSE  
                    . . .  
                    valueN-1 WHEN conditionN-1 ELSE  
                    valueN;
```





Example: Tri-state Buffer

- Tri-State Buffer

 

<i>C</i>	<i>A</i>	<i>Y</i>
0	x	Hi-Z
1	0	0
1	1	1

- Tri-State Inverter

  


Example: Tri-state Buffer (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY tri_state IS  
    PORT ( C : IN          STD_LOGIC;  
           A : IN          STD_LOGIC_VECTOR(7 downto 0);  
           Y : OUT STD_LOGIC_VECTOR (7 DOWNT0 0)  
           );  
END tri_state;
```

Example: Tri-state Buffer (2)

```
ARCHITECTURE tri_state_dataflow OF tri_state IS  
BEGIN  
    Y <= A WHEN (C = '1') ELSE  
        (OTHERS => 'Z');  
END tri_state_dataflow;
```

Example: 4-to-1 multiplexer (1)

 

(a) Graphical symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

Example: 4-to-1 multiplexer (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY mux4to1 IS  
    PORT (A, B, C, D: IN      std_logic;  
          SEL : IN      std_logic_vector (1 downto 0);  
          Z: OUT      std_logic  
    );  
END mux4to1;
```

4-to-1 Multiplexer– example (2)

```
ARCHITECTURE mux4to1_dataflow OF mux4to1 IS  
BEGIN
```

```
END mux4to1_dataflow;
```

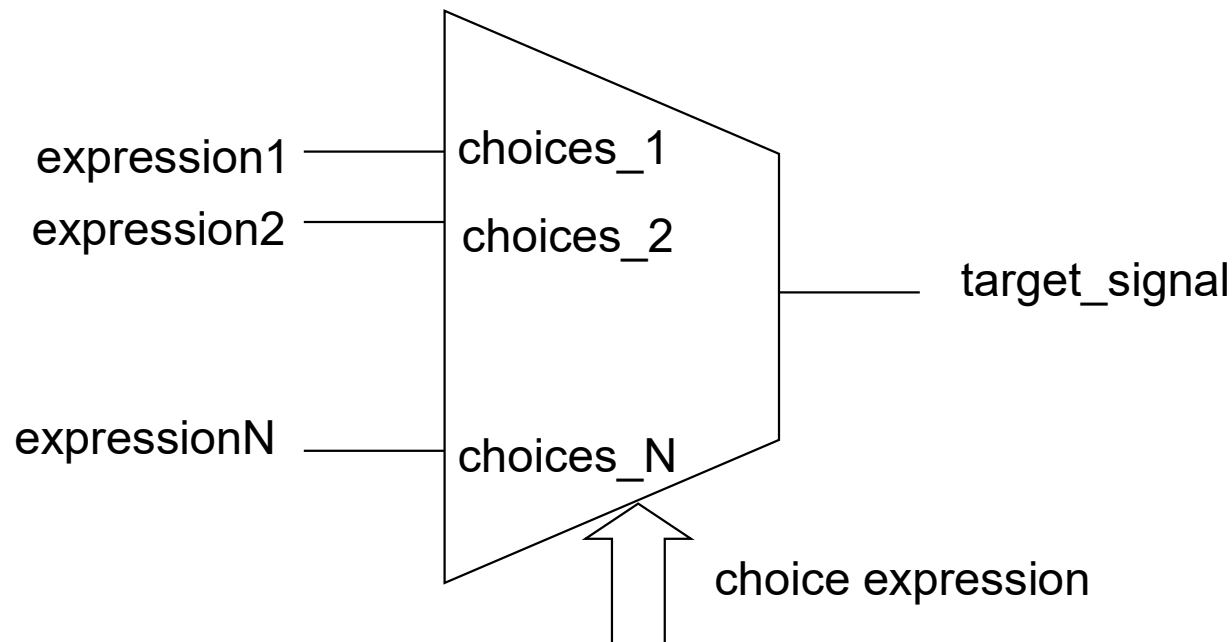

4-to-1 Multiplexer– example (2)

```
ARCHITECTURE mux4to1_dataflow OF mux4to1 IS  
BEGIN  
    Z <= A when SEL="00" else  
        B when SEL="01" else  
        C when SEL="10" else  
        D;  
  
END mux4to1_dataflow;
```

Selected Signal assignment

With – Select - When

```
[label:]  
WITH choice_expression SELECT  
    target_signal <= expression1 WHEN choices_1,  
        expression2 WHEN choices_2,  
        . . .  
        expressionN WHEN choices_N;
```



Rules

- ✓ No two choices can overlap
- ✓ All possible values of choice_expression must be covered by the set of choices, unless an OTHERS choice is present.
- ✓ Allowed formats of *choices_k*:

WHEN value

WHEN value_1 to value_2

WHEN value_1 | value_2 | | value N

Allowed formats of *choice_k* - example

```
SIGNAL a,b,c,d,y: STD_LOGIC;  
SIGNAL sel: STD_LOGIC_VECTOR(2 downto 0)  
WITH sel SELECT  
    y <= a WHEN "000",  
    b WHEN "011" to "110",  
    c WHEN "001" | "111",  
    d WHEN OTHERS;
```

Example: 4-to-1 multiplexer (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY mux4to1 IS  
    PORT (A, B, C, D: IN      std_logic;  
          SEL : IN      std_logic_vector (1 downto 0);  
          Z:    OUT std_logic  
    );  
END mux4to1;
```


Example: 4-to-1 multiplexer (2)

```
ARCHITECTURE mux4to1_dataflow OF mux4to1 IS  
BEGIN  
    WITH SEL SELECT  
        Z <=  A when “00”,  
              B when “01”,  
              C when “10”,  
              D when OTHERS;  
  
END mux4to1_dataflow;
```

QUIZ

How to build a structural model of 16-to-1 multiplexer by using the described 4-to-1 multiplexer ?

QUIZ

 

Package Definition: *My_package*

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
PACKAGE My_package IS  
COMPONENT mux4to1  
PORT ( A, B, C, D : IN          STD LOGIC ;  
        SEL : IN          STD LOGIC VECTOR (1 DOWNT0 0) ;  
        f : OUT          STD LOGIC ) ;  
END COMPONENT ;  
END My_package ;
```

Example: 16-to-1 multiplexer (1)

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
LIBRARY work ;  
USE work.My_package.all ;  
  
ENTITY mux16to1 IS  
    PORT ( w : IN STD LOGIC VECTOR(0 TO 15) ;  
           s: IN STD LOGIC VECTOR(3 DOWNT0 0) ;  
           f : OUT STD LOGIC ) ;  
END mux16to1 ;
```

Example: 16-to-1 multiplexer (2)

ARCHITECTURE Structure **OF** mux16to1 **IS**

SIGNAL m : STD LOGIC VECTOR(0 TO 3) ;

BEGIN

Mux1: mux4to1 **PORT MAP**

(w(0), w(1), w(2), w(3), s(1 DOWNT0 0), m(0)) ;

Mux2: mux4to1 **PORT MAP**

(w(4), w(5), w(6), w(7), s(1 DOWNT0 0), m(1)) ;

Mux3: mux4to1 **PORT MAP**

(w(8), w(9), w(10), w(11), s(1 DOWNT0 0), m(2)) ;

Mux4: mux4to1 **PORT MAP**

(w(12), w(13), w(14), w(15), s(1 DOWNT0 0), m(3)) ;

Mux5: mux4to1 **PORT MAP**

(m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f) ;


END Structure ;

QUIZ

Write VHDL code for a 2-to-4 binary decoder by using selected signal assignment statements?

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

Example: 2-to-4 Decoder (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY dec2to4 IS  
    PORT (E: IN          std_logic;  
           w : IN          std_logic_vector (1 downto 0);  
           y: OUT         std_logic_vector (3 downto 0)  
    );  
END dec2to4;
```


Example: 2-to-4 Decoder (2)

```
ARCHITECTURE dec2to4_dataflow OF dec2to4 IS  
  Signal t : std_logic_vector(2 downto 0);  
BEGIN  
  t <= E & w;  
  WITH t SELECT  
    y <=    "0001" when "100",  
            "0010" when "101",  
            "0100" when "110",  
            "1000" when "111",  
            "0000" when OTHERS;  
  
END dec2to4_dataflow;
```

QUIZ

How to build a structural model of 4-to-16 decoder by using the described 2-to-4 decoder ?

QUIZ

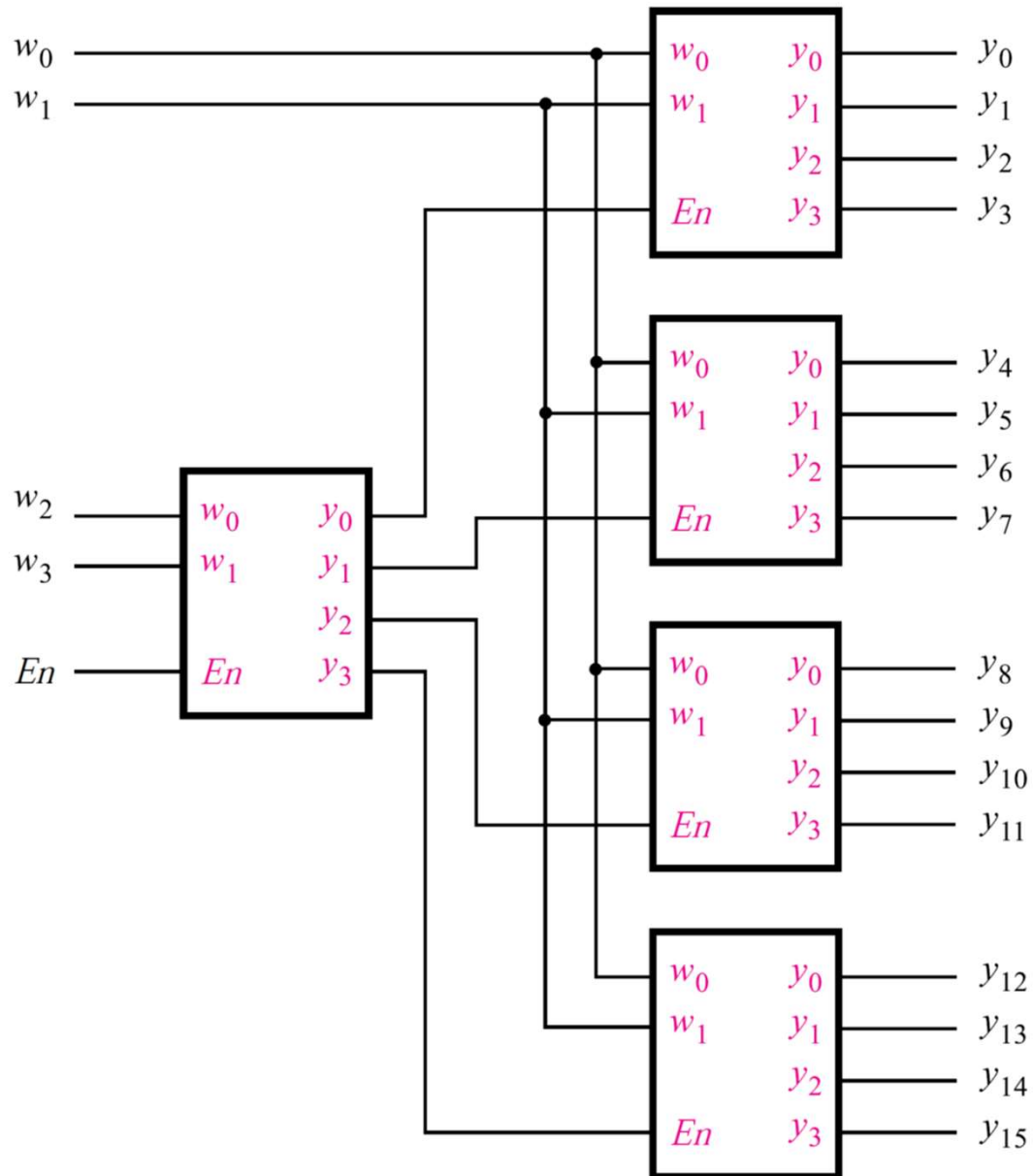

Generate Statements: Motivation

```
ARCHITECTURE adder_4bit_structure OF adder_4bit IS  
  signal c: std_logic_vector (4 downto 0);  
  component FULLADDER  
    port (x, y, cin: in std_logic;  
          s, cout: out std_logic);  
  end component;  
BEGIN  
  FA0: FULLADDER  
    port map (x(0), y(0), cin, sum(0), c(1));  
  FA1: FULLADDER  
    port map (x(1), y(1), c(1), sum(1), c(2));  
  FA2: FULLADDER  
    port map (x(2), y(2), c(2), sum(2), c(3));  
  FA3: FULLADDER  
    port map (x(3), y(3), c(3), sum(3), c(4));  
  Cout <= c(4);  
END adder_4bit_structure ;
```

Generate Statements: Syntax

For - Generate

```
Generate_Label: FOR i IN 0 TO N GENERATE  
    Logic_Expression;  
    Component_Label: Componet_name  
        PORT MAP (Port1, Port2,..., Portn ) ;  
END GENERATE ;
```

Note:

- ✓ The generate statement must have a label
- ✓ The variable i is not explicitly declared in the code; it is automatically defined as a local variable whose scope is limited to the FOR-GENERATE statement

Generate Statements: Example 1

```
ARCHITECTURE adder_4bit_structure OF adder_4bit IS  
  signal c: std_logic_vector (4 downto 0);  
  component FULLADDER  
    port (x, y, cin: in std_logic;  
          s, cout: out std_logic);  
  end component;  
BEGIN  
  C(0) <= cin;  
  G1: FOR i IN 0 TO 3 GENERATE  
    FA: FULLADDER  
      port map (x(i), y(i), c(i), sum(i), c(i+1));  
  END GENERATE ;  
  
  Cout <= c(4);  
  
END adder_4bit_structure ;
```

Generate Statements: Example 2

**Rewrite code for a 16-to-1 multiplexer using a
FOR GENERATE statement!**

Generate Statements: Example 2

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.My_package.all ;
ENTITY mux16to1 IS
  PORT ( w : IN STD_LOGIC_VECTOR(0 TO 15) ;
         s : IN STD_LOGIC_VECTOR(3 DOWNT0 0) ;
         f : OUT STD_LOGIC ) ;
END mux16to1 ;

ARCHITECTURE Structure OF mux16to1 IS
  SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
  G1: FOR i IN 0 TO 3 GENERATE
    Muxes: mux4to1 PORT MAP (
      w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNT0 0), m(i) ) ;
  END GENERATE ;
  Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;
END Structure ;
```

Generate Statements: Syntax

IF - Generate

```
Generate_Label: IF expression GENERATE  
    Logic_Expression;  
    Component_Label: Componet_name  
        PORT MAP (Port1, Port2,..., Portn ) ;  
END GENERATE ;
```

Note:

- ✓ The generate statement must have a label

Generate Statements: Example 3

**Rewrite code for a 4-to-16 decoder using
FOR-GENERATE and IF-GENERATE
statements!**

Generate Statements: Example 3

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.My_package.all ;
ENTITY dec4to16 IS
PORT ( w : IN STD LOGIC VECTOR(3 DOWNT0 0) ;
      En : IN STD LOGIC ;
      y : OUT STD_LOGIC_VECTOR (0 TO 15) ) ;
END dec4to16 ;

ARCHITECTURE Structure OF dec4to16 IS
SIGNAL m : STD LOGIC VECTOR(0 TO 3) ;
BEGIN

  G1: FOR i IN 0 TO 3 GENERATE
    Dec ri: dec2to4 PORT MAP ( w(1 DOWNT0 0), m(i), y(4*i TO 4*i+3) );
  G2: IF i=3 GENERATE
    Dec left: dec2to4 PORT MAP ( w(i DOWNT0 i-1), En, m ) ;
  END GENERATE ;
END GENERATE ;
END Structure ;
```


Sequential Assignment Statements

- ✓ The ordering of the *sequential assignment statements* may affect the meaning of the code.
- ✓ The sequential assignment statements be placed inside another type of statement, called a *process* statement
- ✓ VHDL provides two types of sequential assignment statements:
 - *if-then-else* statement
 - *case* statement

Process Statement

```
[process_label:] PROCESS [ (sensitivity_list) ] [IS]  
    [[VARIABLE or CONSTANT declarations]] -- No Signal  
BEGIN  
    --list of sequential statements such as:  
        --simple signal assignments  
        --variable assignments  
        -- case statements  
        -- if-then-else statements  
        -- For statements  
        -- WAIT statements  
END PROCESS [process_label];
```

IF-THEN-ELSE Statement

Syntax:

```
IF condition1 THEN
    --sequential statements
ELSIF condition2 THEN
    --sequential statements
ELSE
    --sequential statements
END IF;
```

Note:

The **if-then-else** statement must **ALWAYS** be inside a process construct!

IF-THEN-ELSE Statement: Example

```
-- 2-to-1 Multiplexer
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY mux2to1 IS
PORT ( w0, w1, s : IN STD LOGIC ;
        f : OUT STD LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
PROCESS ( w0, w1, s )
BEGIN
    IF s = '0' THEN
        f <= w0 ;
    ELSE
        f <= w1 ;
    END IF ;
END PROCESS ;
END Behavior ;
```

IF-THEN-ELSE Statement: QUIZ

-- 2-to-1 Multiplexer

LIBRARY ieee ;

USE ieee.std logic 1164.all ;

ENTITY mux2to1 **IS**

PORT (w0, w1, s : **IN STD LOGIC** ;
 f : **OUT STD LOGIC**) ;

END mux2to1 ;

ARCHITECTURE Behavior **OF** mux2to1 **IS**

BEGIN

PROCESS (w0, w1, s)

BEGIN

f <= w0 ;

IF s = '1' **THEN**

f <= w1 ;

END IF ;

END PROCESS ;

END Behavior ;

QUIZ

nand_gate.vhd: various implementations of architecture body

```
ARCHITECTURE model OF nand_gate IS  
    -- signal declaration (of internal signals X)  
    signal X: std_logic;  
BEGIN  
    x <= a AND b;  
    z <= NOT X;  
END model;
```

Vs.

```
ARCHITECTURE model OF nand_gate IS  
    -- signal declaration (of internal signals X)  
    signal X: std_logic;  
BEGIN  
    z <= NOT x;  
    x <= a AND b;  
END model;
```

IF-THEN-ELSE Statement: QUIZ

-- 2-to-1 Multiplexer

LIBRARY ieee ;

USE ieee.std logic 1164.all ;

ENTITY mux2to1 **IS**

PORT (w0, w1, s : **IN STD LOGIC** ;
 f : **OUT STD LOGIC**) ;

END mux2to1 ;

ARCHITECTURE Behavior **OF** mux2to1 **IS**

BEGIN

PROCESS (w0, w1, s)

BEGIN

IF s = '1' **THEN** f <= w1 ; **END IF** ;

 f <= w0 ;

END PROCESS ;

END Behavior ;

QUIZ

```
ARCHITECTURE model OF nand_gate IS  
    -- signal declaration (of internal signals X)  
    signal X: std_logic;  
BEGIN  
    z <= '0';  
    z <= NOT x;  
    x <= a AND b;  
END model;
```


QUIZ

How to write VHDL code of 4-to-1 multiplexer by using the if-then-else and process statements ?

IF-THEN-ELSE Statement: QUIZ

```
-- one-bit equality comparator.  
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY compare1 IS  
PORT ( A, B : IN STD LOGIC ;  
        AeqB : OUT STD LOGIC ) ;  
END compare1 ;  
ARCHITECTURE Behavior OF compare1 IS  
BEGIN  
  PROCESS ( A, B )  
  BEGIN  
    AeqB <= '0' ;  
    IF A = B THEN  
      AeqB <= '1' ;  
    END IF ;  
  END PROCESS ;  
END Behavior ;
```

IF-THEN-ELSE Statement: QUIZ

-- one-bit equality comparator.

LIBRARY ieee ;

USE ieee.std logic 1164.all ;

ENTITY compare1 IS

PORT (A, B : **IN** STD LOGIC ;
 AeqB : **OUT** STD LOGIC) ;

END compare1 ;

ARCHITECTURE Behavior **OF** compare1 IS

BEGIN

PROCESS (A, B)

BEGIN

IF A = B **THEN**


 AeqB <='1' ;

END IF ;

END PROCESS ;

END Behavior ;

 What is the circuit synthesized from the code?



implied memory

CASE Statement

Syntax:

```
CASE expression IS
    WHEN choice_1 =>
        --sequential statements
    WHEN choice_2 =>
        --sequential statements
        -- branches are allowed
    [WHEN OTHERS => --sequential statements ]
END CASE;
```

Note:

The **Case** statement must ALWAYS be inside a process construct!

CASE Statement

Rules:

- ✓ *expression* must evaluate to an integer, an enumerated type or a one-dimensional array
- ✓ no two choices can overlap (i.e. each choice can be covered only once)
- ✓ if the “when others” choice is not present, all possible values of the expression must be covered by the set of choices.
- ✓ **Allowed formats of *choices_k*:**

WHEN value

WHEN value_1 to value_2

WHEN value_1 | value_2 | | value N

CASE Statement: Example 1

```
-- 2-to-1 multiplexer
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY mux2to1 IS
PORT ( w0, w1, s : IN STD LOGIC ;
        f : OUT STD LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
PROCESS ( w0, w1, s )
BEGIN

...

END PROCESS ;
END Behavior ;
```

CASE Statement: Example 1

```
-- 2-to-1 multiplexer
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY mux2to1 IS
PORT ( w0, w1, s : IN STD LOGIC ;
        f : OUT STD LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
PROCESS ( w0, w1, s )
BEGIN
    CASE s IS
        WHEN '0' =>
            f <= w0 ;
        WHEN OTHERS =>
            f <= w1 ;

    END CASE ;
END PROCESS ;
END Behavior ;
```

CASE Statement: Example 2

```
-- 2-to-4 dcoder
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY dec2to4 IS
PORT ( w : IN STD LOGIC VECTOR(1 DOWNTO 0) ;
        En : IN STD LOGIC ;
        y : OUT STD LOGIC VECTOR(0 TO 3) ) ;
END dec2to4 ;
```


CASE Statement: Example 2

```
ARCHITECTURE Behavior OF dec2to4 IS  
BEGIN
```

```
END Behavior ;
```

CASE Statement: Example 2

```
ARCHITECTURE Behavior OF dec2to4 IS  
BEGIN  
  PROCESS ( w, En )  
  BEGIN  
    IF En = '1' THEN  
      CASE w IS  
        WHEN "00" =>  
          y <= "1000" ;  
        WHEN "01" =>  
          y <= "0100" ;  
        WHEN "10" =>  
          y <= "0010" ;  
        WHEN OTHERS =>  
          y <= "0001" ;  
      END CASE ;  
    ELSE  
      y <= "0000" ;  
    END IF ;  
  END PROCESS ;  
END Behavior ;
```

QUIZ

How to write VHDL code of a ALU unit by using the CASE and process statements ?

Operation	Inputs	Outputs
	<i>s2 s1 s0</i>	F
Clear	0 0 0	0 0 0 0
B−A	0 0 1	<i>B − A</i>
A−B	0 1 0	<i>A − B</i>
ADD	0 1 1	<i>A + B</i>
XOR	1 0 0	<i>A XOR B</i>
OR	1 0 1	<i>A OR B</i>
AND	1 1 0	<i>A AND B</i>
Preset	1 1 1	1 1 1 1