



**VietNam National University
University of Engineering and Technology**

Modelling Sequential Logic Circuit and FSM with VHDL


TS. Nguyễn Kiêm Hùng
Email: kiemhung@vnu.edu.vn

Laboratory for Smart Integrated Systems


Objectives

- In this lecture you will be introduced to:
 - **VHDL constructs used to implement storage elements**
 - **Design of Flip-flops, Registers, Shift registers, Counters by using VHDL**
 - **Design of sequential circuits, finite state machines**

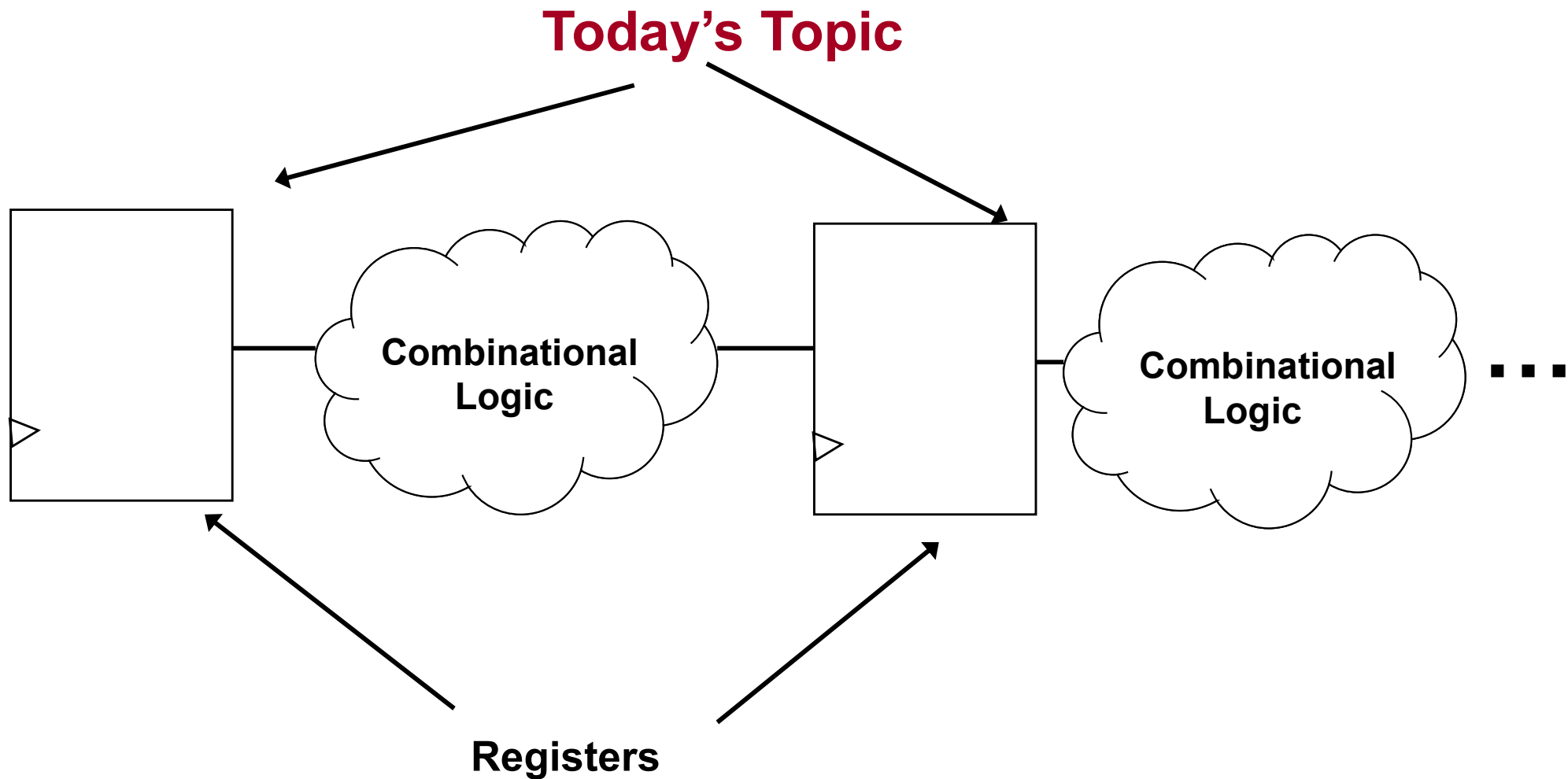Register Transfer Level (RTL) Description



VHDL Design Styles

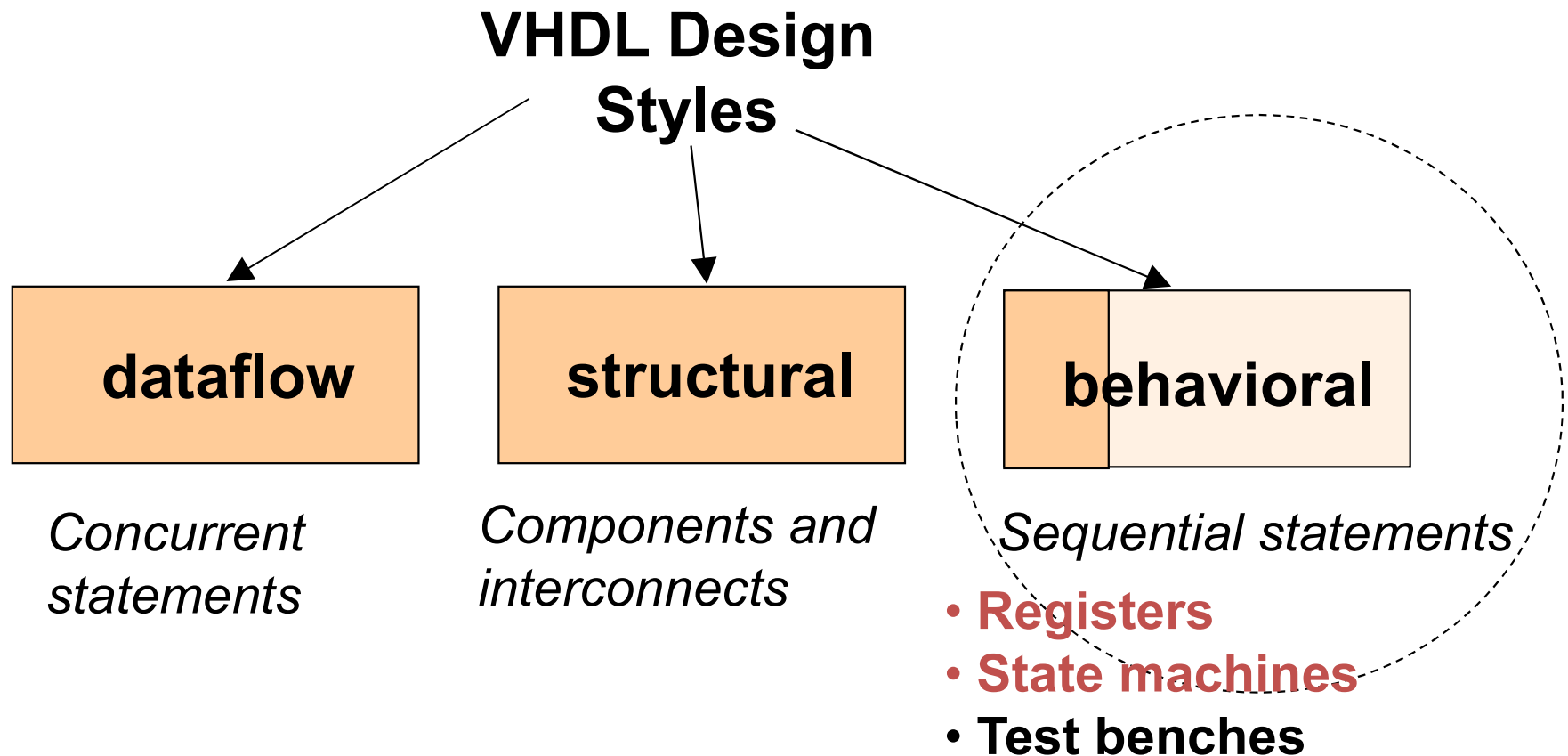

Data Objects

Data Objects

ARCHITECTURE acrhitecture_name **OF** entity_name **IS**

-- Signal and constant declaration is here

→ **SIGNAL** signal_name: data_type [:= initial value];

→ **CONSTANT** constant_name: data_type [:= initial value]; --global

BEGIN

PROCESS ()

-- Variable and Constant declaration is here

CONSTANT constant_name: data_type [:= initial value]; --local

→ **VARIABLE** constant_name: data_type [:= initial value];

BEGIN

END PROCESS ;

END acrhitecture_name ;


Signals (here)

SIGNAL represent the logic signals or wires in a circuit, and are a function of the signal assignment statements (\Leftarrow)


CONSTANT N: Integer;

SIGNAL a : STD_LOGIC_VECTOR (N-1 DOWNTO 0);

N = 1

 

N = 8

 

Constants

- ✓ a data object whose value **CANNOT** be changed.
- ✓ **DO NOT** represent a wire in a circuit
- ✓ the purpose is to improve the readability of code

constant RISE_FALL_TME: time := 2 ns;

constant DELAY1: time := 4 ns;

constant RISE_TIME, FALL_TIME: time:= 1 ns;

constant DATA_BUS: integer:= 16;

Variables

- ✓ DO NOT necessarily represent a wire in a circuit
- ✓ used to hold the results of computations and for the index variables in loops
- ✓ A variable can be updated using a variable assignment statement:

Variable_name := expression;

variable CNTR_BIT: bit :=0;

variable VAR1: boolean :=FALSE;

variable SUM: integer range 0 to 256 :=16;

variable STS_BIT: bit_vector (7 downto 0);

Generate Statements: QUIZ

ARCHITECTURE adder_4bit_structure **OF** adder_4bit **IS**

signal c: std_logic_vector (4 **downto** 0);

component FULLADDER

port (x, y, cin: **in** std_logic;
s, cout: **out** std_logic);

end component;

BEGIN

C(0) <= cin;

G1: **FOR** **i** **IN** 0 **TO** 3 **GENERATE**

FA: FULLADDER

port map (x(i), y(i), c(i), sum(i), c(i+1));

END GENERATE ;

Cout <= c(4);

V <= c(3) **xor** c(4);

END adder_4bit_structure ;

Where is the variable I stored?



Signal Vs. Variable

Signal Assignment Statement:

Signal_name **<=** expression;

Variable Assignment Statement:

Variable_name **:=** expression;

A signal changes **AFTER A DELAY** after the assignment expression is evaluated.

A variable changes instantaneously when the variable assignment is executed.

Signal Vs. Variable

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY signal_exp IS
    PORT (TRIGGER : IN STD_LOGIC;
          Result : OUT integer);
END signal_exp;
ARCHITECTURE bev OF signal_exp IS
    --SIGNAL TRIGGER, RESULT: integer := 0;
    SIGNAL s1: integer :=1;
    SIGNAL s2: integer :=2;
    SIGNAL s3: integer :=3;
BEGIN
    PROCESS
    BEGIN
        WAIT on TRIGGER;
        s1 <= s2;
        s2 <= s1 + s3;
        s3 <= s2;
        RESULT <= s1 + s2 + s3;
    END PROCESS;
END bev;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY variable_exp IS
    PORT (TRIGGER : IN STD_LOGIC;
          Result : OUT integer);
END variable_exp;
ARCHITECTURE bev OF variable_exp IS
    --SIGNAL TRIGGER, RESULT: integer := 0;
BEGIN
    PROCESS
        VARIABLE v1: integer :=1;
        VARIABLE v2: integer :=2;
        VARIABLE v3: integer :=3;
    BEGIN
        WAIT on Trigger;
        v1 := v2;
        v2 := v1 + v3;
        v3 := v2;
        Result <= v1 + v2 + v3;
    END PROCESS;
END bev;
```

Signal Vs. Variable

```
ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
  PROCESS ( w, En )
  BEGIN
    IF En = '1' THEN
      CASE w IS
        WHEN "00" =>
          y <= "1000" ;
        WHEN "01" =>
          y <= "0100" ;
        WHEN "10" =>
          y <= "0010" ;
        WHEN OTHERS =>
          y <= "0001" ;

      END CASE ;
    ELSE
      y <= "0000" ;
    END IF ;
  END PROCESS ;
END Behavior ;
END bev;
```

```
ARCHITECTURE Behavior OF dec2to4 IS
  SIGNAL t : STD_LOGIC_VECTOR(2 downto 0);
BEGIN
  PROCESS ( w, En )
  BEGIN
    t <= En&w;
    CASE t IS
      WHEN "100" =>
        y <= "1000" ;
      WHEN "101" =>
        y <= "0100" ;
      WHEN "110" =>
        y <= "0010" ;
      WHEN "111" =>
        y <= "0001" ;
      WHEN OTHERS =>
        y <= "0000" ;


    END CASE ;
  ;
  END PROCESS ;
END Behavior ;
END bev;
```

Describing Sequential Logic

Sequential Assignment Statements

- ✓ The ordering of the *sequential assignment statements* may affect the meaning of the code.
- ✓ The sequential assignment statements be placed inside another type of statement, called a *process* statement
- ✓ VHDL provides two types of sequential assignment statements:
 - **IF-THEN-ELSE** statement
 - **CASE** statement
- ✓ and more:
 - Attribute of data object
 - **WAIT** statements
 - **WAIT ON** signal changes
 - **WAIT UNTIL** an expression is true
 - **WAIT FOR** a specific amount of time
 - Etc.


Gated D Latch

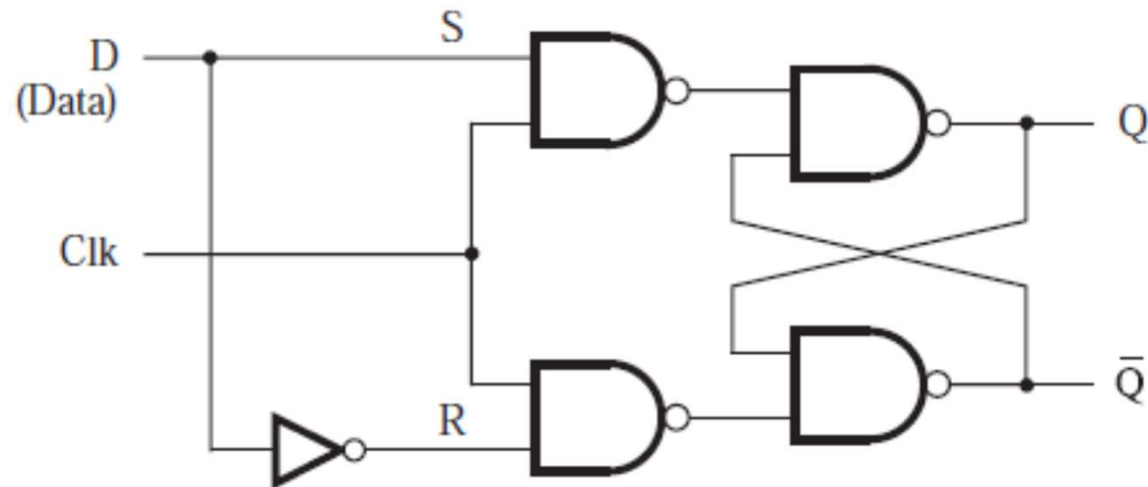

(a) Circuit

Clk	D	$Q(t+1)$
0	-	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol


Gated D Latch

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY latch IS  
    PORT ( D, Clk : IN STD LOGIC ;  
           Q : OUT STD LOGIC) ;  
END latch ;  
ARCHITECTURE Behavior OF latch IS  
BEGIN  
    PROCESS (      )  
    BEGIN  
        IF          THEN  
  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

Gated D Latch

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY latch IS  
    PORT ( D, Clk : IN STD LOGIC ;  
           Q : OUT STD LOGIC) ;  
END latch ;  
ARCHITECTURE Behavior OF latch IS  
BEGIN  
    PROCESS ( D, Clk )  
    BEGIN  
        IF Clk = '1' THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```


D FLIP-FLOP

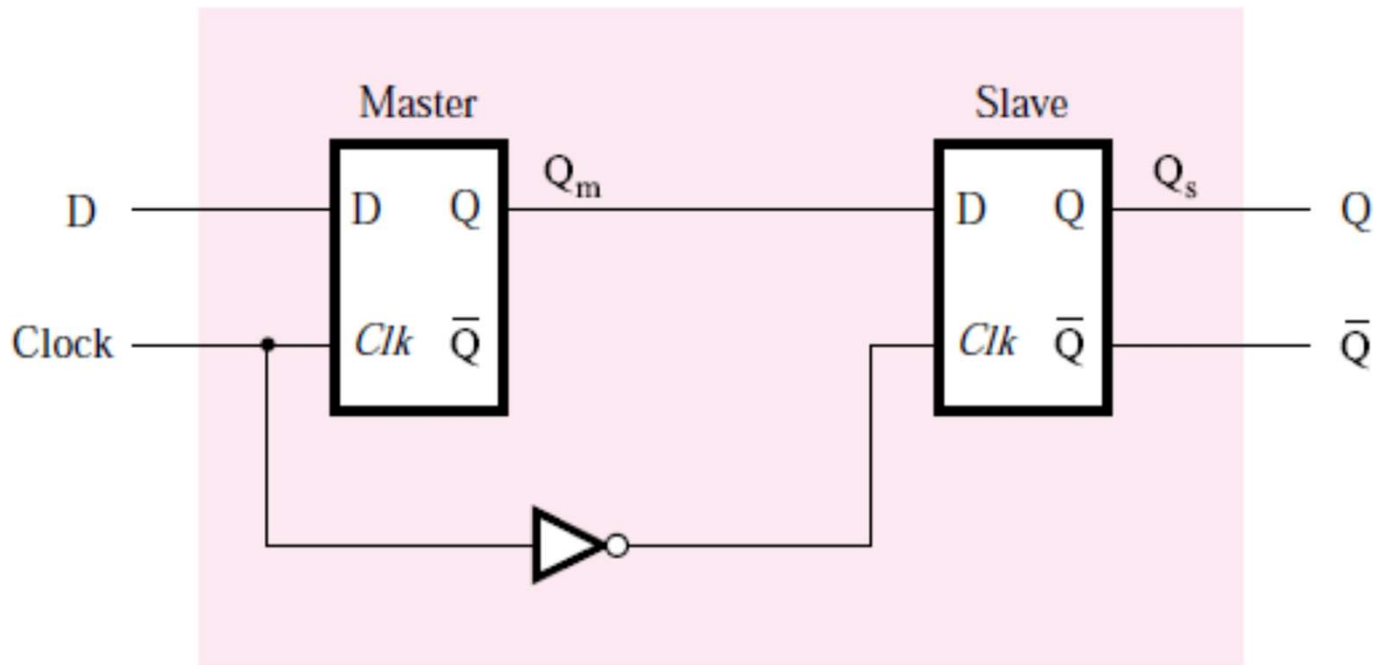

(a) Circuit

Clk	D	Q(t+1)
↓	0	0
↓	1	1
Others	-	Q(t)

(b) Characteristic table

 

(c) Graphical symbol

D FLIP-FLOP

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY flipflop IS  
    PORT ( D, Clock : IN STD LOGIC ;  
          Q : OUT STD LOGIC) ;  
END flipflop ;  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS ( Clock )  
    BEGIN  
        IF (Clock'EVENT AND Clock = '0') THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

contains only the clock signal



' EVENT attribute refers to any change in the *Clock* signal



D FLIP-FLOP: Alternative Code


```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY flipflop IS
    PORT ( D, Clock : IN STD LOGIC ;
          Q : OUT STD LOGIC) ;
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
    BEGIN
        PROCESS
            BEGIN
                WAIT UNTIL Clock'EVENT AND Clock = '0';
                Q <= D ;

            END PROCESS ;
        END Behavior ;
```

D FLIP-FLOP with ASYNCHRONOUS CLEAR

Clear	Clock	D	$Q(t+1)$
0	-	-	0
1	\uparrow	0	0
1	\uparrow	1	1
1	Others	-	$Q(t)$

(a) Characteristic table

 

D flip-flop with asynchronous clear

D FLIP-FLOP with ASYNCHRONOUS CLEAR

```

LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY flipflop IS
PORT ( D, nClear, Clock : IN STD LOGIC ;
        Q : OUT STD LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS (      )
        BEGIN


        END PROCESS ;
END Behavior ;

```

D FLIP-FLOP with ASYNCHRONOUS CLEAR

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY flipflop IS  
PORT ( D, nClear, Clock : IN STD LOGIC ;  
        Q : OUT STD LOGIC) ;  
END flipflop ;  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS ( nClear, Clock )  
    BEGIN  
        IF nClear = '0' THEN  
            Q <= '0' ;  
        ELSIF (Clock'EVENT AND Clock = '1') THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```


D FLIP-FLOP with SYNCHRONOUS CLEAR

 

A synchronous clear

Clear	Clock	D	Q(t+1)
0	↑	-	0
1	↑	0	0
1	↑	1	1
Others	Others	-	Q(t)

(b) Characteristic table

D FLIP-FLOP with SYNCHRONOUS CLEAR

```

LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY flipflop IS
PORT ( D, nClear, Clock : IN STD LOGIC ;
        Q : OUT STD LOGIC) ;
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
        BEGIN

    END PROCESS ;
END Behavior ;

```


D FLIP-FLOP with SYNCHRONOUS CLEAR

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY flipflop IS  
PORT ( D, nClear, Clock : IN STD LOGIC ;  
        Q : OUT STD LOGIC) ;  
END flipflop ;  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
  PROCESS  
    BEGIN  
      WAIT UNTIL Clock'EVENT AND Clock = '1';  
      IF nClear = '0' THEN  
        Q <= '0' ;  
      ELSE  
        Q <= D ;  
      END IF ;  
    END PROCESS ;  
END Behavior ;
```

QUIZ

Write VHDL code for a Master-slave D flip-flop with *Clear* and *Preset*?

Clear	Preset	Clock	D	Q(t+1)
0	-	↑	-	0
1	0	↑	-	1
1	1	↑	0	0
1	1	↑	1	1
Others	Others	Others	-	Q(t)

 

Master-slave D flip-flop with synchronous *Clear* and synchronous *Preset*

D flip-flop with synchronous *Clear* and *Preset*

```

LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY flipflop IS
PORT ( D, nClear, nPreset, Clock : IN STD LOGIC ;
        Q : OUT STD LOGIC) ;
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( )
        BEGIN

END PROCESS ;
END Behavior ;

```


D flip-flop with synchronous *Clear* and *Preset*

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY flipflop IS
PORT ( D, nClear, nPreset, Clock : IN STD LOGIC ;
        Q : OUT STD LOGIC) ;
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS
    BEGIN
      WAIT UNTIL Clock'EVENT AND Clock = '1';
      IF nClear = '0' THEN
        Q <= '0' ;
      ELSIF nPreset = '0' THEN
        Q <= '1' ;
      ELSE
        Q <= D ;
      END IF ;
    END PROCESS ;
  END Behavior ;
```

n-bit Register with Asynchronous Clear

Register is a set of n flip-flops is used to store n bits of information, such as an n -bit number.

Reset	En	Clk	D	Q(t+1)
1	-	-	-	0
0	1	↓	0	0
0	1	↓	1	1
Others	Others	Others	-	Q(t)

 

Standard Register Symbol

n-bit Register with Asynchronous Clear

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D : IN STD_LOGIC_VECTOR(N -1 DOWNT0 0) ;
          Reset, Clk, En : IN STD LOGIC ;
          Q : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regn ;
ARCHITECTURE Behavior OF regn IS
    BEGIN
        PROCESS (      )
            BEGIN


                END PROCESS ;
        END Behavior ;
```


n-bit Register with Asynchronous Clear

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY regn IS  
  GENERIC ( N : INTEGER := 16 ) ;  
  PORT ( D : IN STD_LOGIC_VECTOR(N -1 DOWNT0 0) ;  
         Reset, Clock, En : IN STD LOGIC ;  
         Q : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;  
END regn ;  
ARCHITECTURE Behavior OF regn IS  
  BEGIN  
    PROCESS ( Reset, Clk )  
      BEGIN  
        IF Reset = '1' THEN  
          Q <= (OTHERS => '0') ;  
        ELSIF Clk'EVENT AND Clk = '0' THEN  
          IF (En = '1') THEN  
            Q <= D ;  
          END IF;  
        END IF ;  
      END PROCESS ;  
END Behavior ;
```

FOUR-BIT PARALLEL-ACCESS SHIFT REGISTER

2-to-1 multiplexer

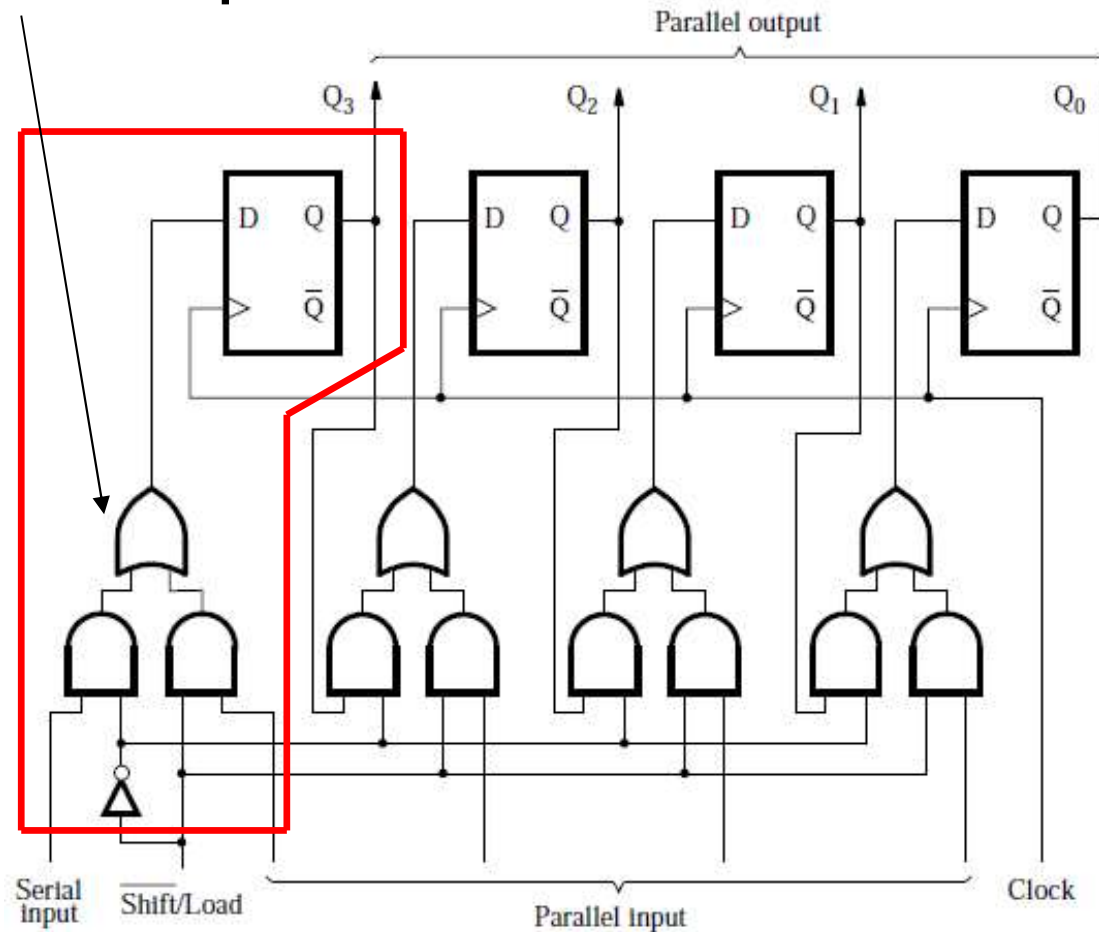

The control signal ***Shift/Load*** is used to select the mode of operation:

- If *Shift/Load* = 0, then the circuit operates as a shift register.
- If *Shift/Load* = 1, then the parallel input data are loaded into the register.

FOUR-BIT SHIFT REGISTER (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN STD_LOGIC ;
           Q : OUT STD_LOGIC ) ;
END muxdff ;

ARCHITECTURE Behavior OF muxdff IS
    BEGIN
        PROCESS
            BEGIN

                END PROCESS ;
    END Behavior ;

```

FOUR-BIT SHIFT REGISTER (1)

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY muxdff IS  
    PORT ( D0, D1, Sel, Clock : IN STD LOGIC ;  
           Q : OUT STD LOGIC ) ;  
END muxdff ;  
ARCHITECTURE Behavior OF muxdff IS  
    BEGIN  
        PROCESS  
            BEGIN  
                WAIT UNTIL Clock'EVENT AND Clock = '1' ;  
                IF Sel = '0' THEN  
                    Q <= D0 ;  
                ELSE  
                    Q <= D1 ;  
                END IF ;  
            END PROCESS ;  
    END Behavior ;
```

FOUR-BIT SHIFT REGISTER (2)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY shift4 IS
PORT ( D : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        L, w, Clock : IN STD LOGIC ;
        Q : BUFFER STD LOGIC VECTOR(3 DOWNTO 0) ) ;
END shift4 ;
ARCHITECTURE Structure OF shift4 IS
  COMPONENT muxdff
    PORT ( D0, D1, Sel, Clock : IN STD LOGIC ;
          Q : OUT STD LOGIC ) ;
  END COMPONENT ;
BEGIN

END Structure ;

```

FOUR-BIT SHIFT REGISTER (2)

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY shift4 IS
PORT ( D : IN STD LOGIC VECTOR(3 DOWNT0 0) ;
        L, w, Clock : IN STD LOGIC ;
        Q : BUFFER STD LOGIC VECTOR(3 DOWNT0 0) ) ;
END shift4 ;
ARCHITECTURE Structure OF shift4 IS
  COMPONENT muxdff
    PORT ( D0, D1, Sel, Clock : IN STD LOGIC ;
          Q : OUT STD LOGIC ) ;
  END COMPONENT ;
  BEGIN
    Stage3: muxdff PORT MAP ( w, D(3), L, Clock, Q(3) ) ;
    Stage2: muxdff PORT MAP ( Q(3), D(2), L, Clock, Q(2) ) ;
    Stage1: muxdff PORT MAP ( Q(2), D(1), L, Clock, Q(1) ) ;
    Stage0: muxdff PORT MAP ( Q(1), D(0), L, Clock, Q(0) ) ;
  END Structure ;
```

FOUR-BIT SHIFT REGISTER: Alternative code

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY shift4 IS  
PORT ( D : IN STD LOGIC VECTOR(3 DOWNT0 0) ;  
        Clock : IN STD LOGIC ;  
        L, w : IN STD LOGIC ;  
        Q : BUFFER STD LOGIC VECTOR(3 DOWNT0 0) ) ;  
END shift4 ;  
ARCHITECTURE Behavior OF shift4 IS  
  BEGIN  
    PROCESS  
      BEGIN  
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;  
        IF L = '1' THEN  
          Q <= D ;  
        ELSE  
          Q(0) <= Q(1) ;  
          Q(1) <= Q(2) ;  
          Q(2) <= Q(3) ;  
          Q(3) <= w ;  
        END IF ;  
      END PROCESS ;  
END Behavior ;
```

FOUR-BIT SHIFT REGISTER: QUIZ

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY shift4 IS
PORT ( D : IN STD LOGIC VECTOR(3 DOWNT0 0) ;
      Clock : IN STD LOGIC ;
      L, w : IN STD LOGIC ;
      Q : BUFFER STD LOGIC VECTOR(3 DOWNT0 0) ) ;
END shift4 ;
ARCHITECTURE Behavior OF shift4 IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL Clock'EVENT AND Clock = '1' ;
    IF L = '1' THEN
      Q <= D ;
    ELSE
      Q(3) <= w ;
      Q(2) <= Q(3) ;
      Q(1) <= Q(2) ;
      Q(0) <= Q(1) ;
    END IF ;
  END PROCESS ;
END Behavior ;
```


QUIZ


Write VHDL code for a n-bit shift register by using **GENERIC** declaration to set the number of bits of the register?

N-BIT SHIFT REGISTER

```
LIBRARY ieee ;  
USE ieee.std logic 1164.all ;  
ENTITY shiftn IS  
    GENERIC ( N : INTEGER := 8 ) ;  
    PORT (D: IN STD LOGIC VECTOR(N-1 DOWNT0 0) ;  
          Clock : IN STD LOGIC ;  
          L, w : IN STD LOGIC ;  
          Q : BUFFER STD LOGIC VECTOR(N-1 DOWNT0 0) ) ;  
END shiftn ;  
ARCHITECTURE Behavior OF shiftn IS  
    BEGIN  
        PROCESS  
            BEGIN  
                WAIT UNTIL Clock'EVENT AND Clock '1' ;  
                IF L = '1' THEN  
                    Q <= D ;  
                ELSE  
                    Genbits: FOR i IN 0 TO N-2 LOOP  
                        Q(i) <= Q(i + 1) ;  
                    END LOOP ;  
                    Q(N-1) <= w ;  
                END IF ;  
            END PROCESS ;  
        END Behavior ;
```

COUNTER

 - ✓ a synchronous register (CLK tick) that increments or decrements its output (Q) at an edge of the clock signal
- ✓ If the enable signal (En) is low the output remains always unchanged.
- ✓ If the load signal (Load) is high the output is changed to the input (D) value on the clock edge.
- ✓ the up signal (Up) is high the output is increased at the next clock edge



Symbol

FOUR-BIT UP COUNTER

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
USE ieee.std logic unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, nReset, E : IN STD LOGIC ; --E: enable
          Q : OUT STD LOGIC VECTOR (3 DOWNT0 0)) ;
END upcount ;
ARCHITECTURE Behavior OF upcount IS

BEGIN
    PROCESS (      )
        BEGIN

END PROCESS ;

END Behavior ;
```

FOUR-BIT UP COUNTER

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
USE ieee.std logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, nReset, E : IN STD LOGIC ;
           Q : OUT STD LOGIC VECTOR (3 DOWNT0 0)) ;
END upcount ;
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD LOGIC VECTOR (3 DOWNT0 0) ;
BEGIN
    PROCESS ( Clock, nReset )
    BEGIN
        IF nReset = '0' THEN
            Count <= "0000";
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

QUIZ

Write VHDL code for a n-bit up counter by using **GENERIC** declaration to set the number of bits of the counter?

N-BIT DOWN COUNTER

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
USE ieee.std logic_unsigned.all ;
ENTITY downcnt IS
    GENERIC ( modulus : INTEGER := 8 ) ;
    PORT ( Clock, L, E : IN STD LOGIC ;
          Q : OUT INTEGER RANGE 0 TO (modulus-1 ) ;
    END downcnt ;
ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
        BEGIN

END PROCESS;

END Behavior ;
```

Requirement:

- On the positive clock edge, if $L = 1$, the counter is loaded with the value *modulus-1*, and if $L = 0$, the count is decremented.
- The counter also includes an enable input, E . Setting $E = 1$ allows the count to be decremented when an active clock edge occurs

N-BIT DOWN COUNTER

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY downcnt IS
    GENERIC ( modulus : INTEGER := 8 ) ;
    PORT ( Clock, L, E : IN STD_LOGIC ;
          Q : OUT INTEGER RANGE 0 TO (modulus - 1));
END downcnt;
ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus - 1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF L = '1' THEN
            Count <= modulus - 1 ;
        ELSE
            IF E = '1' THEN
                IF Count = 0 then
                    Count <= modulus - 1;
                ELSE
                    Count <= Count - 1 ;
                END IF;
            END IF ;
        END IF ;
    END PROCESS;
    Q <= Count ;
END Behavior ;
```


QUIZ


Write VHDL code for a n-bit up/down counter by using **GENERIC** declaration to set the number of bits of the counter. The counter has a port, called *dir*, that indicates the counting direction of the counter: if *dir* = 1 the counter functions as a up counter, and if *dir* = 0 the counter functions as a down counter

Synchronous Sequential Circuits

Synchronous Sequential Circuits

Sequential Circuits: the outputs depend on the past behavior of the circuit, as well as on the present values of inputs.

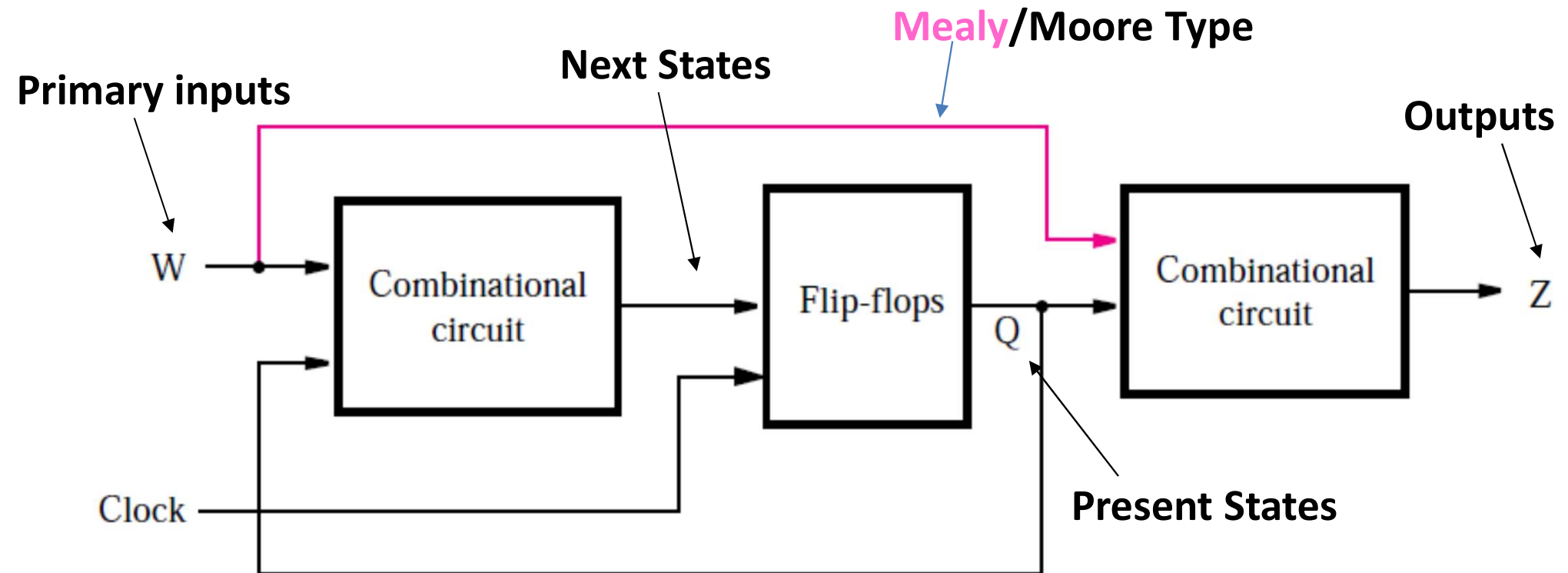
Synchronous: a clock signal is used to control the operation of a sequential circuit



Finite State Machines (FSMs)


Synchronous Sequential Circuits

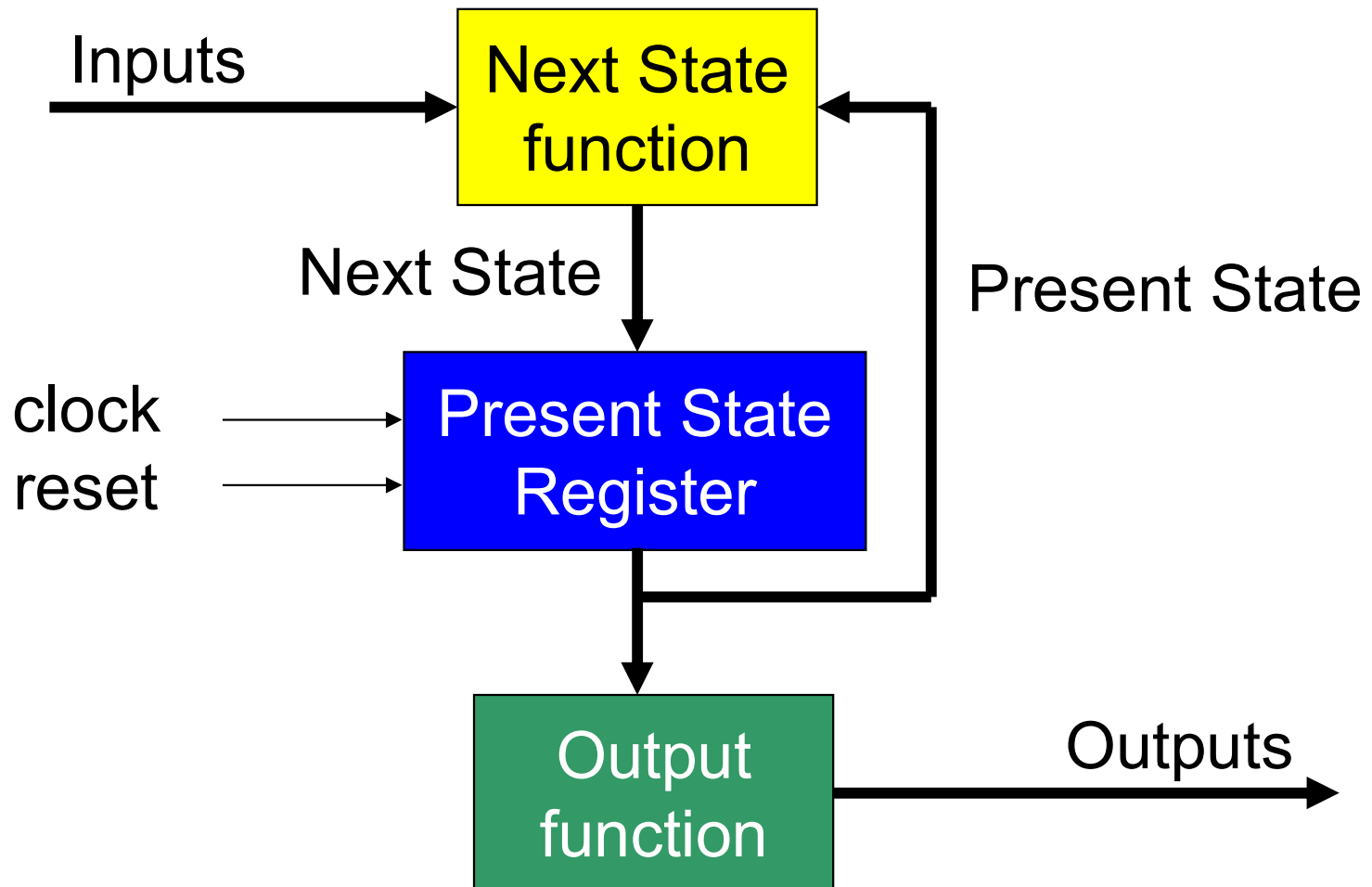- Moore FSM: Output Is a Function of a Present State Only




Synchronous Sequential Circuits

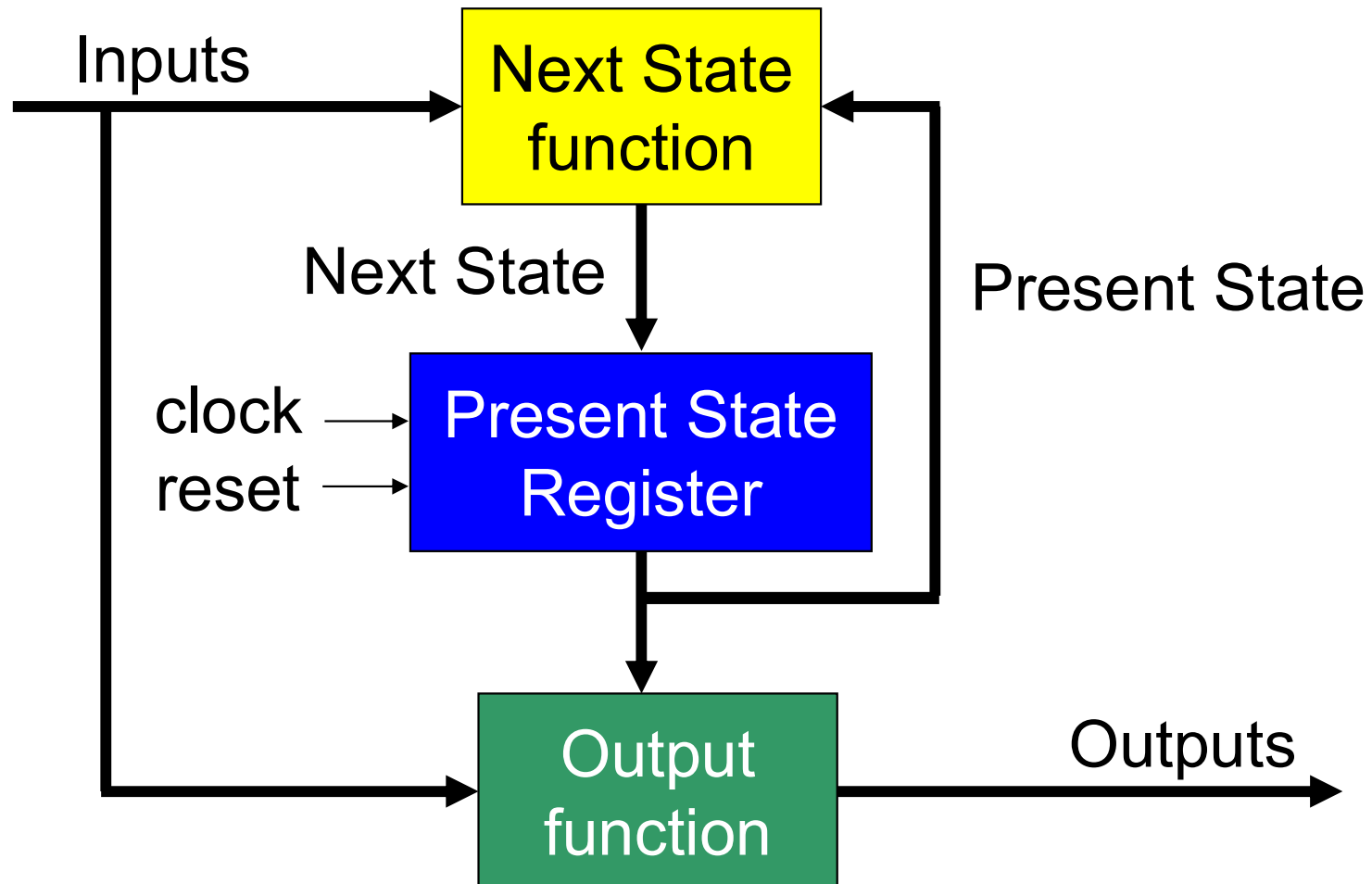- Mealy FSM: Output Is a Function of a Present State and Inputs




Synchronous Sequential Circuits

State diagram of Moore machine

 

Synchronous Sequential Circuits

State diagram of Mealy machine

 

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs Can Be Functionally Equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM (2)

- Mealy FSM Computes Outputs as soon as Inputs Change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has No Combinational Path Between Inputs and Outputs
 - Moore FSM is more likely to have a shorter critical path

Moore FSM - Example 1

 
- Moore FSM that Recognizes Sequence “10”



Meaning of states:	S0: No elements of the Sequence “10” observed	S1: “1” observed	S2: “10” observed

Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”




Meaning
of states:

S0: No elements of the sequence observed
--

S1: “1” observed

Moore & Mealy FSMs – Example 1

 


FSMs in VHDL

- Draw the state diagram using a graphical tool
- **Write VHDL code that represents the state diagram**
 - Finite State Machines Can Be Easily Described With Processes
 - Synthesis Tools Understand FSM Description If Certain Rules Are Followed
 - ✓ **State transitions** should be described **in a process** sensitive to *clock* and *asynchronous reset* signals **only**
 - ✓ **Outputs** described **as concurrent statements** outside the process


Moore FSM in VHDL

process(clock, reset)

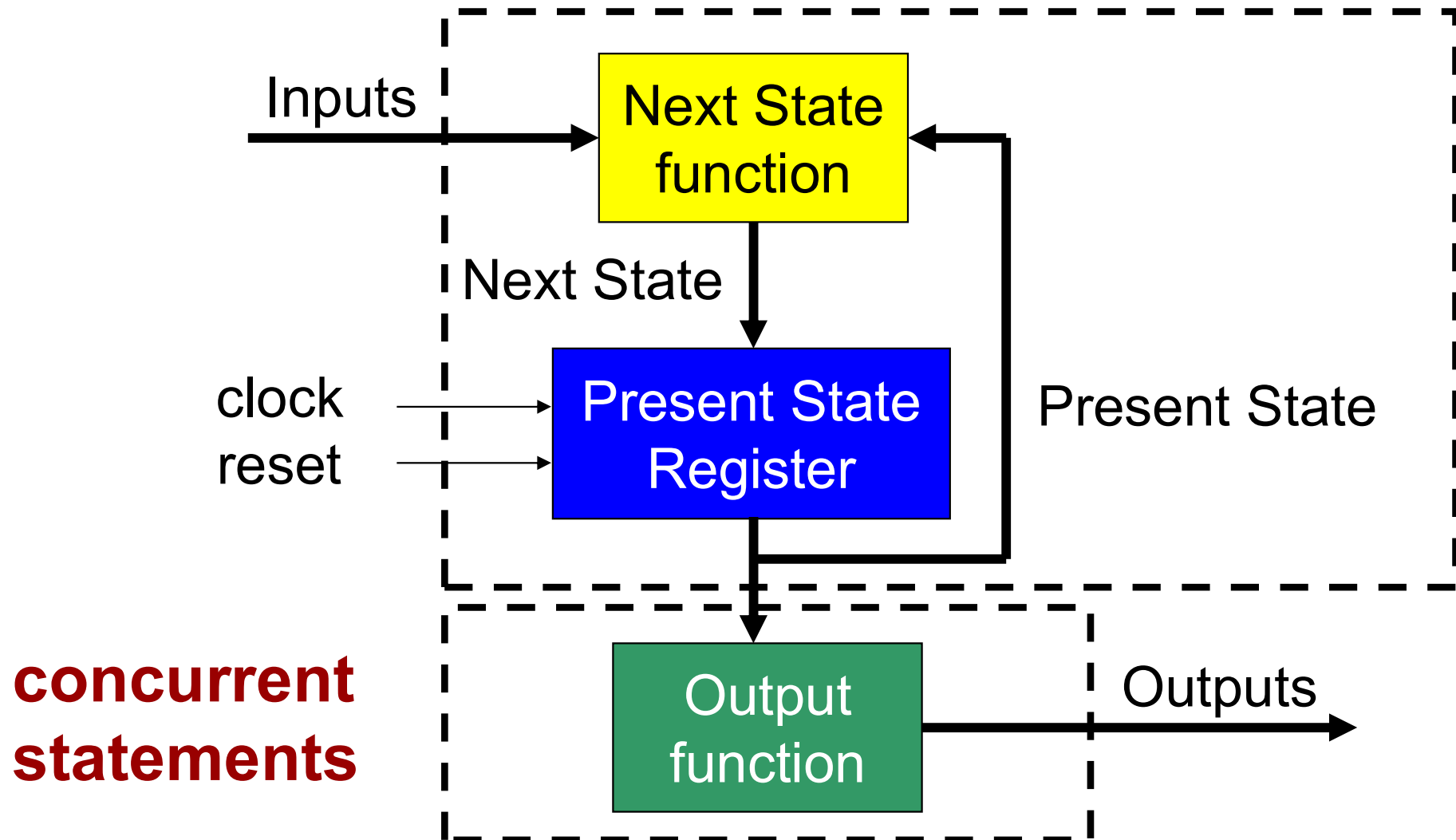

Mealy FSM in VHDL

process(clock, reset)

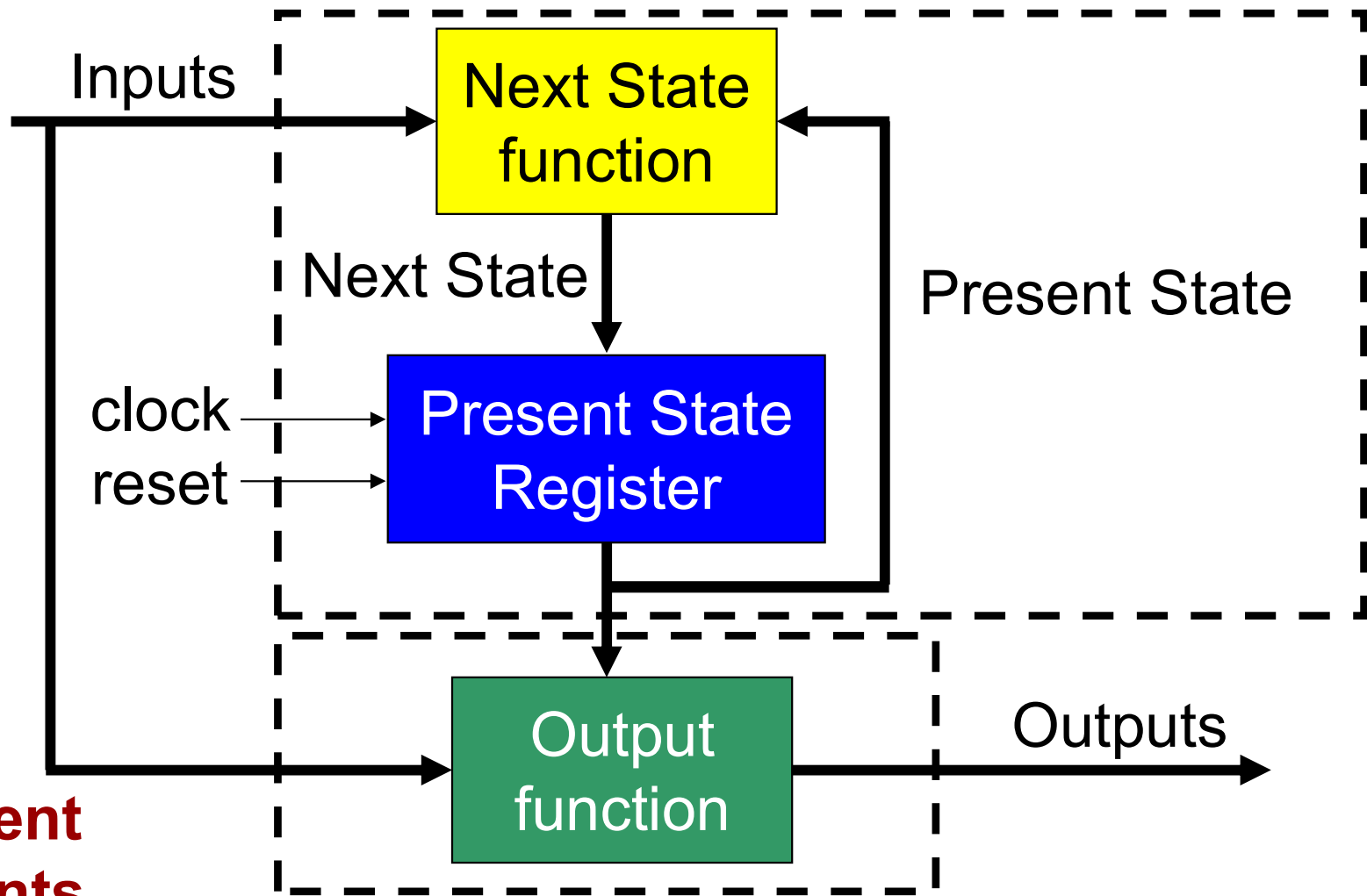

**concurrent
statements**

Example of Moore machine

Sequence detector recognizes sequence “11”:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of a clock signal.
3. The output z is equal to 1 if during two consecutive clock cycles the input w was equal to 1. Otherwise, the value of z is equal to 0.

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Example of Moore machine


Building state diagram: how many states are needed and which transitions are possible from one state to another

State table

State diagram of “11” Sequence detector

 Example of Moore machine

Building state diagram: how many states are needed and which transitions are possible from one state to another




Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

State table

State diagram of “11” Sequence detector

Example of Moore machine

Implementation of the circuit

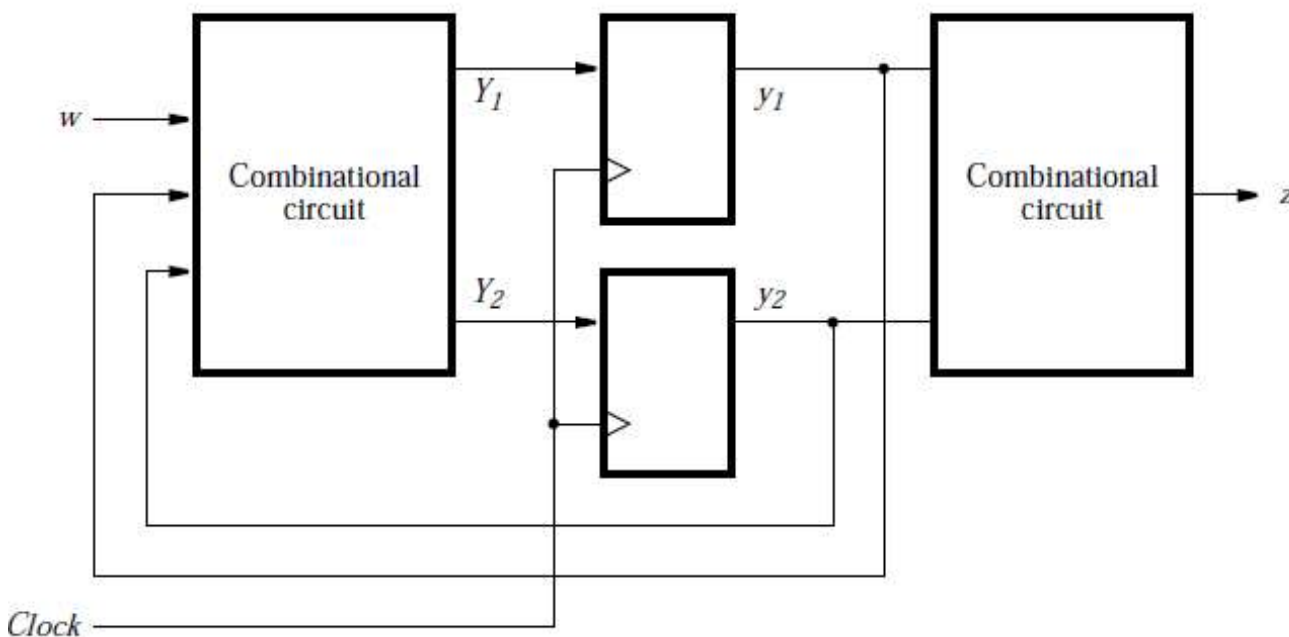

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

State-assigned table

Sequential circuit

VHDL CODE

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY detector11 IS
    PORT ( Clock, nReset, w : IN STD LOGIC ;
          z : OUT STD LOGIC ) ;
    END detector11 ;
ARCHITECTURE Behavior OF detector11 IS
    TYPE State_type IS (A, B, C) ;
    SIGNAL y : State_type ;
    BEGIN
        -- State transitions
        PROCESS ( nResetn, Clock )
            BEGIN

        END PROCESS ;
        -- Output function

    END Behavior ;
```

VHDL CODE

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY detector11 IS
    PORT ( Clock, nReset, w : IN STD LOGIC ;
          z : OUT STD LOGIC ) ;
END detector11 ;
ARCHITECTURE Behavior OF detector11 IS
    TYPE State_type IS (A, B, C) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( nResetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN
                        y <= A ;
```

VHDL CODE

```
ELSE
    y <= B ;
END IF ;
WHEN B =>
    IF w = '0' THEN
        y <= A ;
    ELSE
        y <= C ;
    END IF ;
WHEN C =>
    IF w = '0' THEN
        y <= A ;
    ELSE
        y <= C ;
    END IF ;
END CASE ;
END IF ;
END PROCESS ;
z <= '1' WHEN y = C ELSE '0' ;
END Behavior ;
```

QUIZ

Write testbench and use ModelSim to simulate the above detector?

Example of Mealy machine

Sequence detector recognizes sequence “11”:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of a clock signal.
3. The output z is equal to 1 if during two consecutive clock cycles the input w was equal to 1. Otherwise, the value of z is equal to 0.

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Example of Mealy machine


Building state diagram: how many states are needed and which transitions are possible from one state to another

State diagram of “11” Sequence detector

State table

 Example of Mealy machine

Building state diagram: how many states are needed and which transitions are possible from one state to another




State diagram of “11” Sequence detector

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

State table

Example of Mealy machine

Implementation of the circuit

 

Sequential circuit

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A	0	1	0	0
B	1	1	0	1

State-assigned table

VHDL CODE

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY detector11 IS
    PORT ( Clock, nReset, w : IN STD LOGIC ;
          z : OUT STD LOGIC ) ;
    END simple ;
ARCHITECTURE Behavior OF detector11 IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
    BEGIN
        -- State transitions
        PROCESS ( nResetn, Clock )
            BEGIN

        END PROCESS ;
        -- Output function

    END Behavior ;
```

VHDL CODE

```
LIBRARY ieee ;
USE ieee.std logic 1164.all ;
ENTITY detector11 IS
    PORT ( Clock, Resetn, w : IN STD LOGIC ;
          z : OUT STD LOGIC ) ;
END detector11 ;
ARCHITECTURE Behavior OF detector11 IS
    TYPE State type IS (A, B) ;
    SIGNAL y : State type ;
BEGIN
    PROCESS ( Resetn, Clock ) -- for state transition
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN y <= A ;
                    ELSE
                        y <= B ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

VHDL CODE

```
    WHEN B =>
        IF w = '0' THEN
            y <= A ;
        ELSE
            y <= B ;
        END IF ;
    END CASE ;
END IF ;
END PROCESS ;
PROCESS ( y, w ) -- for output transition
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

QUIZ

Write testbench and use ModelSim to simulate the above detector?

Writing Testbenches

```
ENTITY detector11_tb IS END ENTITY;
--
ARCHITECTURE bev OF detector11_tb IS
    SIGNAL w, clock, nReset, z : std_logic := '0';
    COMPONENT detector11 IS
        PORT ( Clock, nReset, w : IN STD LOGIC ;
              z : OUT STD LOGIC ) ;
    END COMPONENT ;

BEGIN
    DUT1: detector110
        PORT MAP (Clock, nReset, w, z);
    rst <= '1' AFTER 31 NS, '0' AFTER 54 NS;
    clock <= NOT clock AFTER 7 NS WHEN NOW<=165 NS ELSE '0';
    PROCESS BEGIN
        WAIT FOR 23 NS; w <= '0';
        WAIT FOR 21 NS; w <= '1';
        WAIT FOR 19 NS; w <= '1';
        WAIT FOR 31 NS; w <= '0';
        WAIT;
    END PROCESS;
    PROCESS (w) BEGIN
        REPORT "Signal w changed to:" & std_logic'IMAGE(w) & " at " & TIME'IMAGE(NOW) SEVERITY NOTE;
    END PROCESS;
END ARCHITECTURE bev;
```