



**VietNam National University
University of Engineering and Technology**

CMOS TECHNOLOGY FOR VLSI IMPLEMENTATION

TS. Nguyễn Kiêm Hùng

Email: kiemhung@vnu.edu.vn

Laboratory for Smart Integrated Systems

Objectives

- In this lecture you will be introduced to:
 - How transistors operate and form simple switches
 - CMOS logic gates
 - Basic characteristics of electronic circuits
 - CMOS Fabrication


Outline



- **MOS Transistors**
- NMOS vs. CMOS Logic Circuits
- MOS Logic Circuits
- CMOS Fabrication and Layout
- Summary


Review: Digital System Example

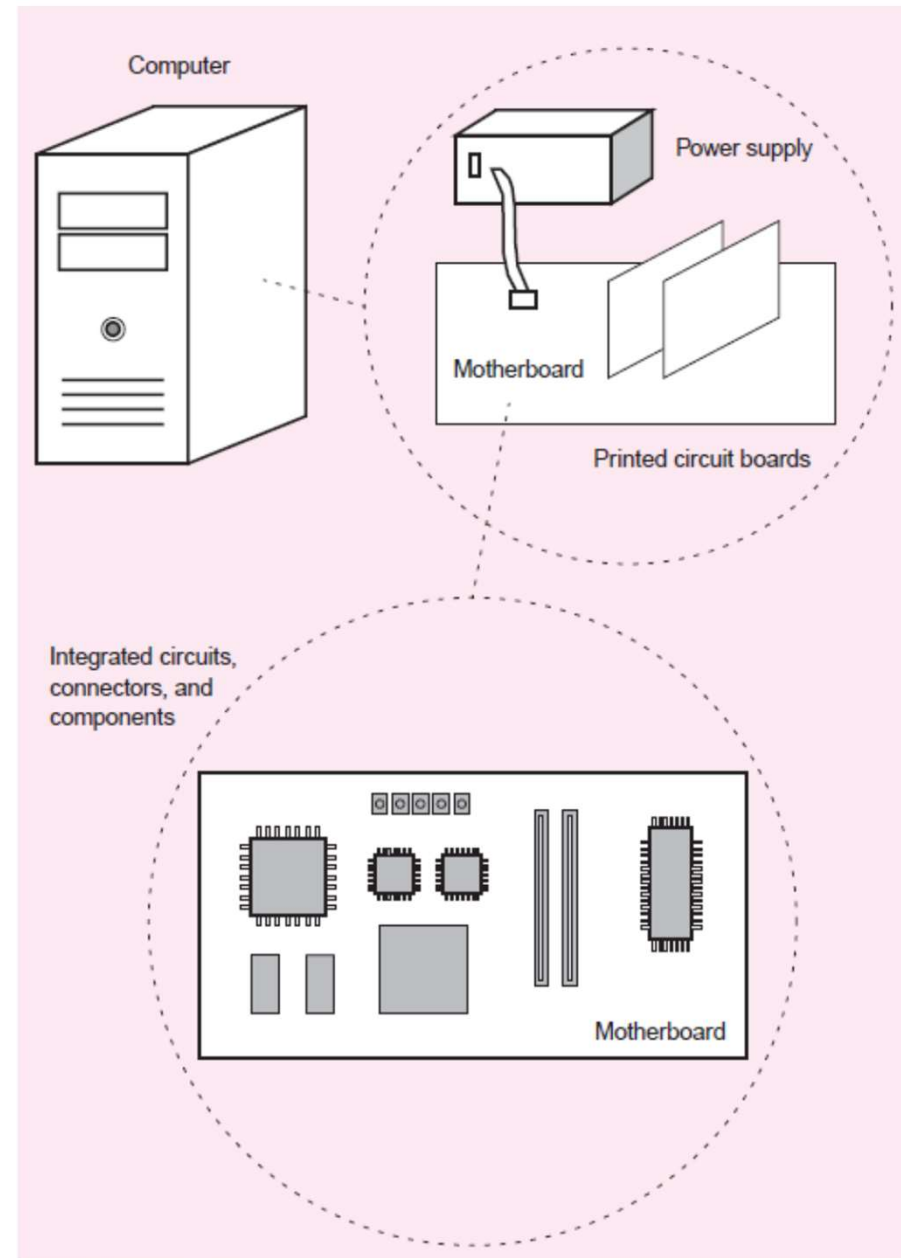- **Structure of Computer**
 - Motherboard
 - Power Supply
 - Slots & daughter boards
 - ICs (Integrated Circuits)



Review: Digital System Example

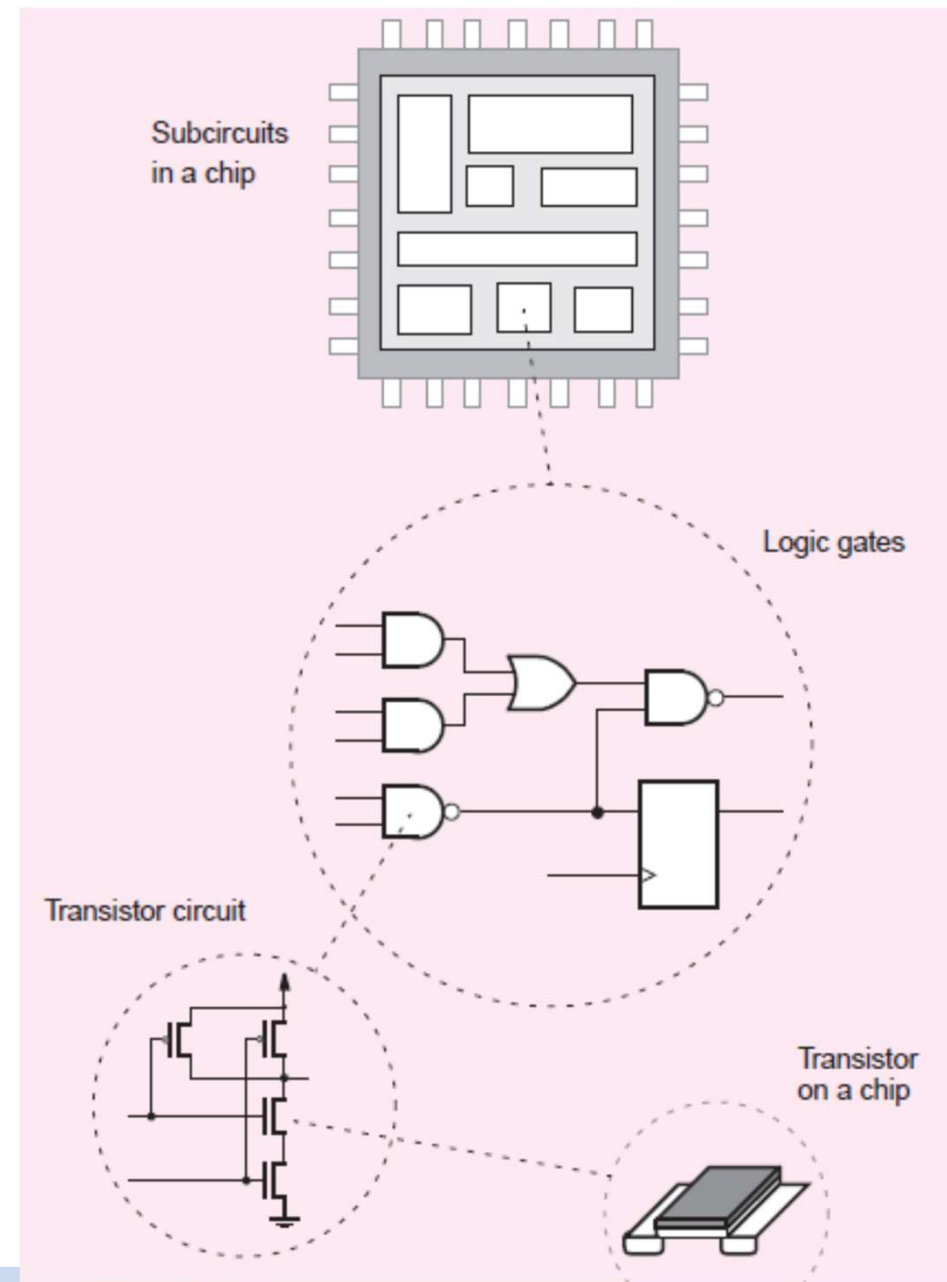
- Structure of a IC
 - Include several Sub-circuits
 - arithmetic operations, store data, or control the flow of data
 - Logic circuit comprises a network of connected *logic gates*
 - logic gate performs a very simple function
 - Logic gates are built with transistors
 - Transistors are implemented by fabricating various layers of material on a silicon chip



MOS TRANSISTOR

- **A Metal-Oxide-Semiconductor (*MOS*) structure**

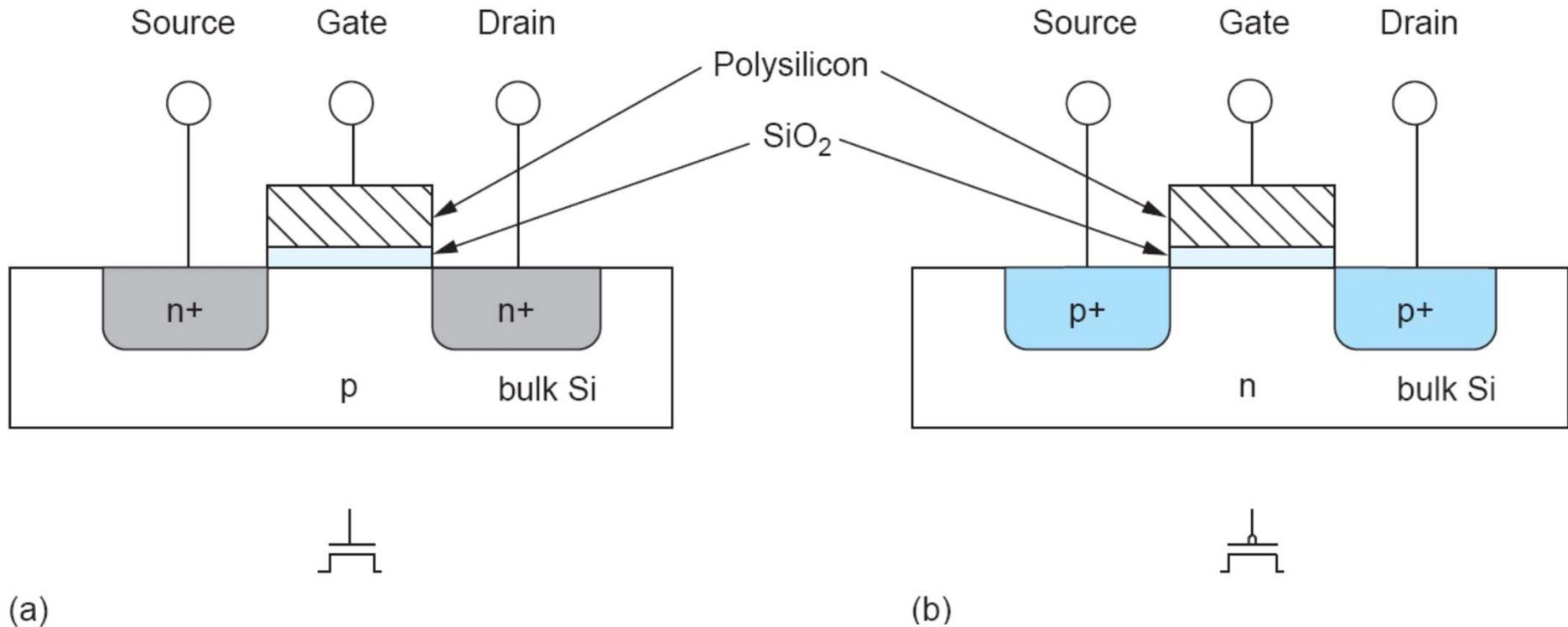
- superimposing several layers of conducting and insulating materials
- chemical processing steps: oxidation of the silicon, selective introduction of dopants, and deposition and etching of metal wires and contacts



nMOS transistor (a) and pMOS transistor (b)

nMOS TRANSISTOR

 
- Four terminals: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal – oxide – semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal*



* Metal gates are returning today!


nMOS TRANSISTOR

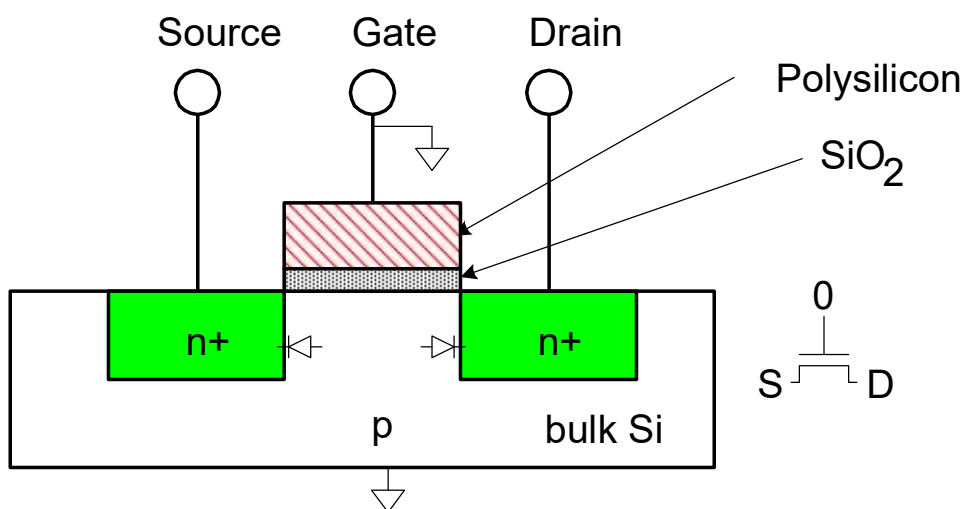- Body is usually tied to ground (0 V)
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS TRANSISTOR

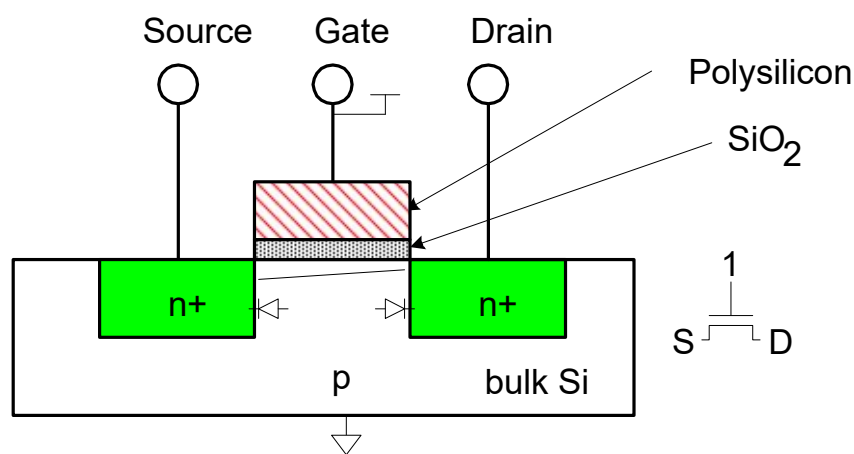- When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS TRANSISTOR

 - Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage


- $GND = 0\text{ V}$
- In 1980's, $V_{DD} = 5\text{V}$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$

MOS TRANSISTOR

 
- Transistor symbols and Switch-level models




(b) NMOS transistor

 


(b) PMOS transistor

 

 
(c) Simplified symbol for an NMOS transistor



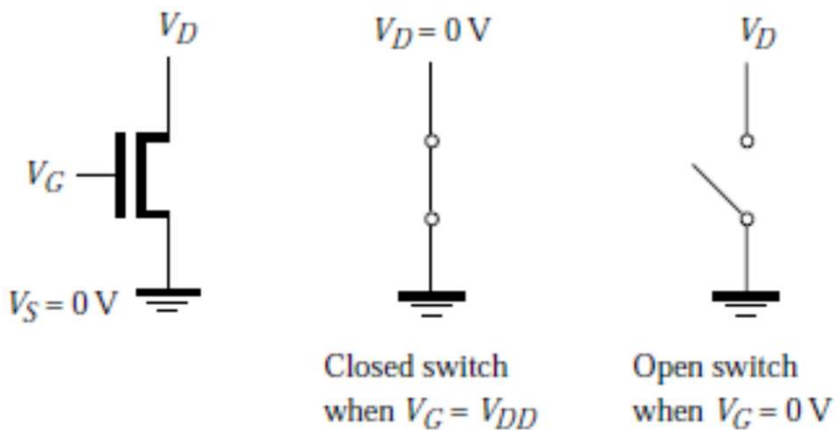(c) Simplified symbol for an PMOS transistor




nMOS Transistor

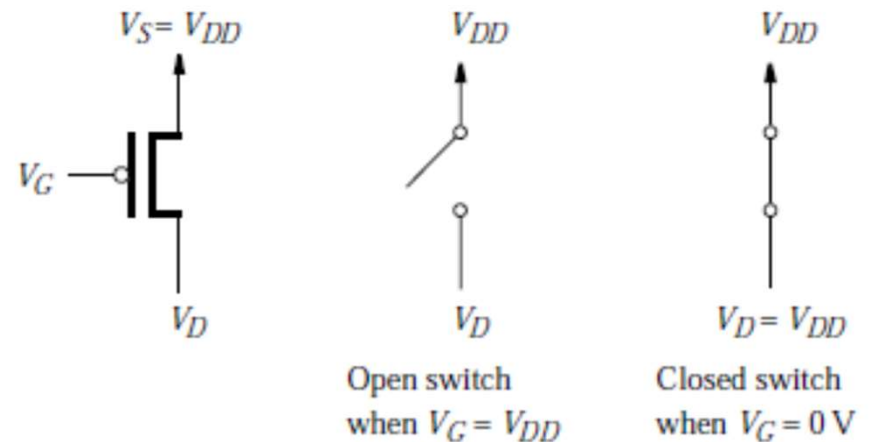

pMOS Transistor

MOS TRANSISTOR







- Pass transistor

 

Pass transistor strong and degraded outputs

MOS TRANSISTOR


- Transmission gate

   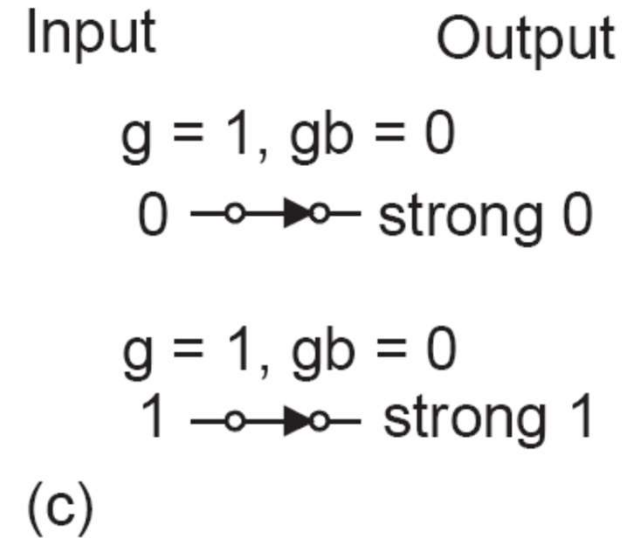  


Transmission gate

MOS TRANSISTOR

- Inverting gate: *fully restored*

 


Bad non-inverting buffer

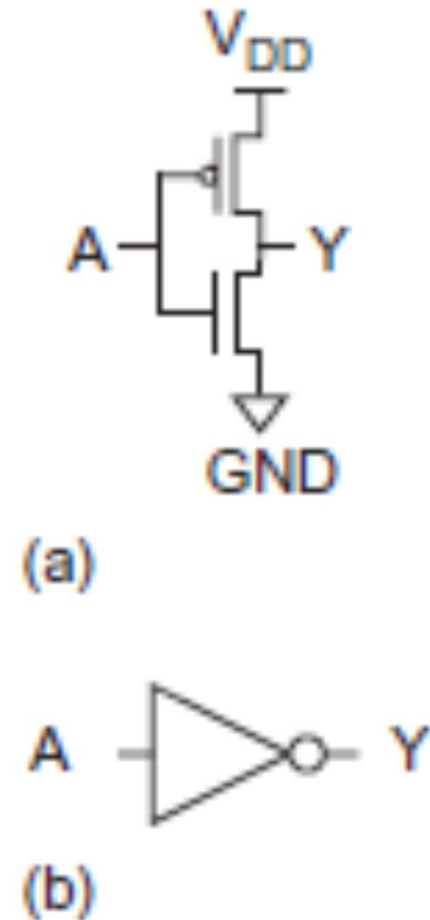

Inverter schematic (a) and symbol (b)

MOS TRANSISTOR

 - Solution for building non-inverting gates




Various implementations of a CMOS 4-input AND gate

Outline

- MOS Transistors
- • **NMOS vs. CMOS Logic Circuits**
- MOS Logic Circuits
- CMOS Fabrication and Layout
- Summary

NMOS vs. CMOS LOGIC CIRCUITS

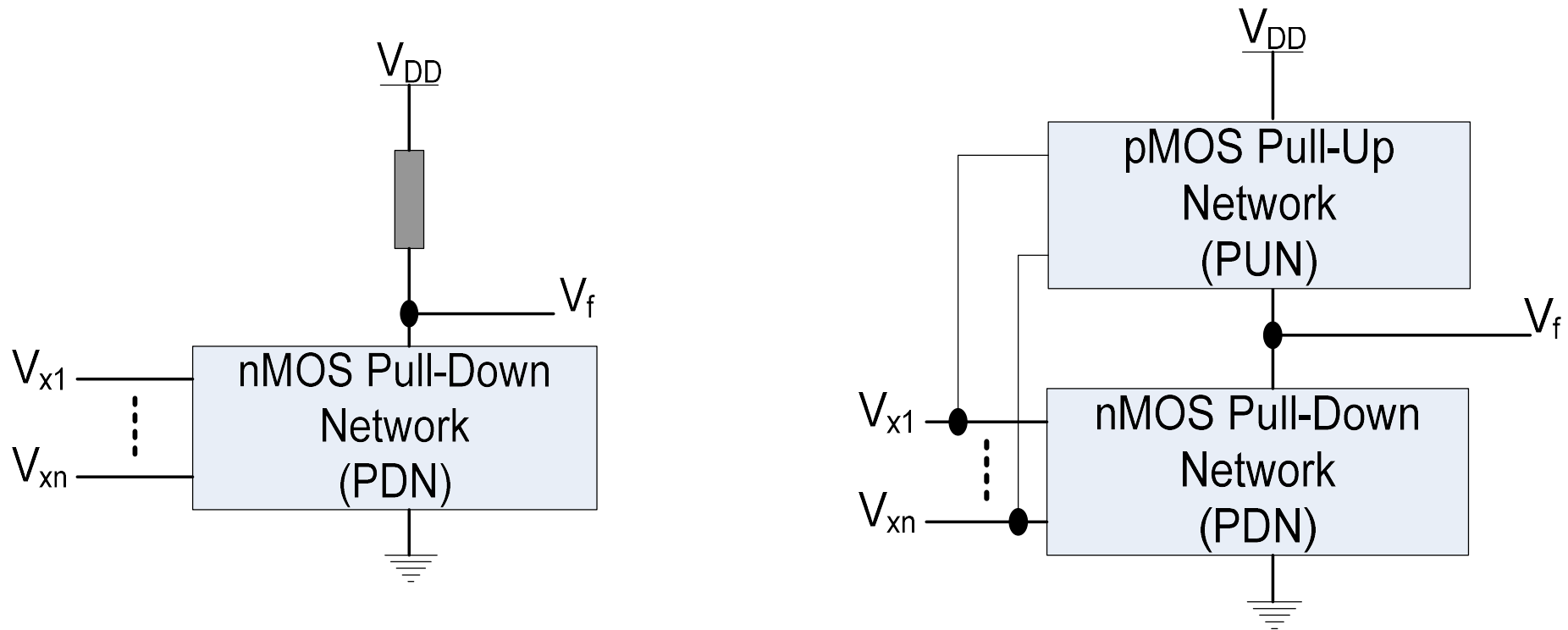- **Pull-down Network (PDN)**: composed of NMOS transistors in series (or parallel)
- **Pull-up Network (PUN)**: composed of PMOS transistors in parallel (or series)
- PDN and PUN networks are complements of each other, have equal numbers of transistors:
 - either the PDN pulls V_f down to Gnd or the PUN pulls V_f up to V_{DD}



Structure of a NMOS circuit

te


Structure of a CMOS circuit

Outputs of CMOS LOGIC CIRCUITS

- **High impedance or floating Z output:** when both pull-up and pull-down are OFF
 - Importance in multiplexers, memory elements, and tristate bus drivers
- **Contention (or Crowbarred) X level:** when both pull-up and pull-down are simultaneously turned ON
 - indeterminate output level
 - dissipates static power
 - is usually an unwanted condition

Output states of CMOS gates

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z	1
Pull-down ON	0	Contention (X)

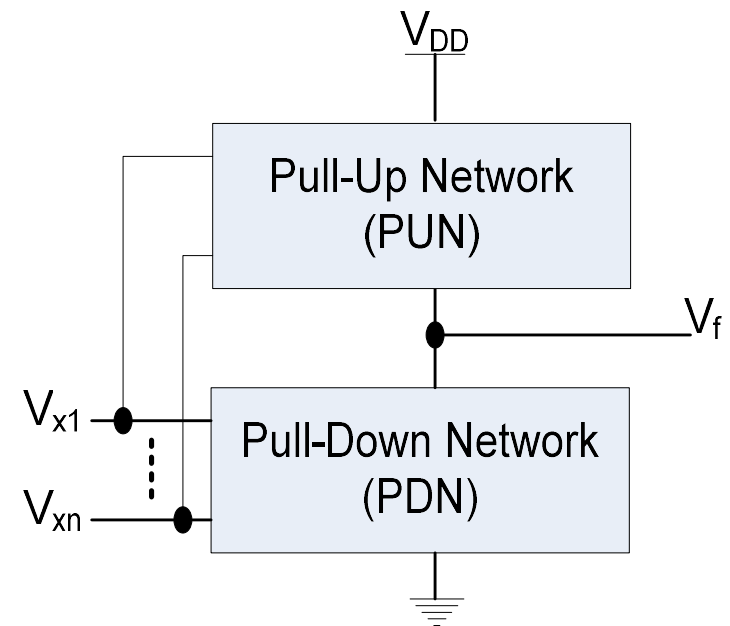

Structure of a CMOS circuit

Outline



- MOS Transistors
- NMOS vs. CMOS Logic Circuits
- • **CMOS Logic Circuits**
- CMOS Fabrication and Layout
- Summary

CMOS LOGIC CIRCUITS

- Inverter: $Y = \overline{A}$

Inverter truth table

A	Y
0	1
1	0

 
 


Symbol (a) and (b) Inverter schematic

MOS LOGIC CIRCUITS


- 2-input NAND Gate: $Y = \overline{A \cdot B}$

A	B	Y
0	0	
0	1	
1	0	
1	1	

  

MOS LOGIC CIRCUITS

 - **k-input NAND Gate:**
 - k series nMOS transistors
 - k parallel pMOS transistor:




3-input NAND gate schematic

MOS LOGIC CIRCUITS

- 2-input NOR Gate:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A + B}$$

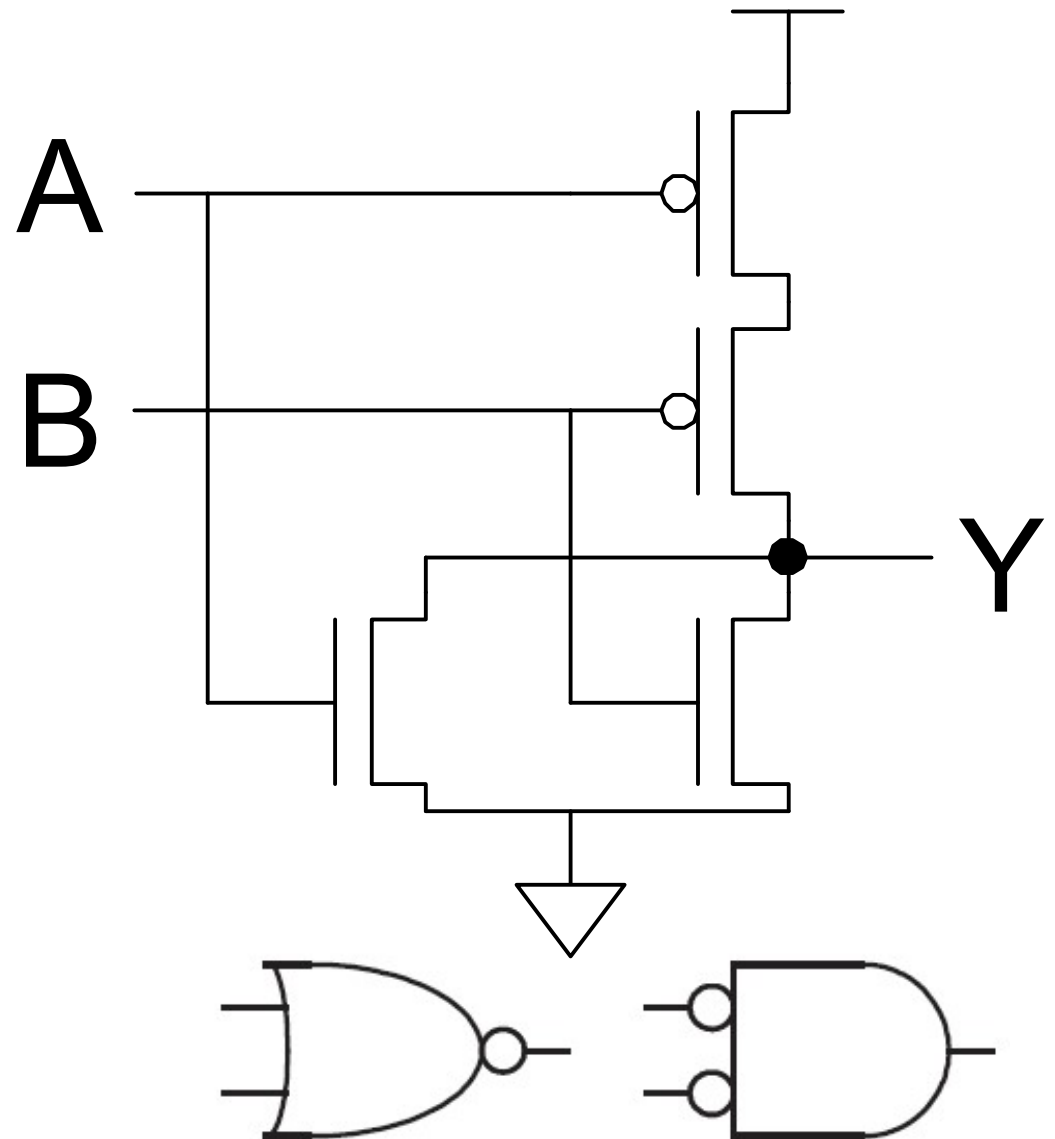



QUIZ

Sketch a k-input CMOS NOR gate?

MOS LOGIC CIRCUITS

- **Tristate Buffer:**
 - *Tristate buffer produces Z when not enabled*


EN	A	Y
0	0	
0	1	
1	0	
1	1	

  

MOS LOGIC CIRCUITS

- **Tristate Buffer:**

 
- Transmission Gate acts as tristate buffer
- Advantage: Only two transistors
- Drawback: **Nonstoring** - output level is not driven from V_{DD} or GND
 - Noise on A is passed on to Y



MOS LOGIC CIRCUITS

- **Tristate Inverter:**

 
- *Application:* To allow multiple units to drive a common bus
- *Drawback:* Delay between different EN signals switching can cause contention



MOS LOGIC CIRCUITS

- **Multiplexer:**
 - 2:1 multiplexer chooses between two inputs



S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 

MOS LOGIC CIRCUITS


- **Multiplexer:**

  - $Y = SD_1 + \bar{S}D_0$ (too many transistors)
- How many transistors are needed?




MOS LOGIC CIRCUITS

 - **Multiplexer:**
 - Non-storing MUX uses two transmission gates
 - Only 4 transistors




MOS LOGIC CIRCUITS

 - **Inverting Multiplexer:**
 - Use a pair of tristate inverters




(b)

 


(c)

MOS LOGIC CIRCUITS

 - **Sequential Circuits:** have memory, their outputs depend on both current and previous inputs.
 - Examples: latches and flip-flops




Control of an alarm system

 

A simple memory element



MOS LOGIC CIRCUITS

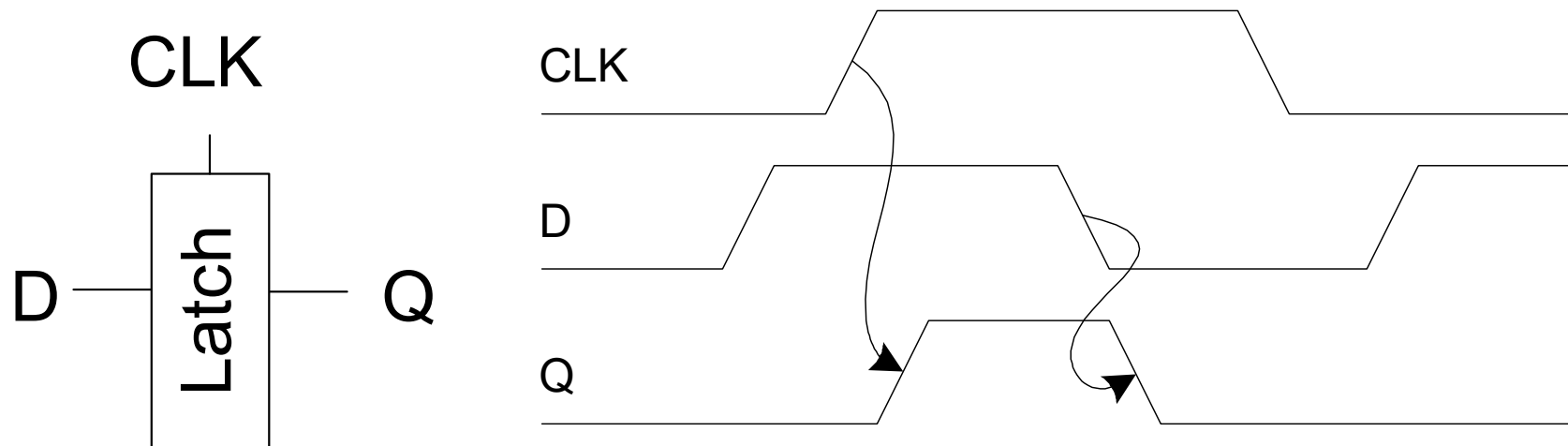- **D Latch:**
 - When $CLK = 1$, latch is *transparent*
 - D flows through to Q like a buffer
 - When $CLK = 0$, the latch is *opaque*
 - Q holds its old value independent of D
 - a.k.a. *transparent latch* or *level-sensitive latch*






MOS LOGIC CIRCUITS

  - **D Latch:**
 - Use a MUX and two inverters



MOS LOGIC CIRCUITS


- **D Latch:**
 - Operation

   

MOS LOGIC CIRCUITS


- **Flip-Flops:**

 - When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



MOS LOGIC CIRCUITS



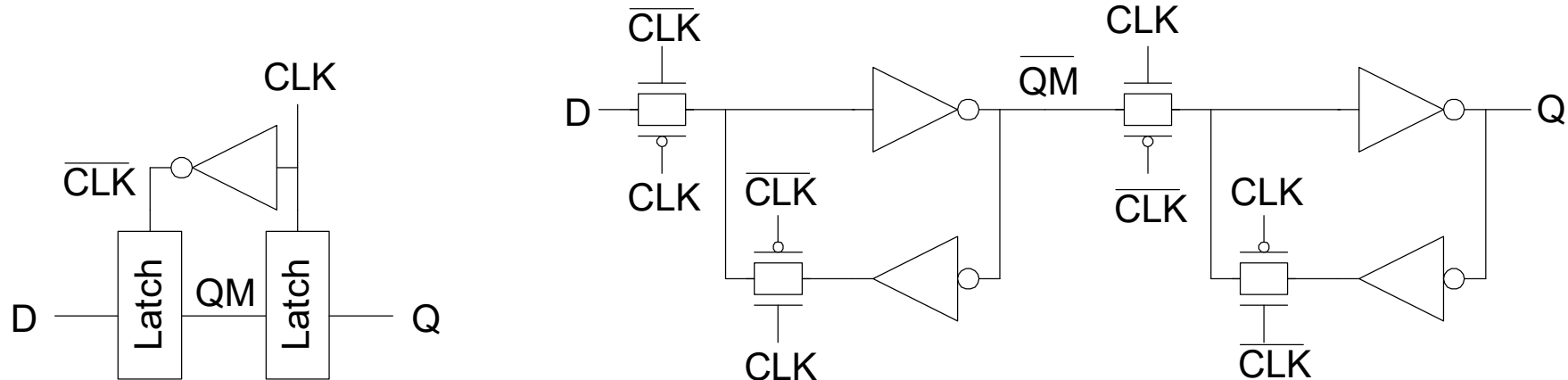
- **Flip-Flops:**
 - Combining between one negative-sensitive D latch and one positive-sensitive D latch



MOS LOGIC CIRCUITS

- **Flip-Flops:**

 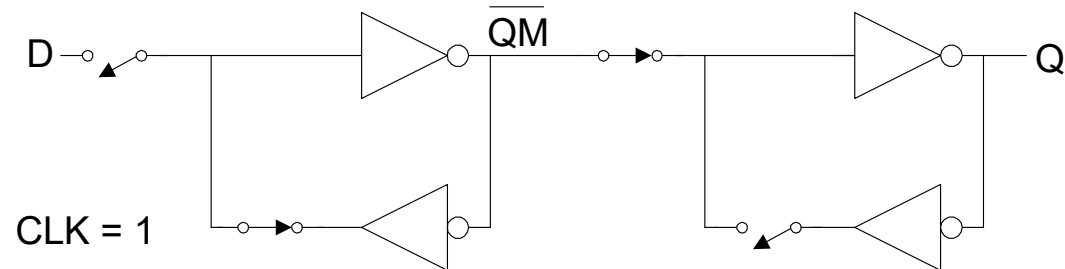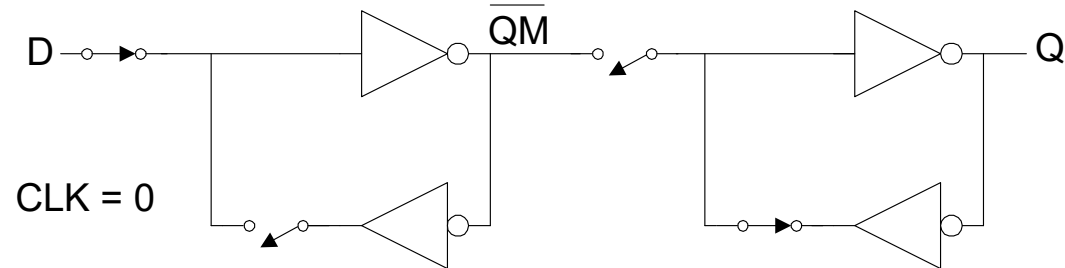- Operation: triggered by positive-edge clock



Outline


- MOS Transistors
- NMOS vs. CMOS Logic Circuits
- MOS Logic Circuits
- • **CMOS Fabrication and Layout**
- Summary

CMOS Fabrication

- CMOS transistors are fabricated on silicon wafer with set of masks
- *Photolithography* process similar to printing press
- On each step, different materials are deposited or etched
- Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process


CMOS Fabrication

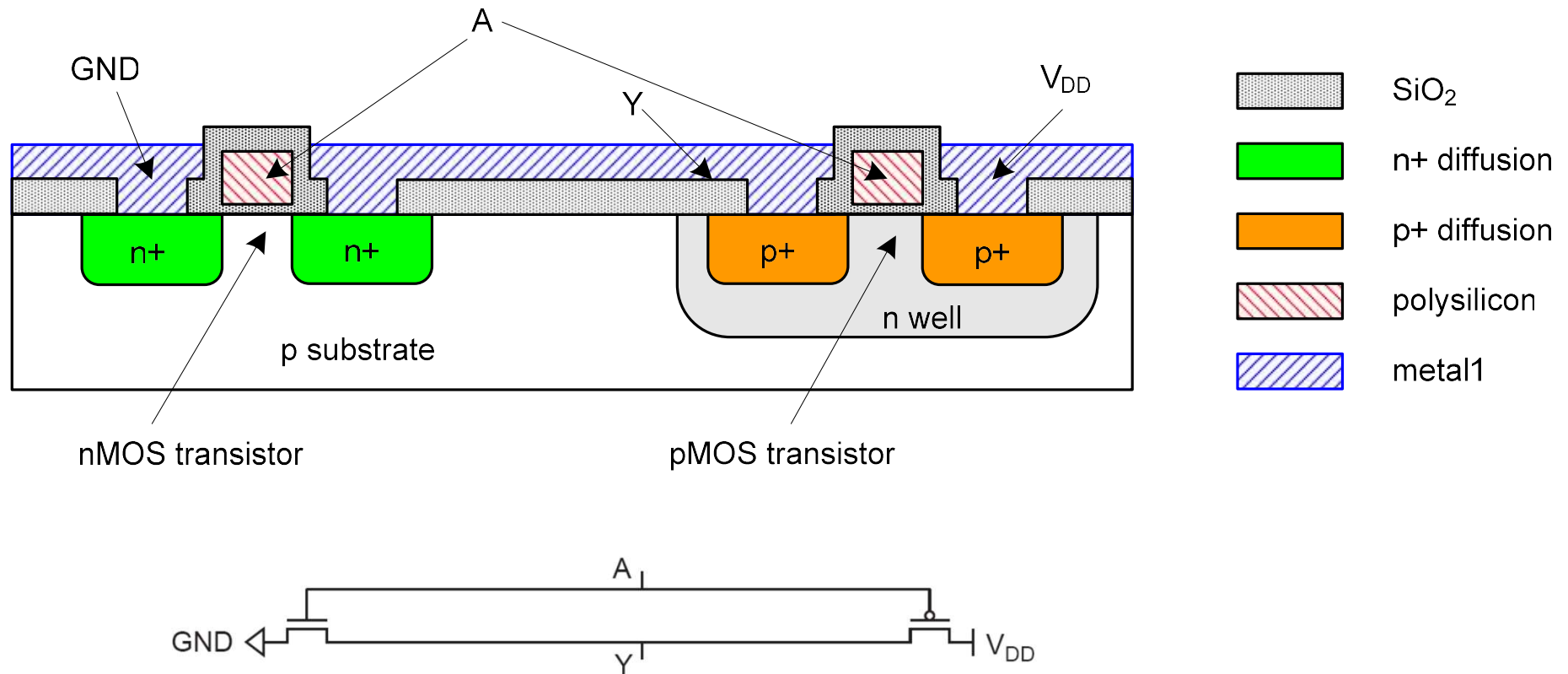- **Cross-section and corresponding schematic of an inverter**
 - **p-type substrate**
 - An **n-well** is diffused (khuếch tán) into the substrate to create n-type body of pMOS transistor.



CMOS Fabrication

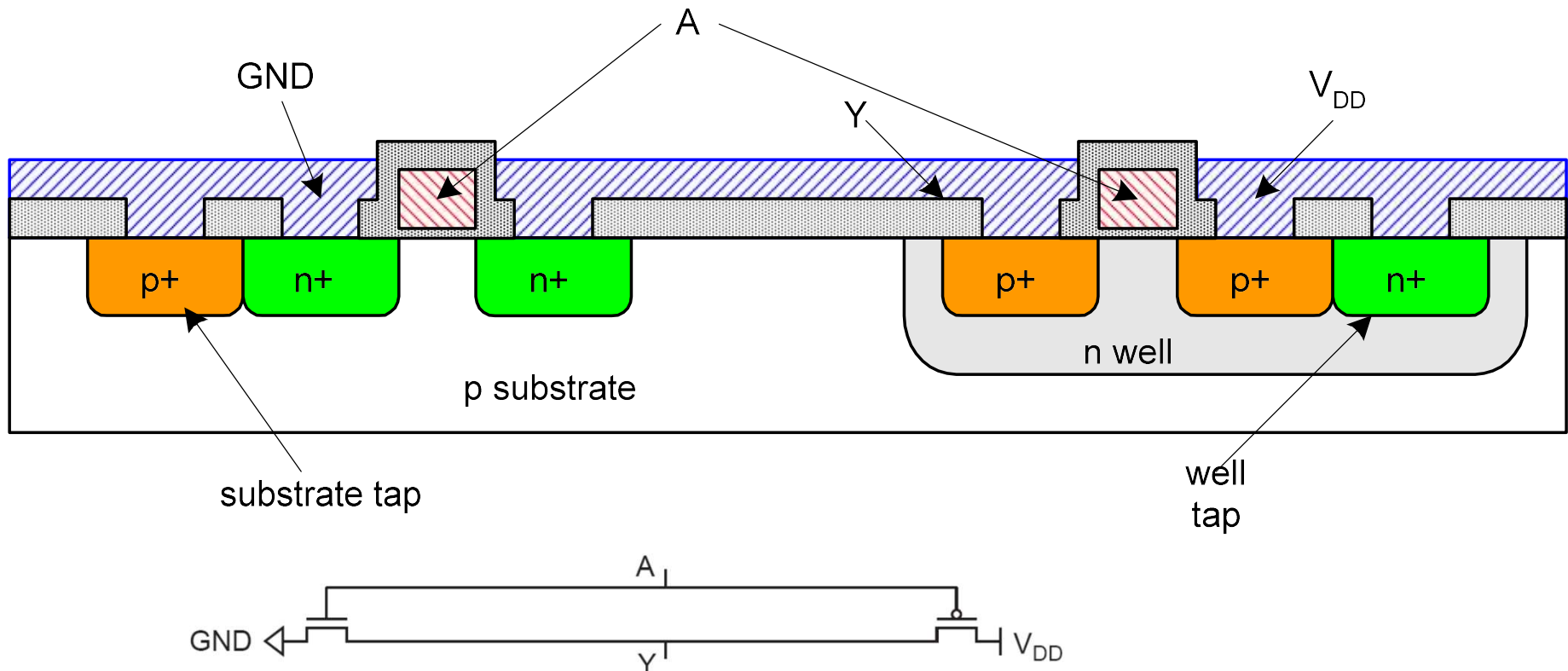- **Cross-section and corresponding schematic of an inverter**
 - Substrate must be tied to GND and n-well to VDD
 - Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
 - Use heavily doped well and substrate contacts / taps




CMOS Fabrication

- The fabrication sequence consists of a series of steps in which layers of the chip are defined through a process called *photolithography* (*quang khắc*):
 - Etching (Ăn mòn)
 - Doping (pha tạp): Diffusion (khuyếch tán) or *Ion Implantation* (Cấy ion)
 - Oxidation
 - Deposition techniques (*phương pháp tạo màng mỏng*): chemical vapor deposition (*Kết tủa hóa trong pha hơi*), ...

CMOS Fabrication

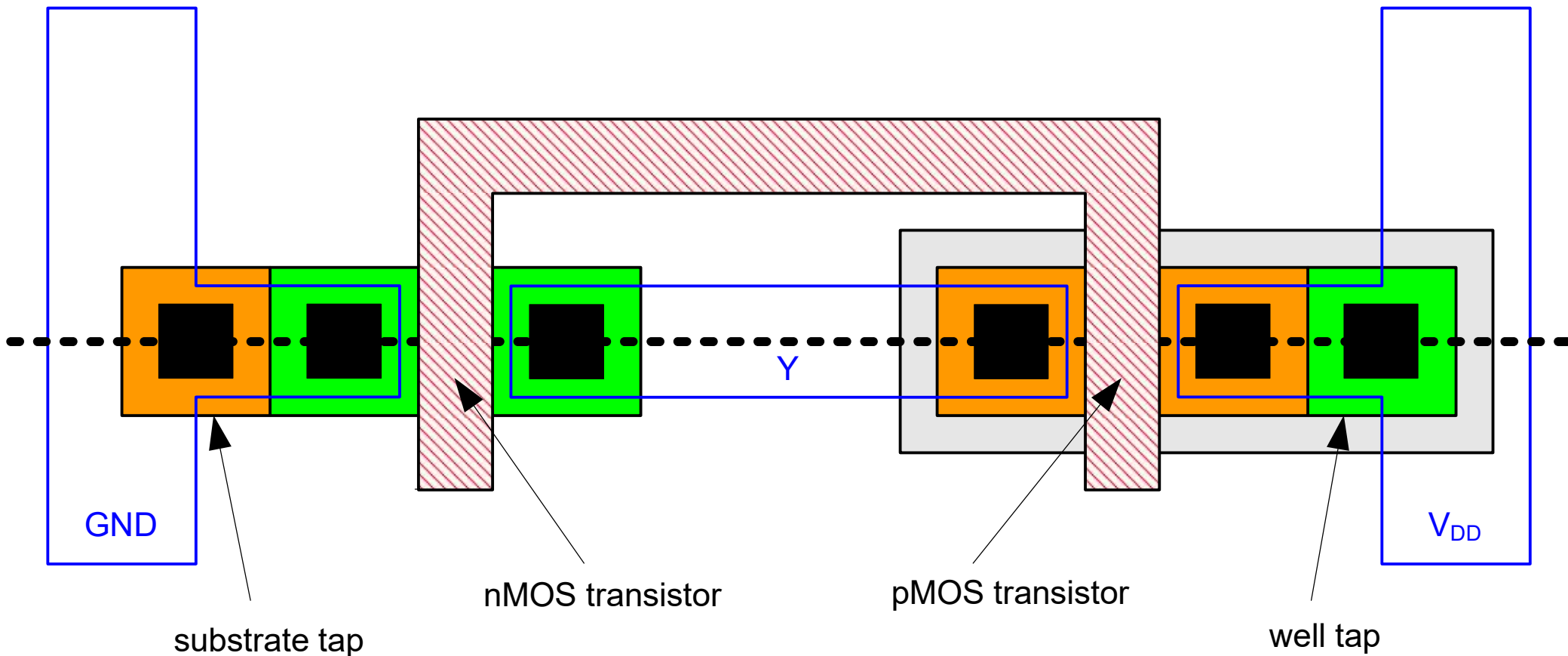
- **Masks** specify where the components (i.e. Transistors and wires) will be manufactured on the chip.



CMOS Fabrication

- The inverter could be defined by a **hypothetical set of six masks:**

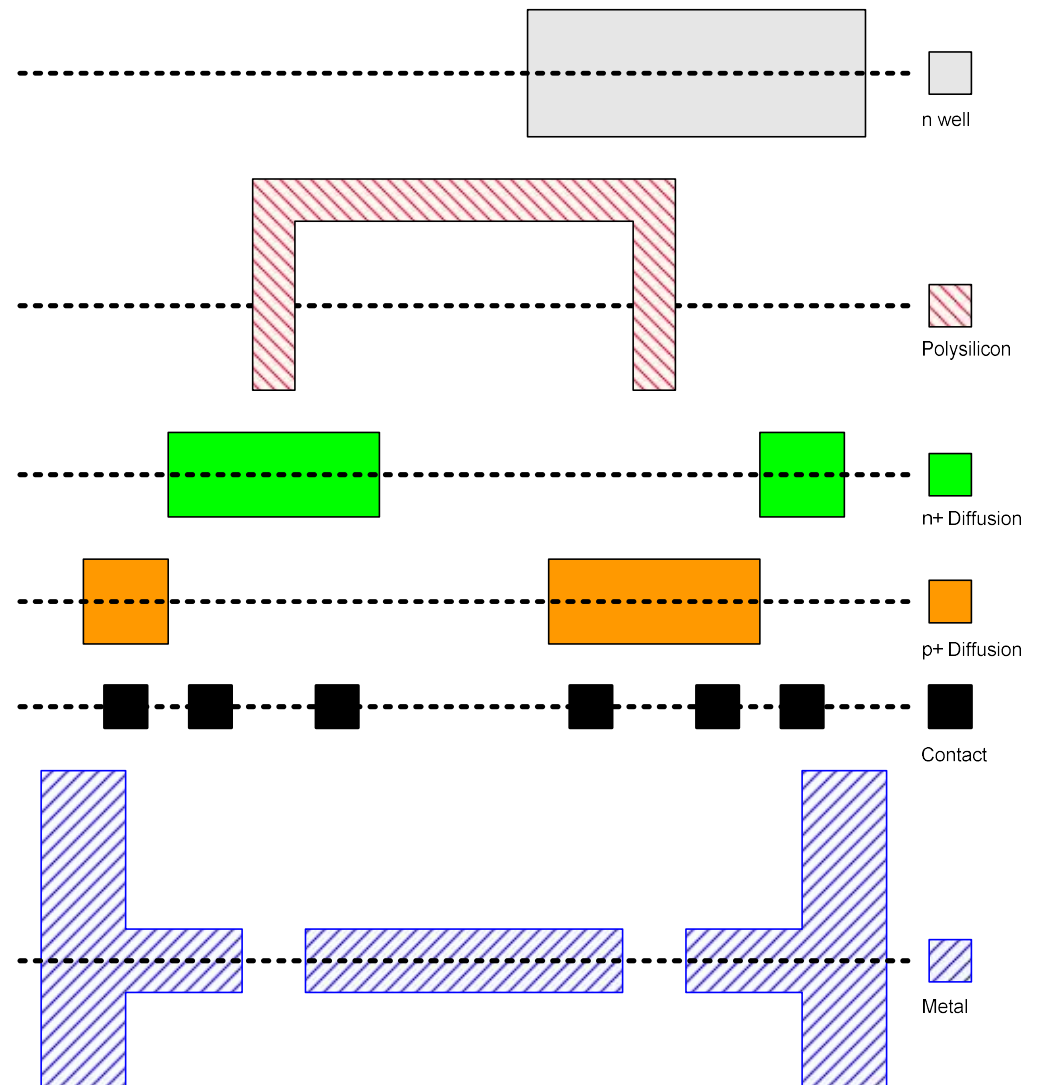- n-well,
- polysilicon,
- n+ diffusion,
- p+ diffusion,
- contacts,
- and metal.



Fabrication

- Chips are built in huge factories called fabs
- Contain clean rooms as large as football fields



Courtesy of International
Business Machines Corporation.
Unauthorized use not permitted.

Fabrication Steps


- Start with blank wafer
- Build inverter from the bottom up
- First step will be to form the n-well
 - Cover wafer with protective layer of SiO_2 (oxide)
 - Remove layer where n-well should be built
 - Implant or diffuse n dopants into exposed wafer
 - Strip off SiO_2



p substrate


Oxidation

 - Grow SiO_2 on top of Si wafer
 - 900 – 1200 C with H_2O or O_2 in oxidation furnace




Photoresist

 - Spin on photoresist
 - Photoresist is a light-sensitive organic polymer
 - Softens where exposed to light




CMOS Fabrication and Layout

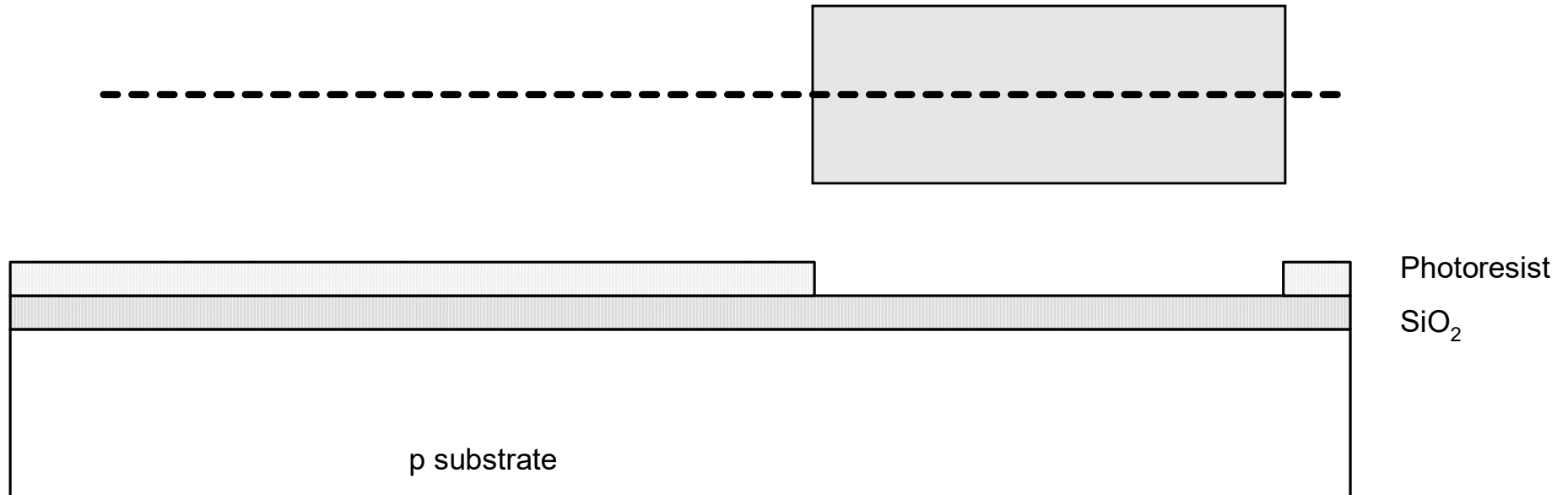- Expose photoresist through n-well mask
- Strip off exposed photoresist




Etch

 - Etch oxide with hydrofluoric (HF) acid
 - Only attacks oxide where photoresist has been exposed




Strip Photoresist

 - Strip off remaining photoresist
 - Use mixture of acids called piranha etch
- Necessary so photoresist doesn't melt in next step



n-well

 - n-well is formed with diffusion or ion implantation
- Diffusion
 - Place wafer in furnace with arsenic gas
 - Heat until As atoms diffuse into exposed Si
- Ion Implantation
 - Blast wafer with beam of As ions
 - Ions blocked by SiO_2 , only enter exposed Si




Strip Oxide

- Strip off the remaining oxide using HF acid
- Back to bare wafer with n-well
- Subsequent steps involve similar series of steps




Polysilicon

 - Deposit very thin layer of gate oxide
- Chemical Vapor Deposition (CVD) of silicon layer
 - Place wafer in furnace with Silane gas (SiH_4)
 - Forms many small crystals called polysilicon
 - Heavily doped to be good conductor




Polysilicon Patterning

 - Use same lithography process to pattern polysilicon




Self-Aligned Process

 - Use oxide and masking to expose where n+ dopants should be diffused or implanted
- N-diffusion forms nMOS source, drain, and n-well contact




N-diffusion

 - Pattern oxide and form n+ regions
- *Self-aligned process* where gate blocks diffusion
- Polysilicon is better than metal for self-aligned gates because it doesn't melt during later processing




N-diffusion cont.

 - Historically dopants were diffused
- Usually ion implantation today
- But regions are still called diffusion




N-diffusion cont.

 - Strip off oxide to complete patterning step




P-Diffusion

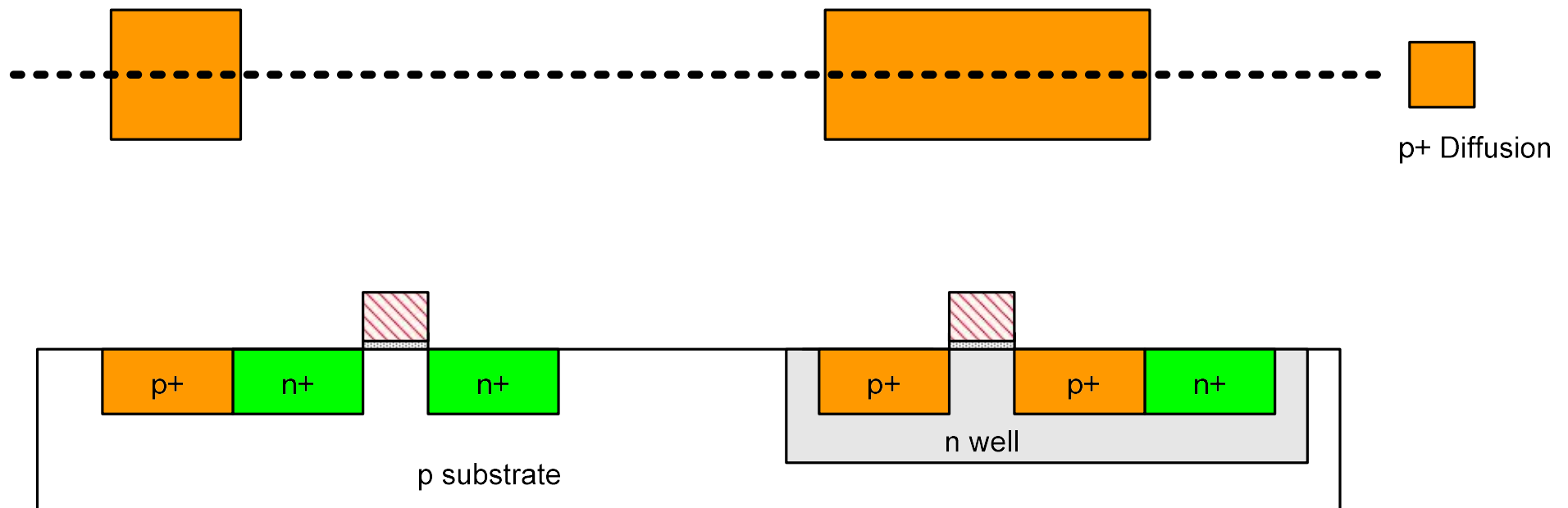- Similar set of steps form p+ diffusion regions for pMOS source and drain and substrate contact




Contacts

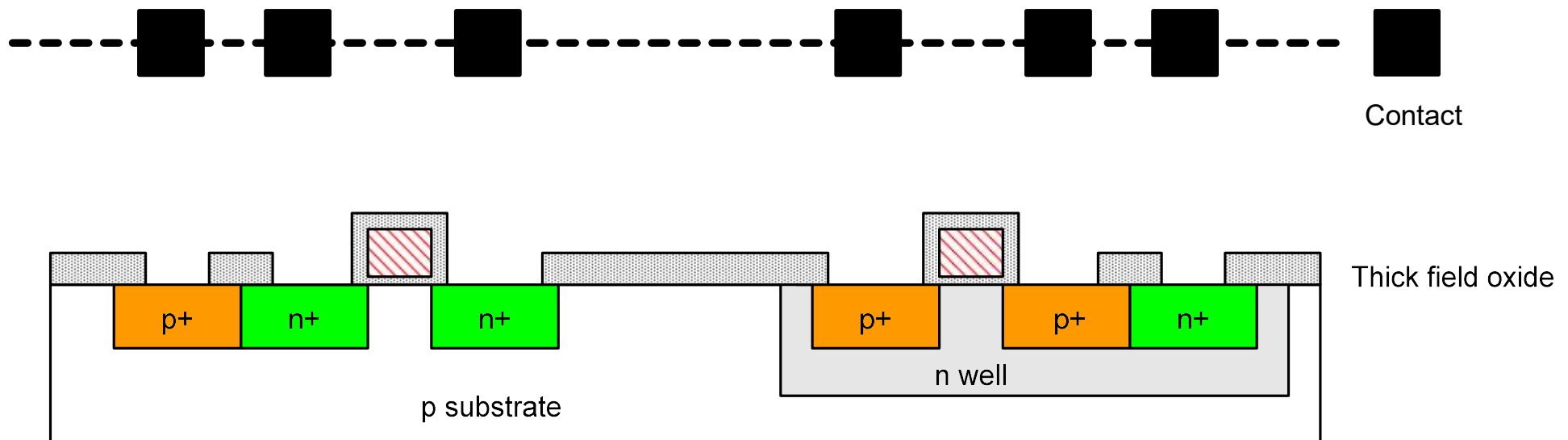- Now we need to wire together the devices
- Cover chip with thick field oxide
- Etch oxide where contact cuts are needed




Metalization

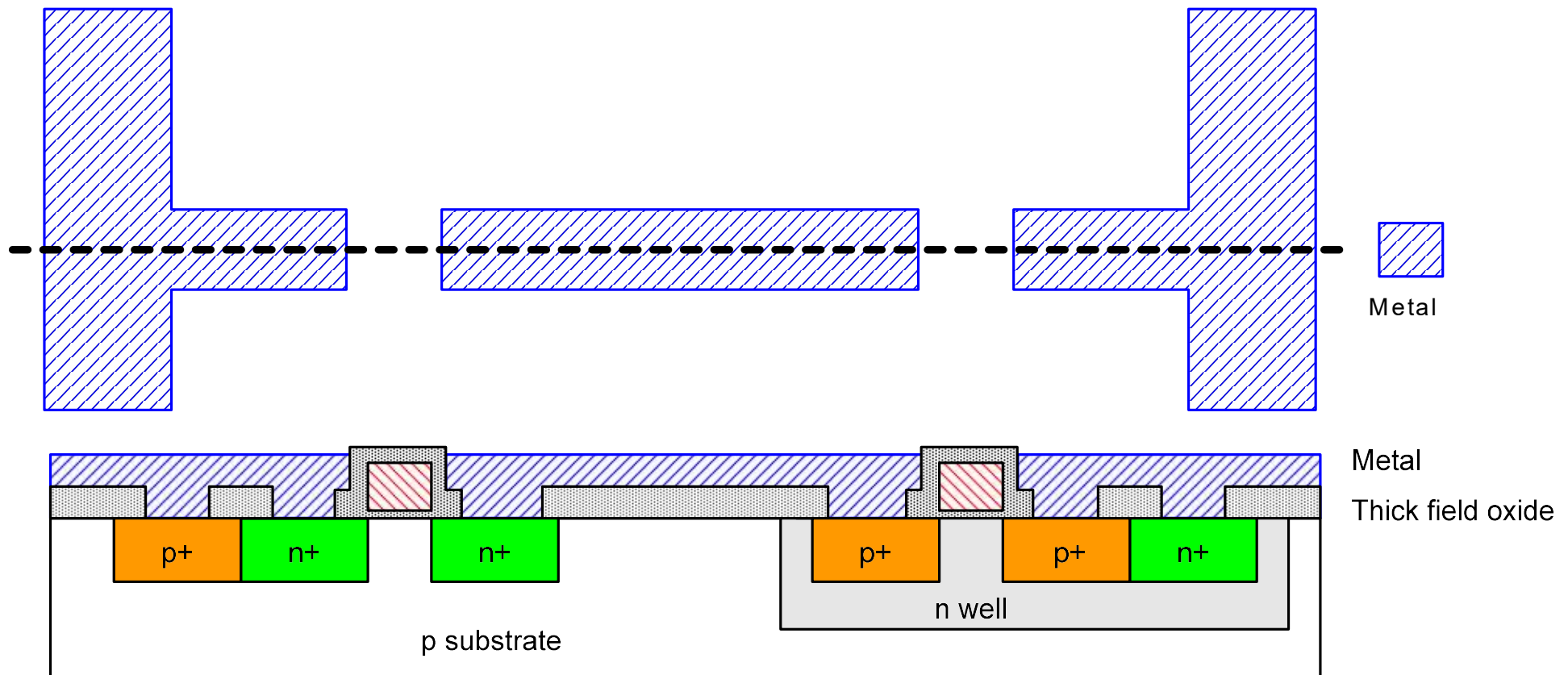- Sputter aluminum over whole wafer
- Pattern to remove excess metal, leaving wires





Fabrication and Package

 - Tapeout final layout
- Fabrication
 - 6, 8, 12" wafers
 - Cut into individual dice
- A single dust particle or wafer defect kills a die



Fabrication and Package

  - **Packaging**
 - Bond gold wires from die I/O pads to package
- **Test that chip operates**
 - Design errors
 - Manufacturing errors



Outline

- MOS Transistors
- NMOS vs. CMOS Logic Circuits
- MOS Logic Circuits
- CMOS Fabrication and Layout
- • **Summary**

Summary

- Concepts and applications of MOS Transistors in digital designs
 - MOS transistors are stacks of gate, oxide, silicon
 - Act as electrically controlled switches
 - Build logic gates out of switches
- MOS Logic Circuits
 - NMOS Vs. CMOS
 - Basic CMOS logic Circuits
- CMOS Layout and Fabrication
 - Draw masks to specify layout of transistors