



**VietNam National University
University of Engineering and Technology**

THIẾT KẾ MẠCH TÍCH HỢP SỐ (DIGITAL IC DESIGN)

TS. Nguyễn Kiêm Hùng

Email: kiemhung@vnu.edu.vn

Lecture 3.2: CPU Architecture and Design

Objectives

In this lecture you will be introduced to:

- **General-purpose Processor Architecture**
- **Techniques for designing General-purpose processor at RTL**

Outline


- **Processor Architecture**
- Programmer's Model
- RT-level custom general-purpose processor design

Introduction

- General-Purpose Processor
 - Processor designed for a variety of computation tasks
 - Low unit cost, because manufacturer spreads NRE (Non-recurring engineering) over large numbers of units
 - Two billions ARM-based microcontrollers was sold *in 2008*
 - Carefully designed since higher NRE is acceptable
 - Can yield good performance, size and power
 - Low NRE cost, short time-to-market/prototype, high flexibility
 - User just writes software; no processor design
 - a.k.a. “microprocessor” – “micro” used when they were implemented on one or a few chips rather than entire rooms


Basic Architecture

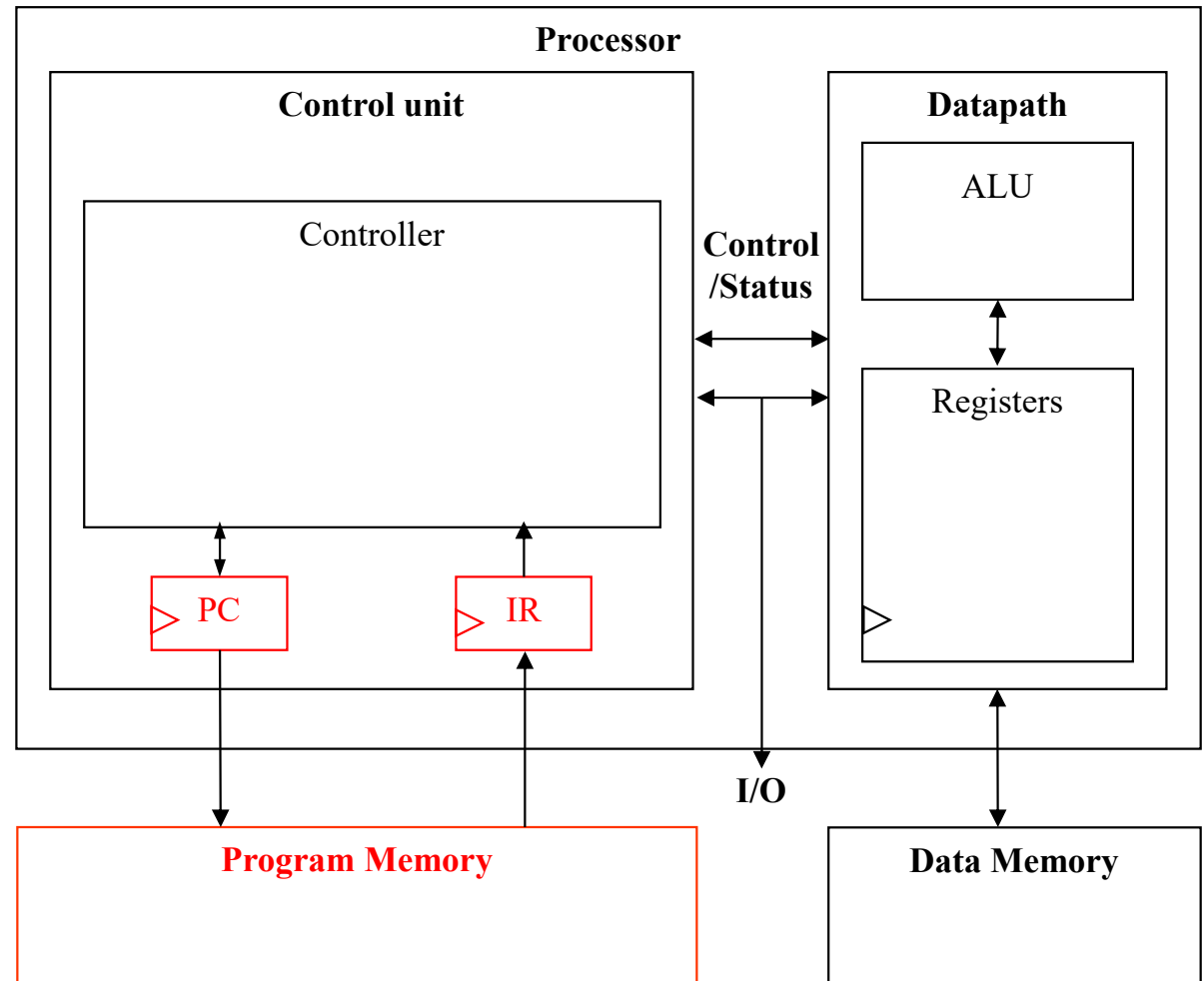- Control unit and datapath
 - Note similarity to single-purpose processor
- Key differences
 - Datapath is general
 - Control unit doesn't store the algorithm – the algorithm is “programmed” into the memory
 - CPU registers: program counter (PC), instruction register (IR), general-purpose registers, etc.




Datapath

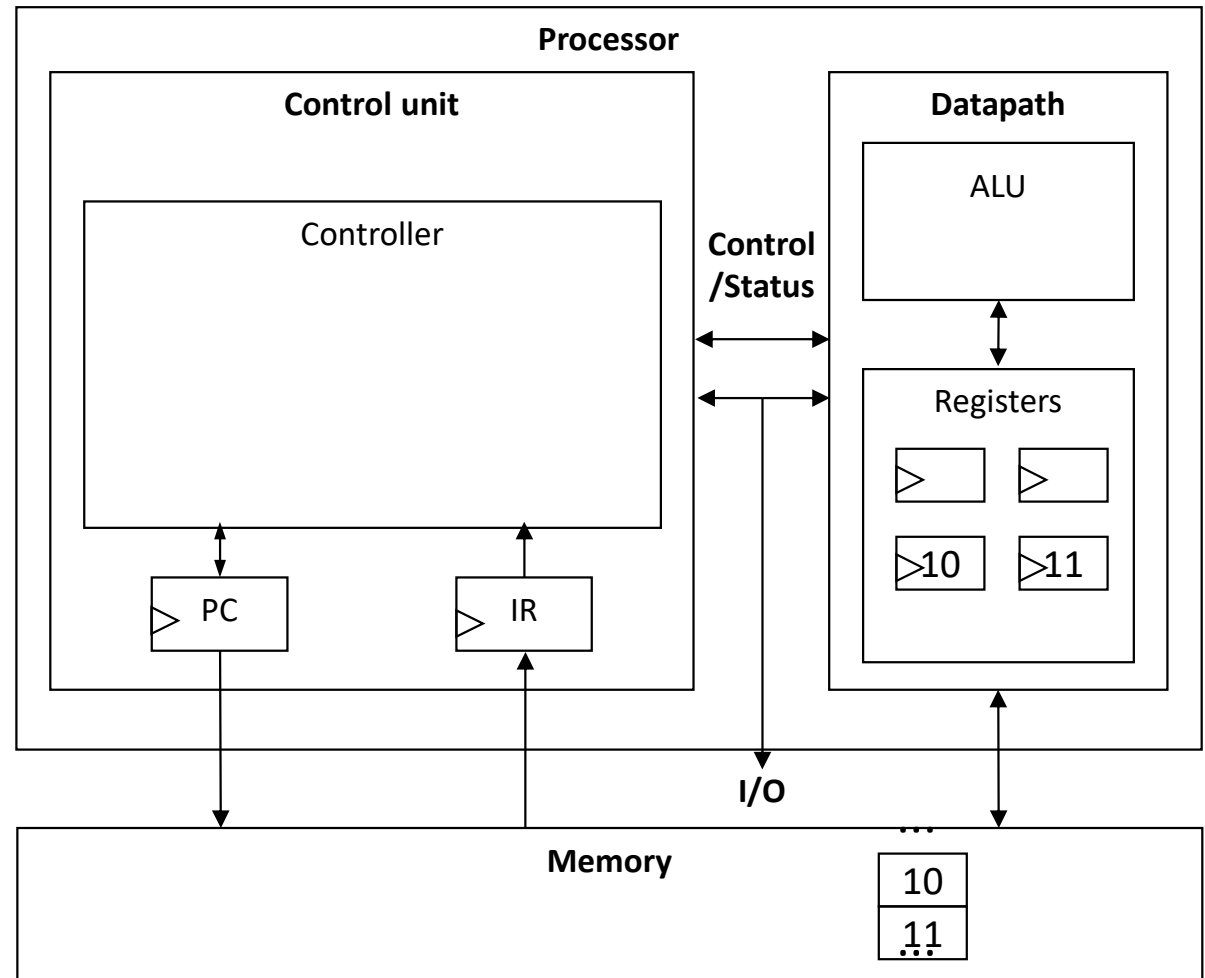- **Function**
 - transforming data and storing temporary data
- **Structure:**
 - ALU (arithmetic-logic unit): transforming data through operations
 - Registers: storing temporary data
 - internal data bus




Datapath Operations

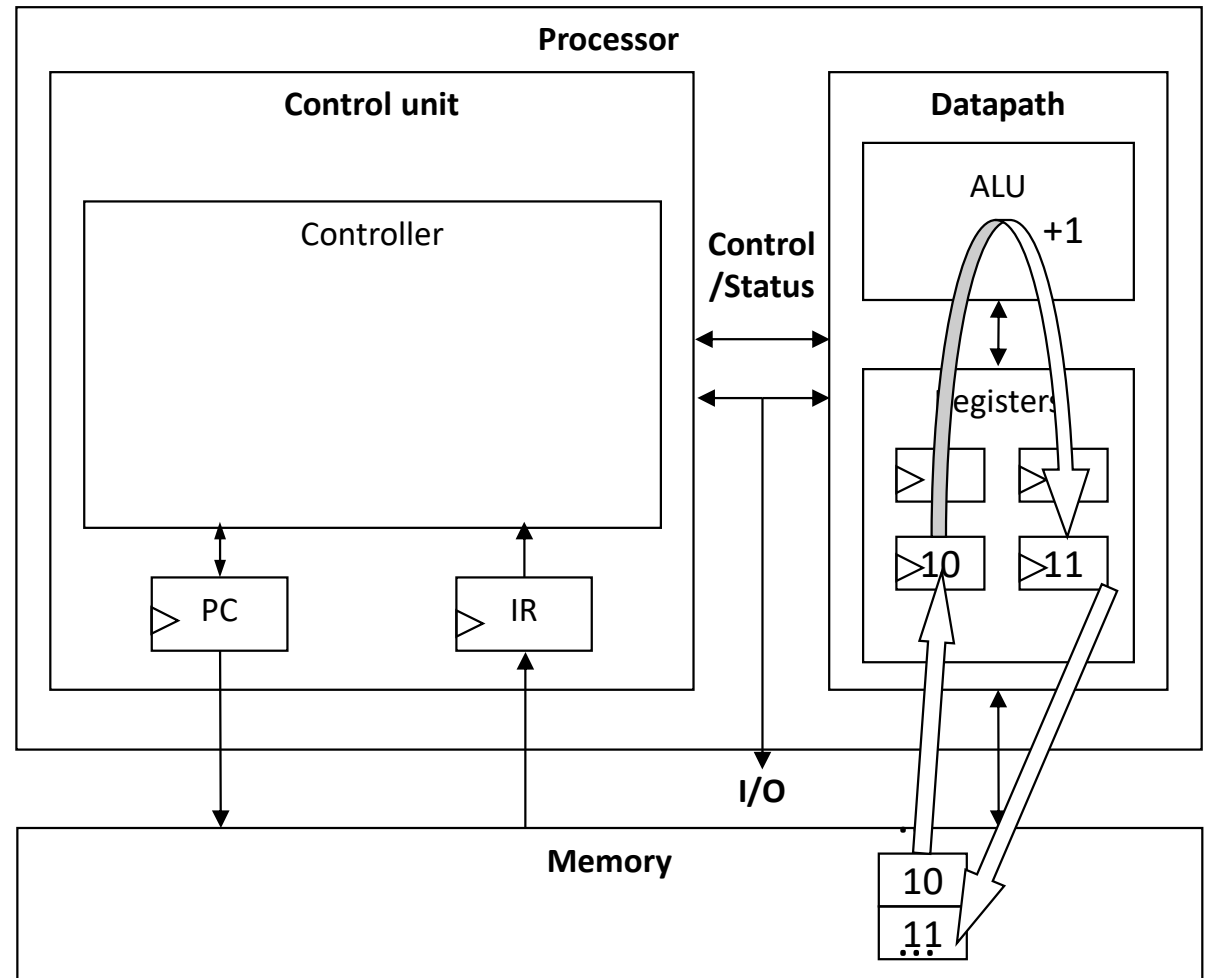- Load
 - Read memory location into register
- ALU operation
 - Input certain registers through ALU, store back in register
- Store
 - Write register to memory location



Control Unit


- **Control unit:** configures the datapath operations
 - Sequence of desired operations (“instructions”) stored in memory – “**Program**”
- **Instruction cycle** – broken into several sub-operations, each one clock cycle, e.g.:
 - *Fetch*: Get next instruction into IR
 - *Decode*: Determine what the instruction means
 - *Fetch operands*: Move data from memory to datapath register
 - *Execute*: Move data through the ALU
 - *Store results*: Write data from register to memory

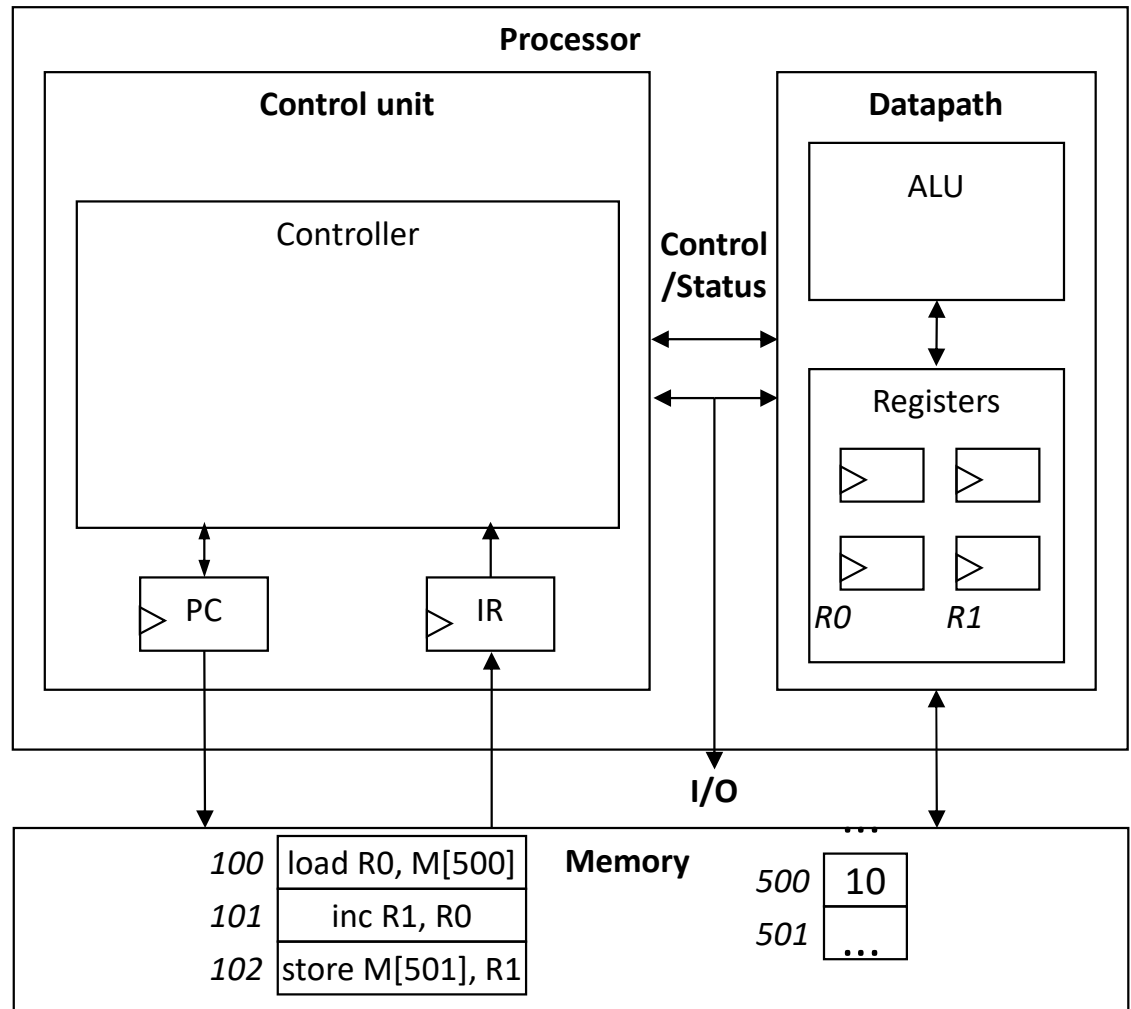

Control Unit Sub-Operations


- **Fetch**

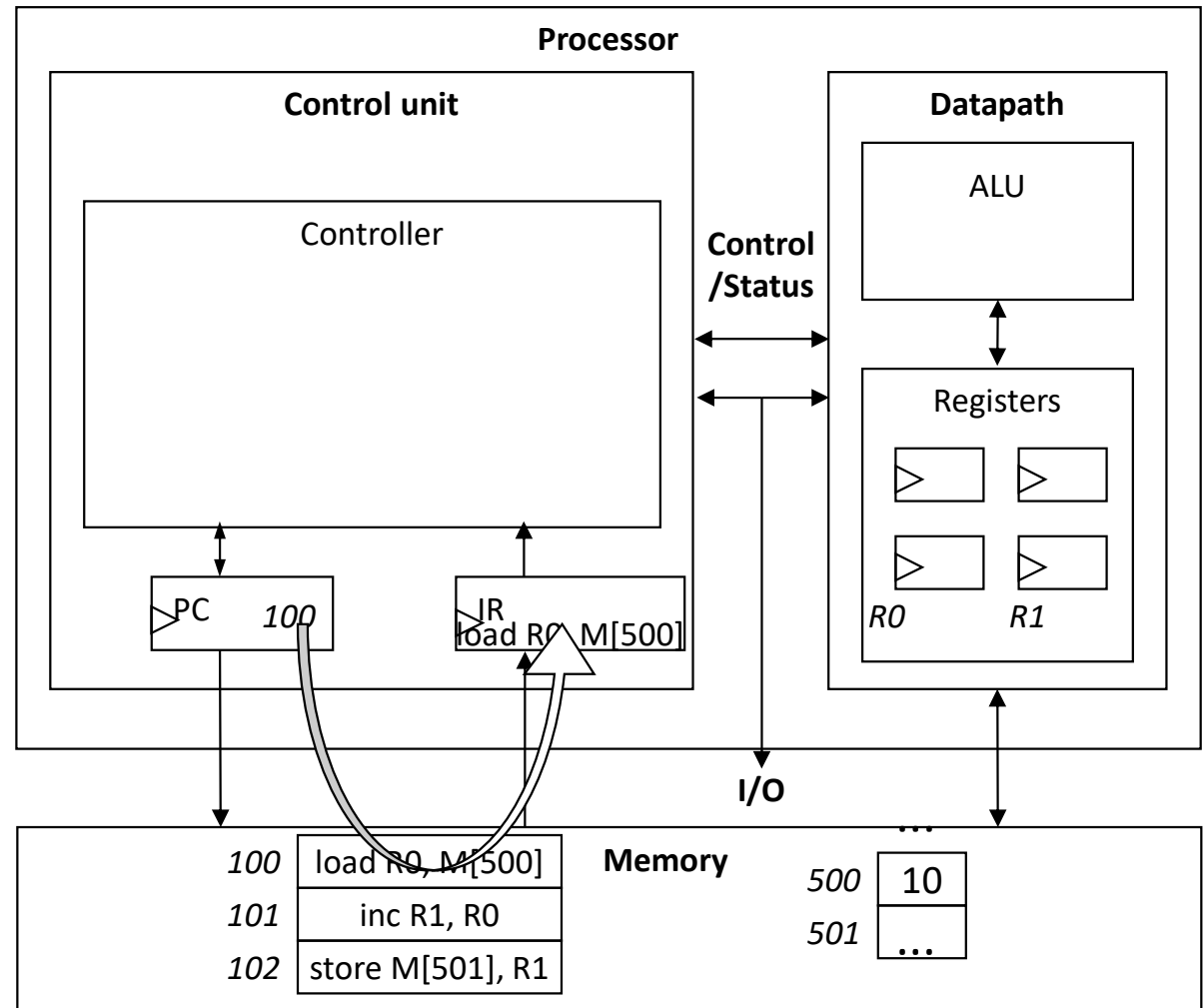- Get next instruction into IR
- PC: program counter, always points to next instruction
- IR: Instructions Register, holds the fetched instruction




Control Unit Sub-Operations

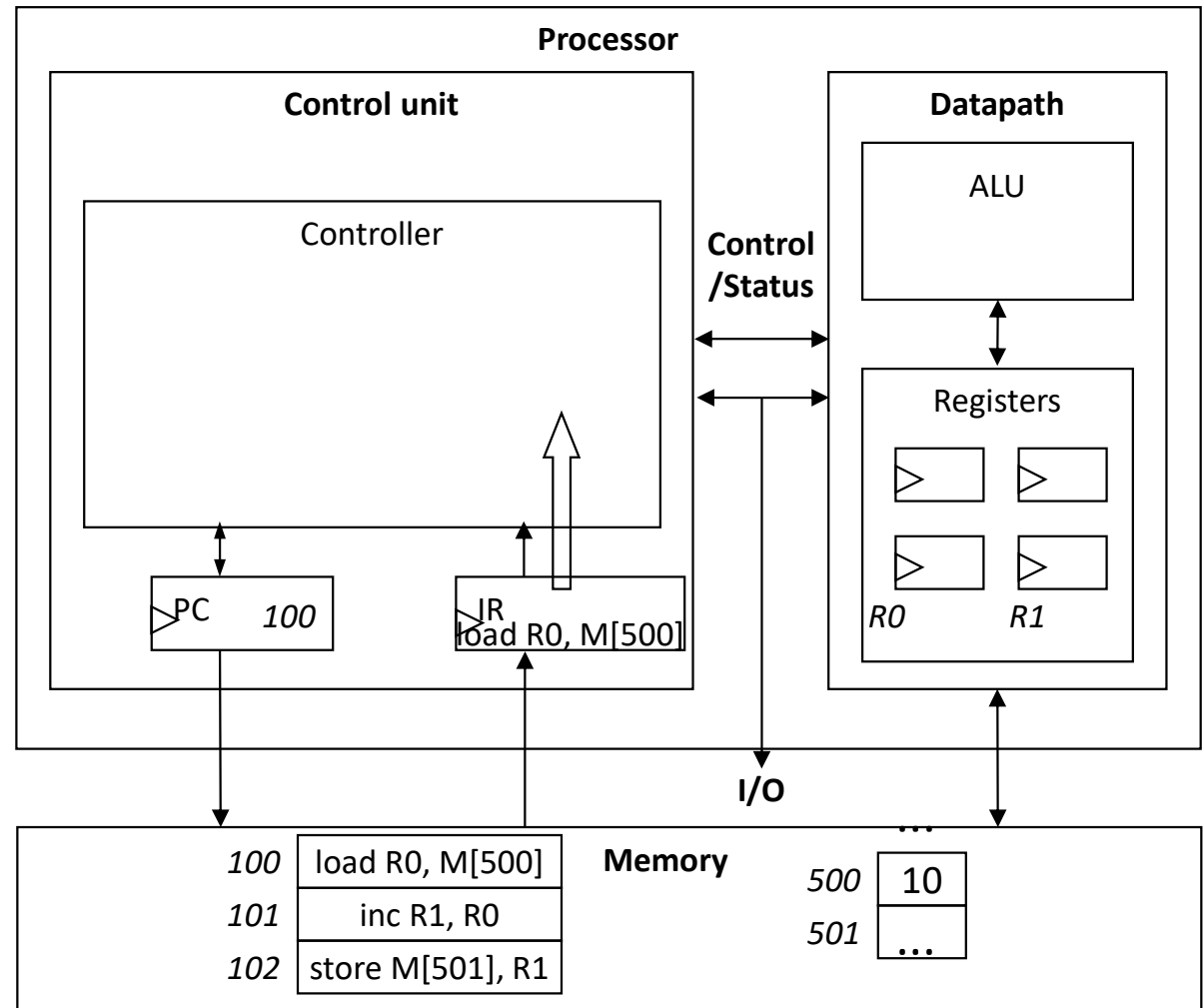- **Decode**
 - Determine what the instruction means




Control Unit Sub-Operations

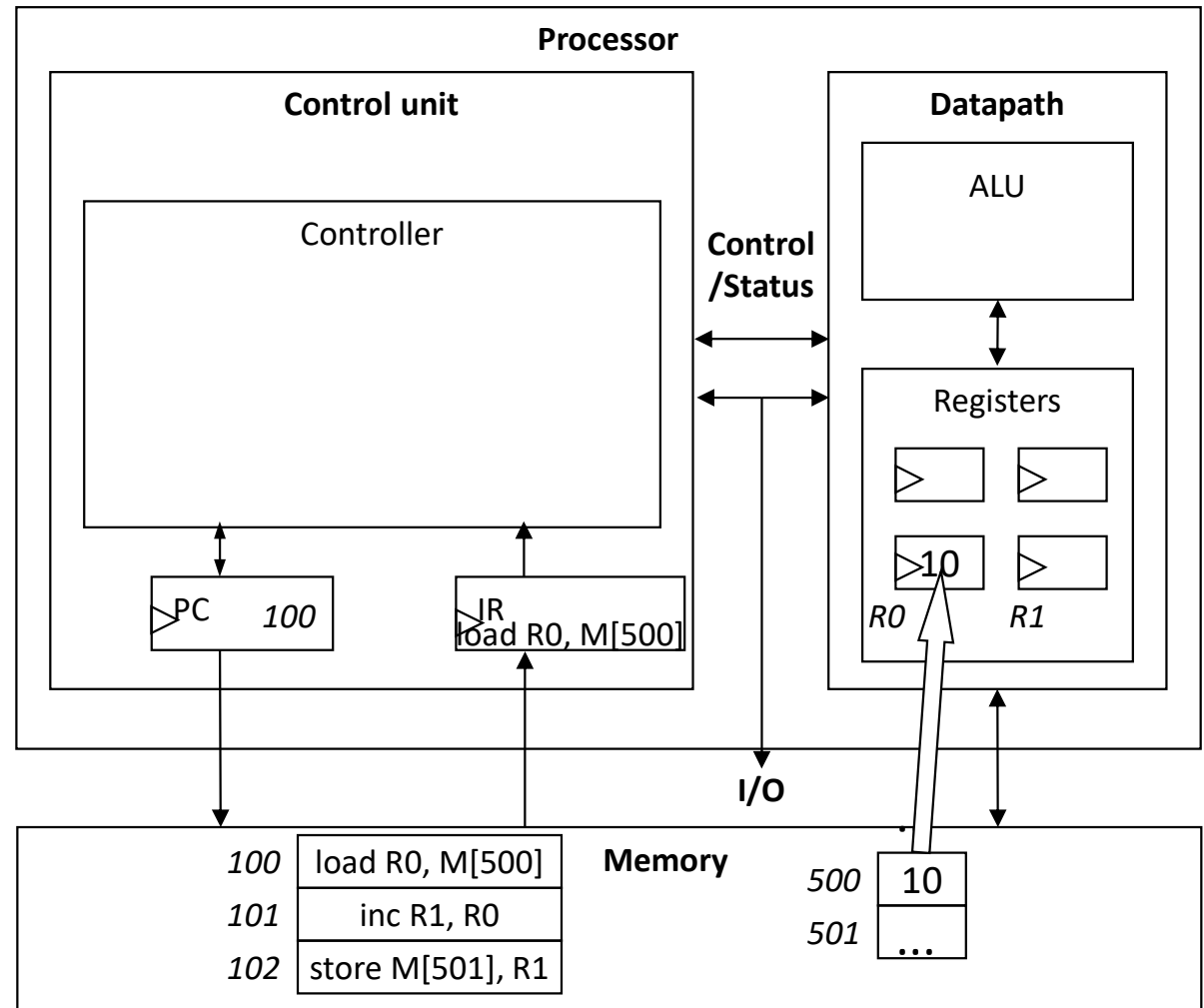- **Fetch operands**
 - Move data from memory to datapath register




Control Unit Sub-Operations

 - **Execute**
 - Move data through the ALU
 - This particular instruction does nothing during this sub-operation




Control Unit Sub-Operations



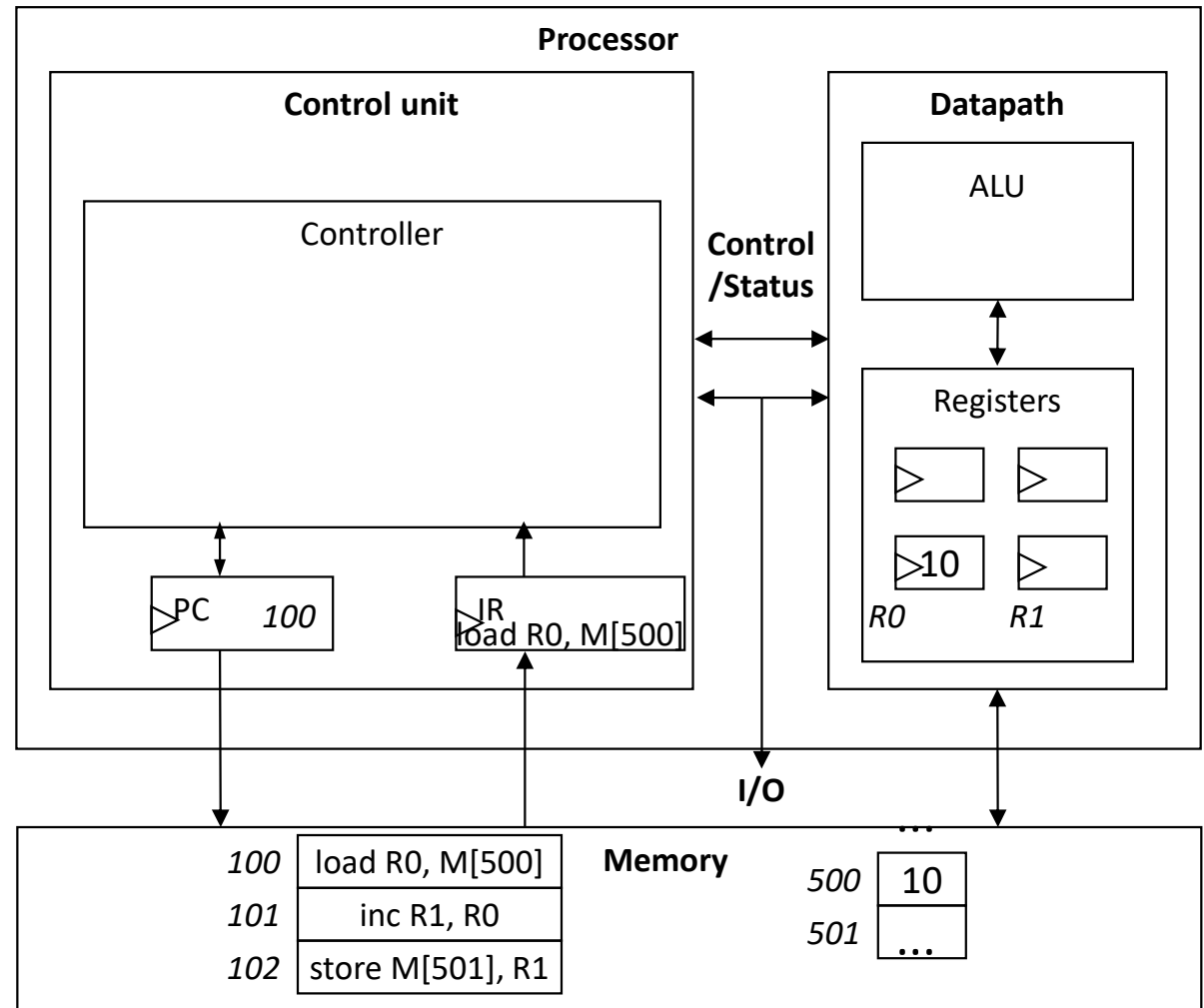
- **Store results**
 - Write data from register to memory
 - This particular instruction does nothing during this sub-operation





Instruction Cycles

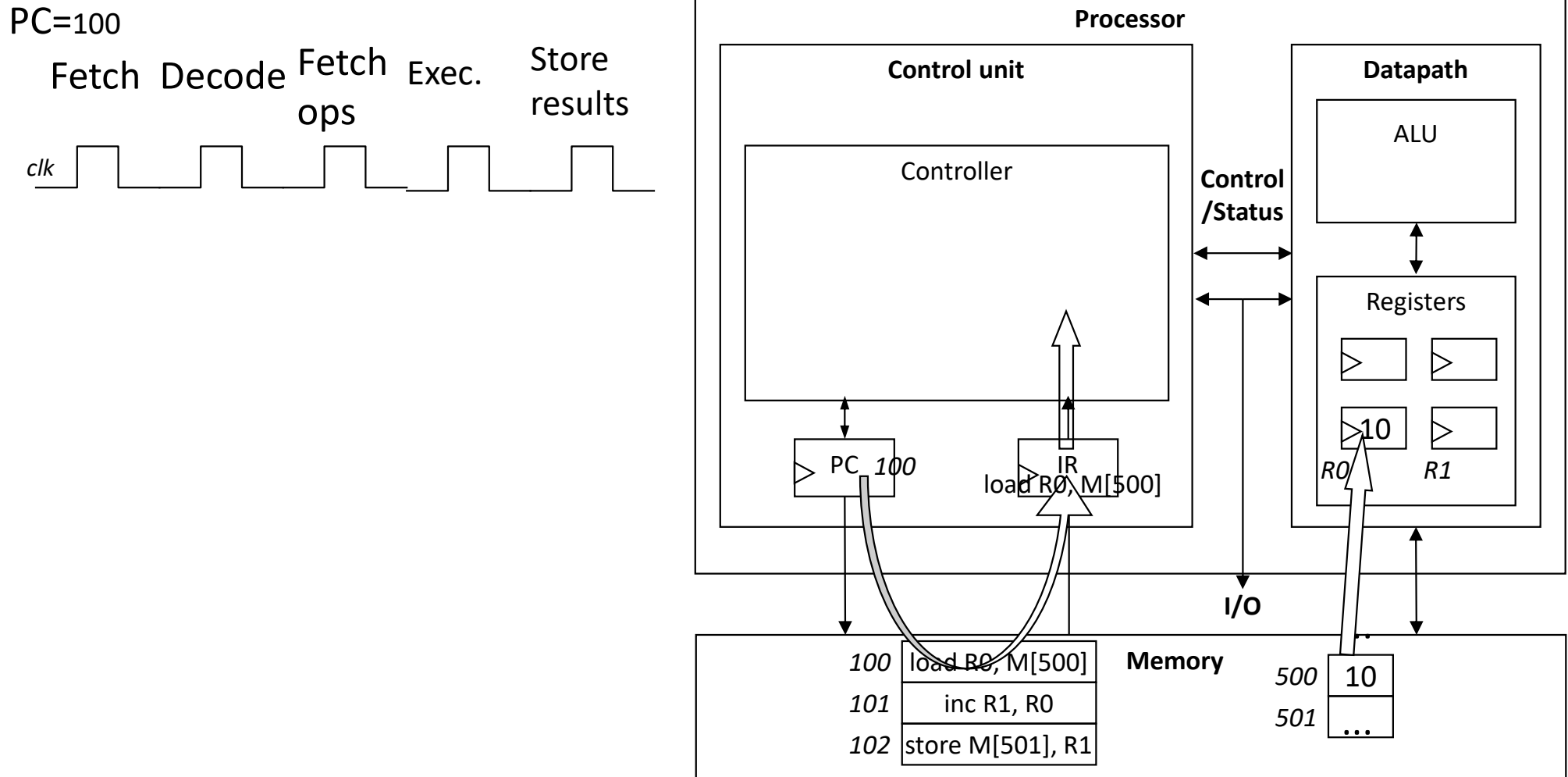

Instruction Cycles

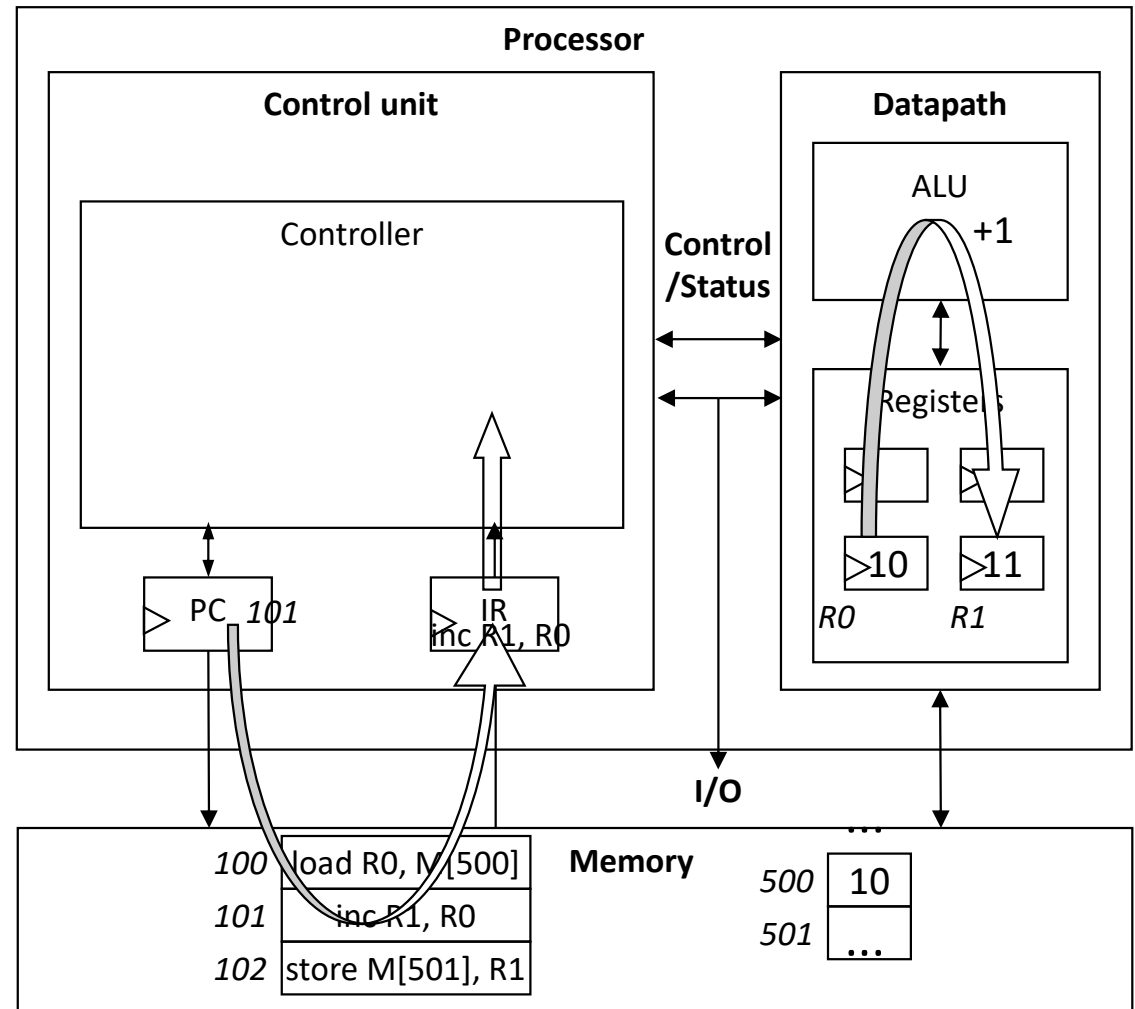  

Instruction Cycles

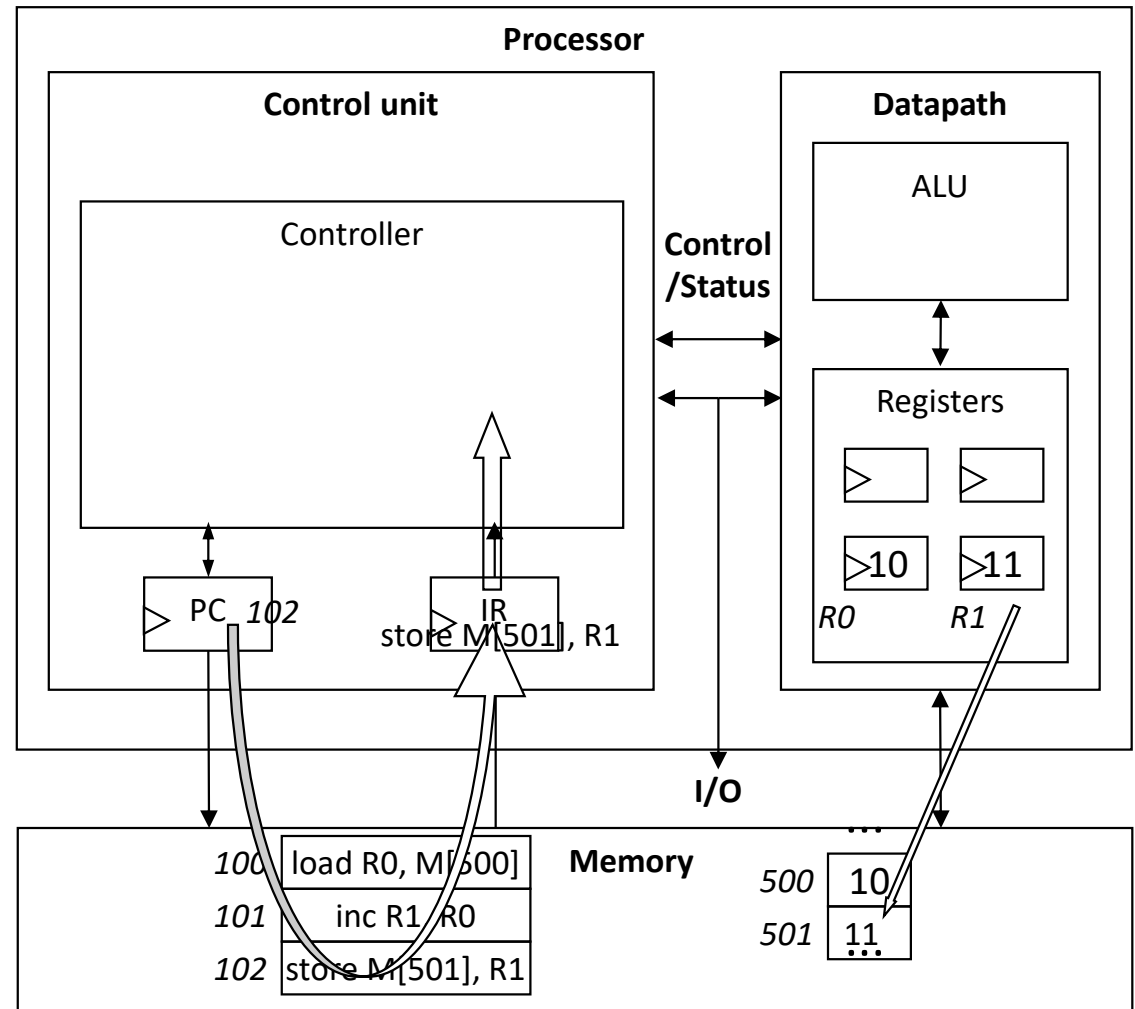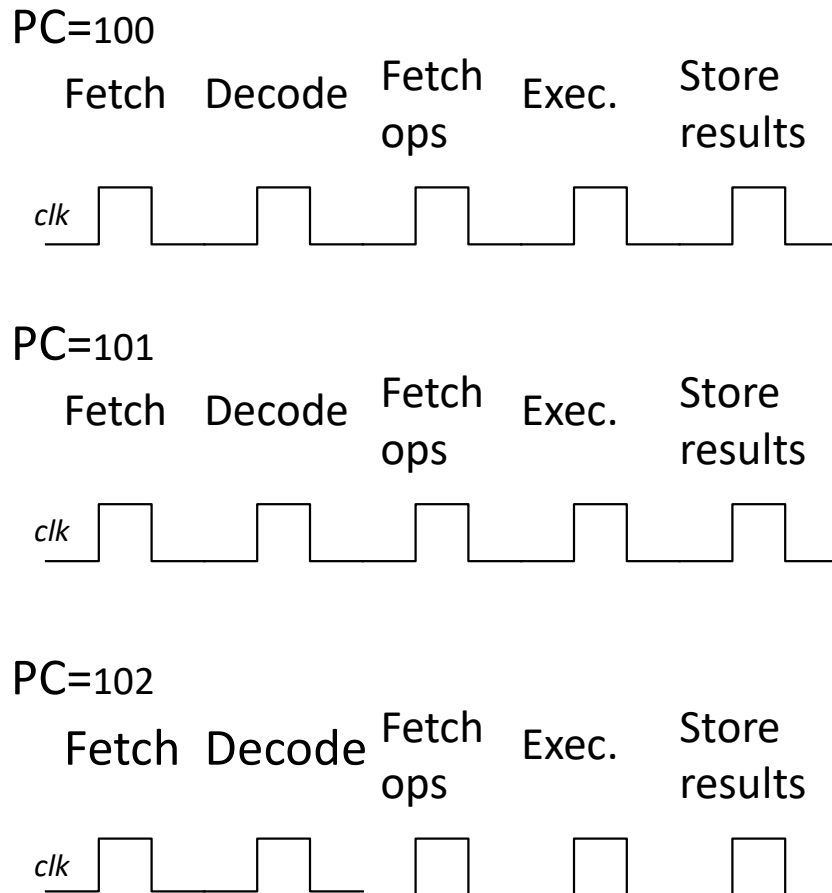

Outline


- Processor Architecture
- **Programmer's View**
- RT-level custom general-purpose processor design

Programmer's View (1)

- Programmer doesn't need detailed understanding of processor's architecture
 - Instead, needs to know what instructions can be executed
- Two levels of instructions:
 - Assembly level
 - Structured languages (C, C++, Java, etc.)
- Most development today done using structured languages
 - But, some assembly level programming may still be necessary
 - Drivers: portion of program that communicates with, and/or drives, peripheral devices
 - Often have detailed timing considerations, extensive bit manipulation
 - Assembly level may be best for these

Example: parallel port driver

LPT Connection Pin	I/O Direction	Register Address
1	Output	0 th bit of register #2
2-9	Output	0 th ~7 th bit of register #0
10,11,12,13,15	Input	6,7,5,4,3 th bit of register #1
14,16,17	Output	1,2,3 th bit of register #2

 

- Using assembly language programming we can configure a PC parallel port to perform digital I/O
 - write and read to three special registers to accomplish this table provides list of parallel port connector pins and corresponding register location
 - Example : parallel port monitors the input switch and turns the LED on/off accordingly

Parallel Port Example

```
; This program consists of a sub-routine that reads
; the state of the input pin, determining the on/off state
; of our switch and asserts the output pin, turning the LED
; on/off accordingly
.386
```

```
CheckPort    proc
    push     ax                ; save the content
    push     dx                ; save the content
    mov     dx, 3BCh + 1      ; base + 1 for register #1
    in      al, dx            ; read register #1
    and     al, 10h           ; mask out all but bit # 4
    cmp     al, 0             ; is it 0?
    jne     SwitchOn          ; if not, we need to turn the LED on


SwitchOff:
    mov     dx, 3BCh + 0      ; base + 0 for register #0
    in      al, dx            ; read the current state of the port
    and     al, fEh           ; clear first bit (masking)
    out     dx, al            ; write it out to the port
    jmp     Done              ; we are done

SwitchOn:
    mov     dx, 3BCh + 0      ; base + 0 for register #0
    in      al, dx            ; read the current state of the port
    or      al, 01h           ; set first bit (masking)
    out     dx, al            ; write it out to the port

Done:  pop     dx                ; restore the content
    pop     ax                ; restore the content
CheckPort    endp
```

```
extern "C" CheckPort(void);    // defined in
                                // assembly

 void main(void) {
    while( 1 ) {
        CheckPort();
    }
}
```



LPT Connection Pin	I/O Direction	Register Address
1	Output	0 th bit of register #2
2-9	Output	0 th ~7 th bit of register #0
10,11,12,13,15	Input	6,7,5,4,3 th bit of register #1
14,16,17	Output	1,2,3 th bit of register #2

Assembly language

- Textual description of instructions, instead of their binary representation.
- Basic features:
 - One instruction per line.
 - Labels provide names for addresses (usually in first column).
 - Instructions often start in later columns.
 - Columns run to end of line.

ARM assembly language example

```
label1  ADR  r4,c  
        LDR  r0,[r4] ; a comment  
        ADR  r4,d  
        LDR  r1,[r4]  
        SUB  r0,r0,r1 ; comment
```

Instruction Set

- **The **Instruction Set** defines:**
 - the interface between software modules and the underlying hardware;
 - what the hardware will do under certain circumstances.
- **Characteristics:**
 - fixed versus variable length;
 - addressing modes;
 - numbers of operands;
 - types of operations supported

Instruction Set

- Why do we need to know the instruction set when designing embedded systems?
 - Most software design effort for many systems is possible to be implemented in high-level languages and knowledge of the instruction set is not required
- But.....
 - Embedded systems require initialisation code and interrupt routines
 - the instruction set is the key to analyzing the performance of programs; Performance gains can be made by writing assembly routines
 - All systems require debugging – possibly at the instruction level
 - Some features of the processor architecture are not available with compilers
 - Etc.

Instruction Set


Instruction 1	opcode	operand1	operand2
Instruction 2	opcode	operand1	operand2
Instruction 3	opcode	operand1	operand2
Instruction 4	opcode	operand1	operand2
...			

- Instruction Set
 - Defines the legal format of instructions for that processor
 - An *opcode* specifies the operation to take place during the instruction:
 - **Data transfer:** memory/register, register/register, I/O, etc.
 - **Arithmetic/logical:** move register through ALU and back
 - **Branches:** determine next PC value when not just PC+1
 - An *operand* field specifies the location of the actual data that takes part in an operation.

A Simple (Trivial) Instruction Set

Assembly instruct.	First byte		Second byte	Operation
MOV Rn, direct	0000	Rn	direct	$Rn = M(\text{direct})$
MOV direct, Rn	0001	Rn	direct	$M(\text{direct}) = Rn$
MOV @Rn, Rm	0010	Rn	Rm	$M(Rn) = Rm$
MOV Rn, @Rm	0111	Rn	Rm	$Rn = M(Rm)$
MOV Rn, #immed.	0011	Rn	immediate	$Rn = \text{immediate}$
ADD Rn, Rm	0100	Rn	Rm	$Rn = Rn + Rm$
SUB Rn, Rm	0101	Rn	Rm	$Rn = Rn - Rm$
JZ Rn, Address	0110	Rn	Address	$PC = \text{Address}$ (only if $Rn = 0$)
Jmp Address	1010	Rn	Address	$PC = \text{Address}$ (always)
	opcode		operands	

Addressing Modes

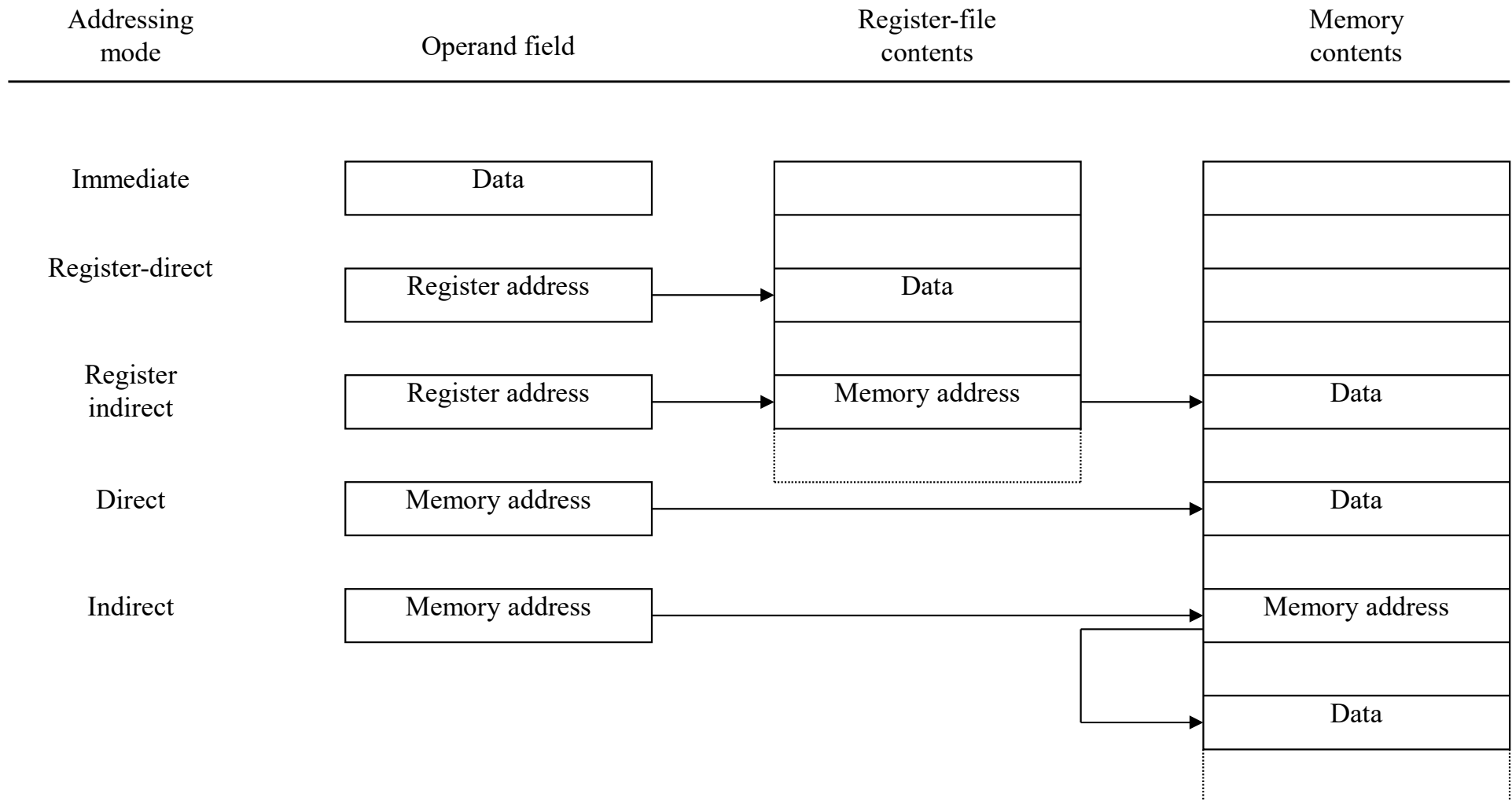

Sample Programs

C program

```
int total = 0;
for (int i=10; i!=0; i--)
    total += i;
// next instructions...
```

Equivalent assembly program

```
0    MOV R0, #0;      // total = 0
1    MOV R1, #10;     // i = 10
2    MOV R2, #1;      // constant 1
3
Loop: JZ R1, Next;     // Done if i=0
4    ADD R0, R1;       // total += i
5    SUB R1, R2;       // i--
6    JMP Loop;         // Jump always
Next: // next instructions...
```

- Exercise: Try some others
 - Handshake: Wait until the value of M[254] is 0, set M[255] to 1, wait until M[254] is 1, set M[255] to 0 (assume those locations are ports: M[254] -> Switch; M[255] -> LED).
 - (Harder) Count the occurrences of zero in an array stored in memory locations 100 through 199.

Programmer's Model (2)

- Program and data memory space
 - Embedded processors often have very limited memory for program and for data
 - e.g., 64 Kbytes program, 256 bytes of RAM (expandable)
- Registers: How many are there?
 - Which registers is visible to the programmer.
- I/O
 - How communicate with external signals?
- Interrupts allow a device to change the flow of control in the CPU and jump to *Interrupt Service Routine* (ISR)
 - Which is the types of interrupts supported by the processor

Outline

- Processor Architecture
- Programmer's Model
- **RT-level custom microarchitecture design of general-purpose processor**

RTL Design Method

- First create instruction set
- Convert instruction set to “complex” state machine
 - Known as **FSMD: finite-state machine with datapath** (or CDFG)
- Partition FSMD into a datapath part and controller part
 - The datapath contains a netlist of functional units like multiplexors, registers, subtractors and a comparator, ...
 - This design is structural
 - The controller is an FSM which issues control signals to the datapath based on the current state and the external inputs.
 - This can be a behavioral description.

Designing a General Purpose Processor

Assembly instruct.	First byte				Second byte		Operation
	15	12	11	8	7	0	
MOV Rn, direct	0000		Rn		direct		Rn = M(direct)
MOV direct, Rn	0001		Rn		direct		M(direct) = Rn
MOV @Rn, Rm	0010		Rn		Rm		M(Rm) = Rn
MOV Rn, #immed.	0011		Rn		immediate		Rn = immediate
ADD Rn, Rm	0100		Rn		Rm		Rn = Rn + Rm
SUB Rn, Rm	0101		Rn		Rm		Rn = Rn - Rm
JZ Rn, relative	0110		Rn		relative		PC = relative (only if Rn is 0)
	⏟		⏟				
	opcode		operands				

A Simple Instruction Set


Designing a General Purpose Processor

- Creating the FSMD

Declarations:

```
bit PC[16], IR[16];  
bit M[64k][16], RF[16][16];
```

FSMD

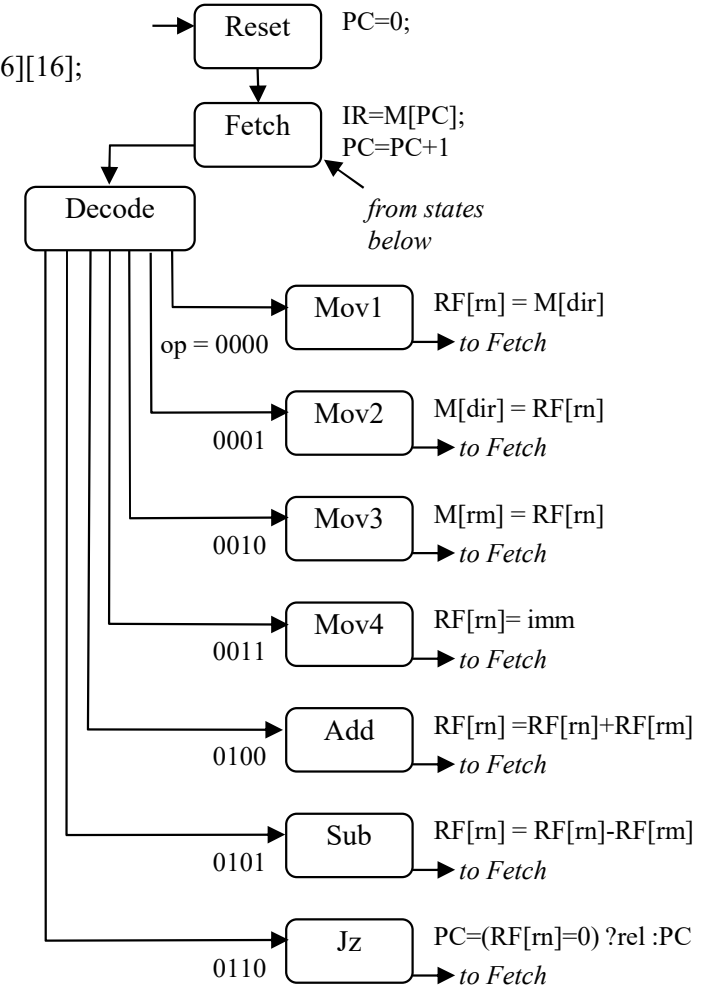

Aliases:



op IR[15..12]	dir IR[7..0]
rn IR[11..8]	imm IR[7..0]
rm IR[7..4]	rel IR[7..0]

Architecture of a Simple Microprocessor

(c) state diagram FSM

Creating the Datapath


(d) Datapath

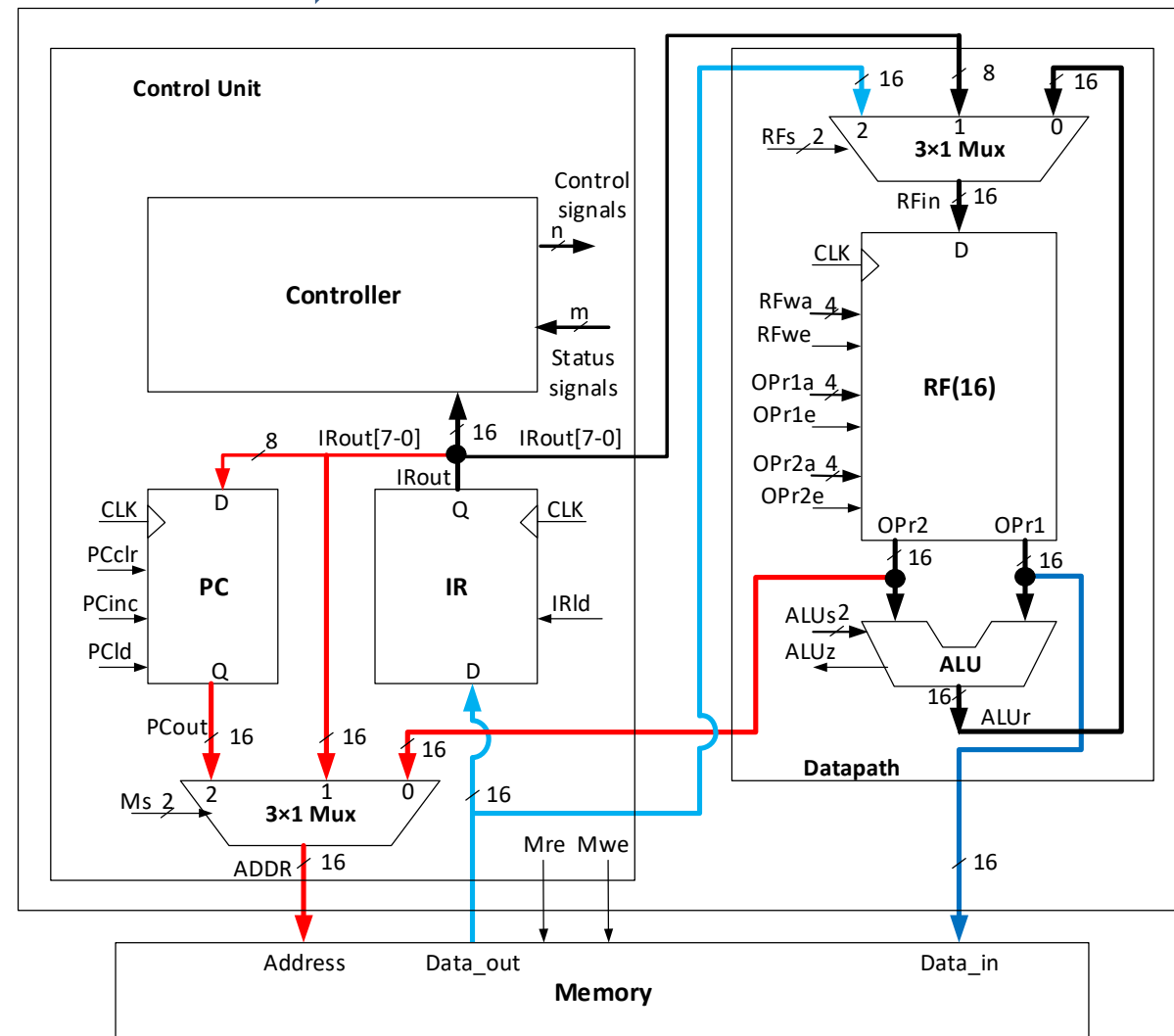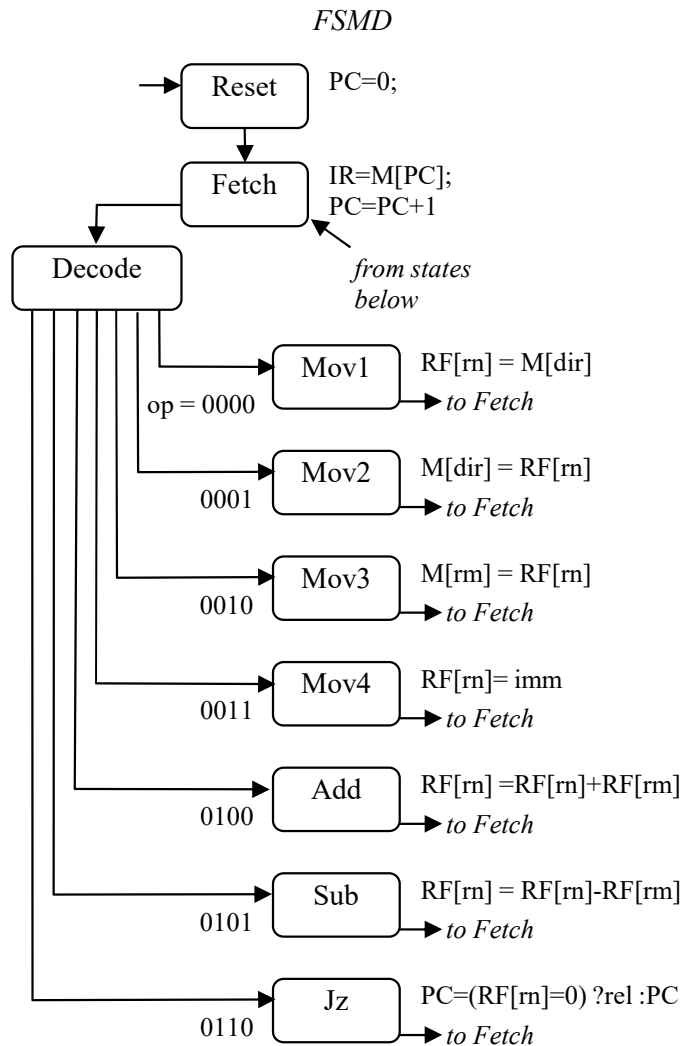

Architecture of a Simple Microprocessor

Creating the Datapath

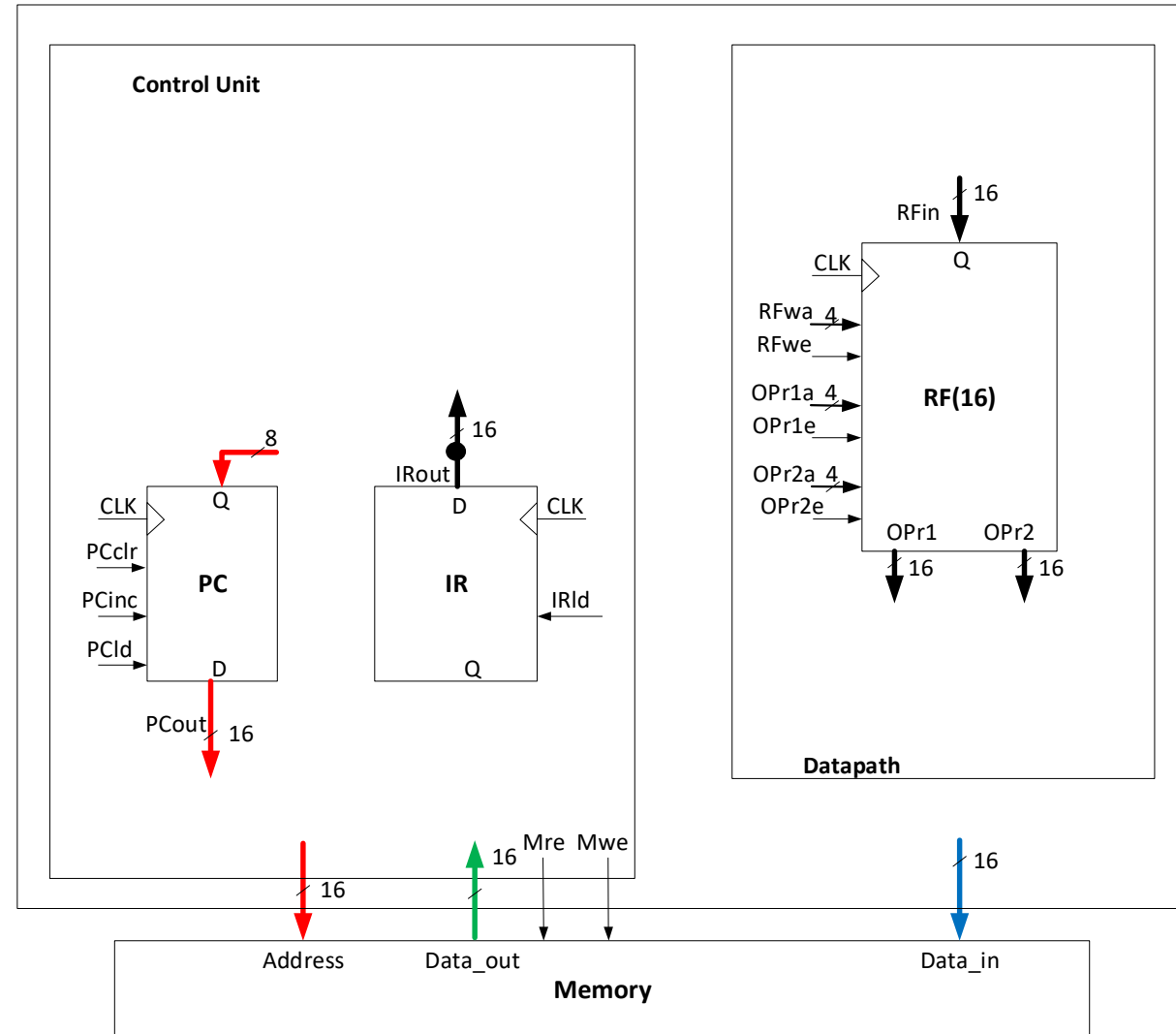
- Storage devices for each declared variable
 - register file holds each of the variables



Architecture of a Simple Microprocessor

Creating the Datapath

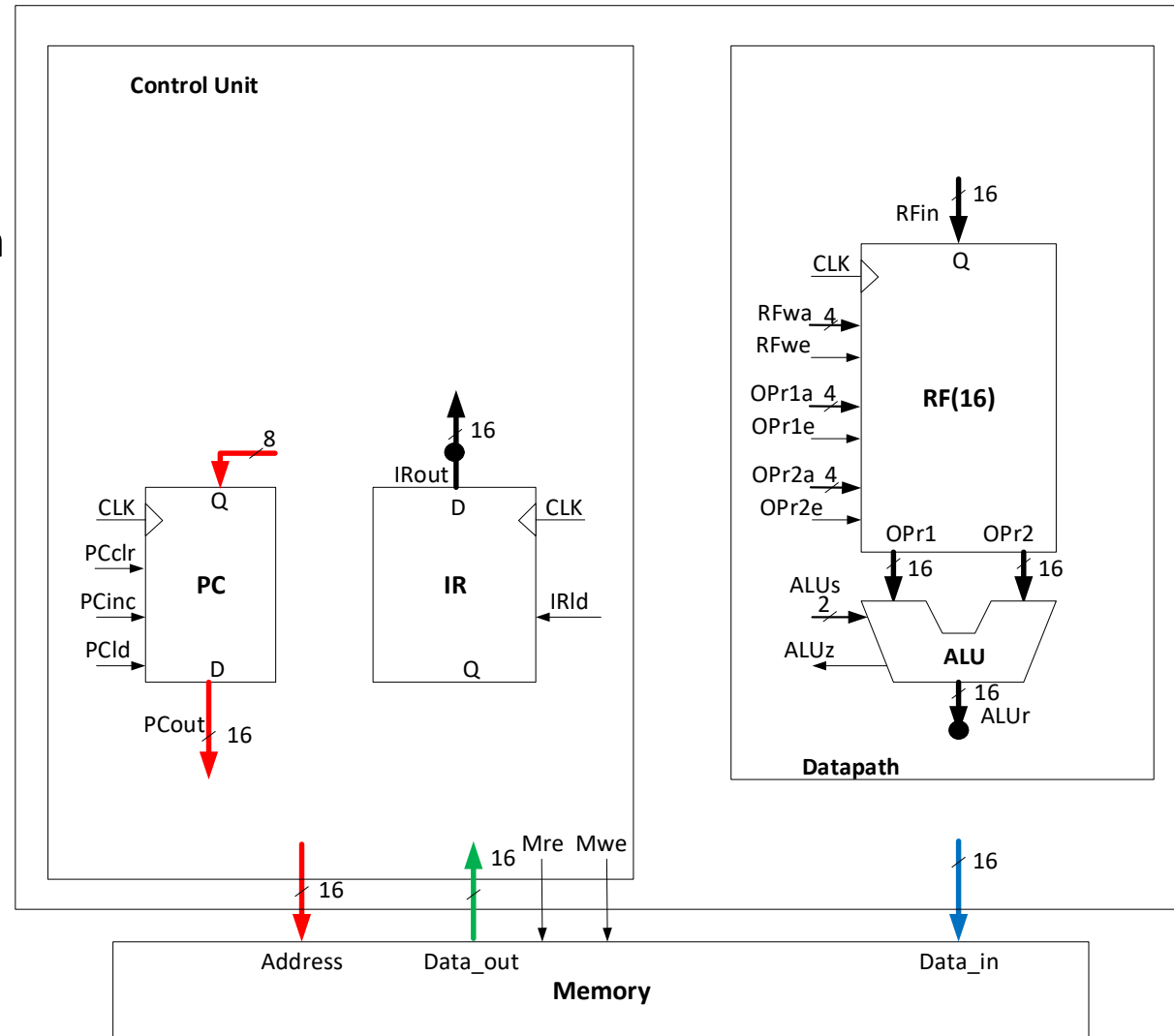
- Storage devices for each declared variable
 - PC, IR, register file holds each of the variables
- Functional units to carry out the FSMD operations
 - One ALU carries out every required operations



Architecture of a Simple Microprocessor


Creating the Datapath

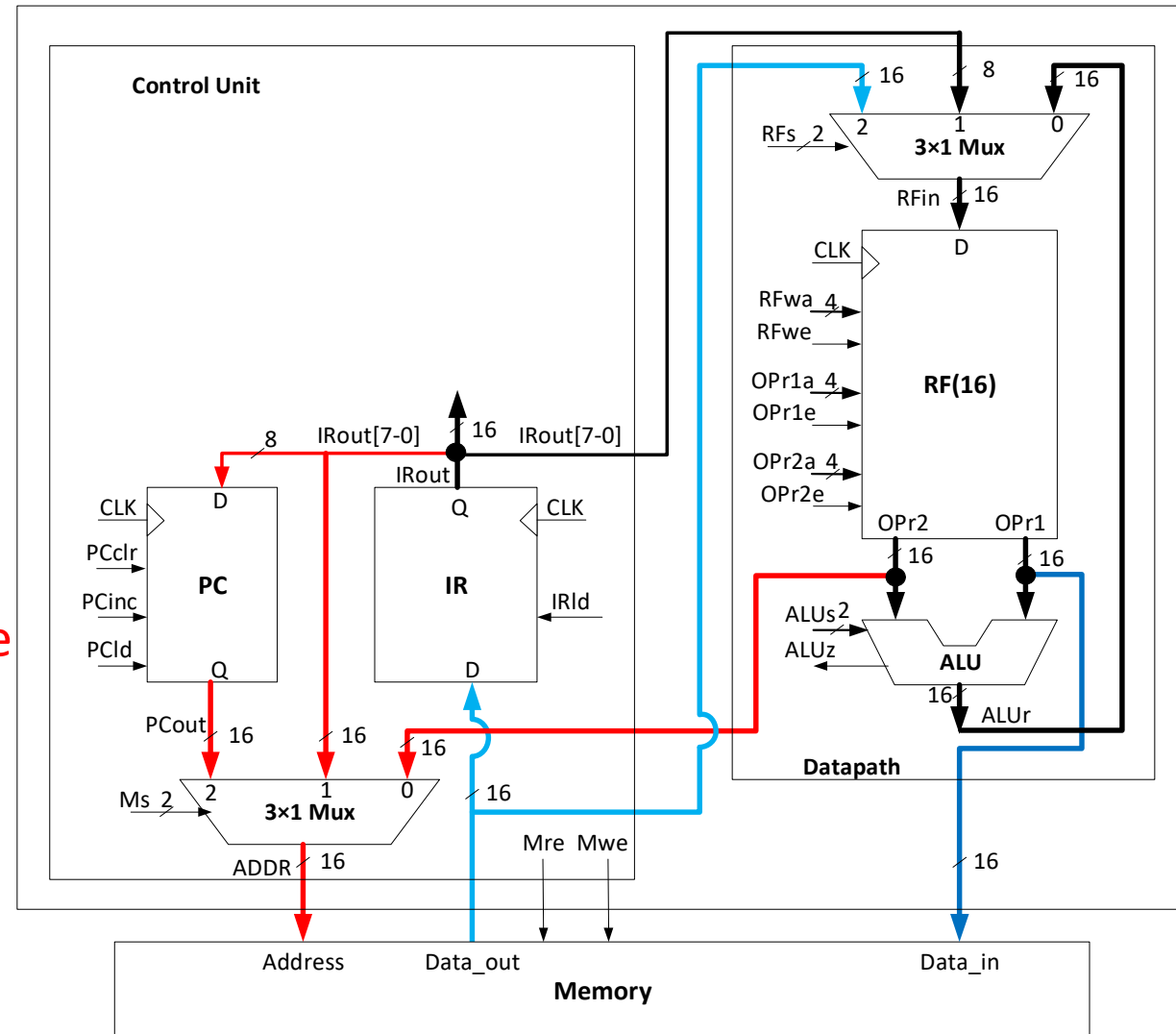- Storage devices for each declared variable
 - register file holds each of the variables
- Functional units to carry out the FSM operations
 - One ALU carries out every required operations
- Connections added among the components' ports corresponding to the operations required by the FSM





Architecture of a Simple Microprocessor

ALUs	ALUr
00	OPr1 + OPr2
01	OPr1 - OPr2
10	OPr1 OR OPr2
10	OPr1 AND OPr2

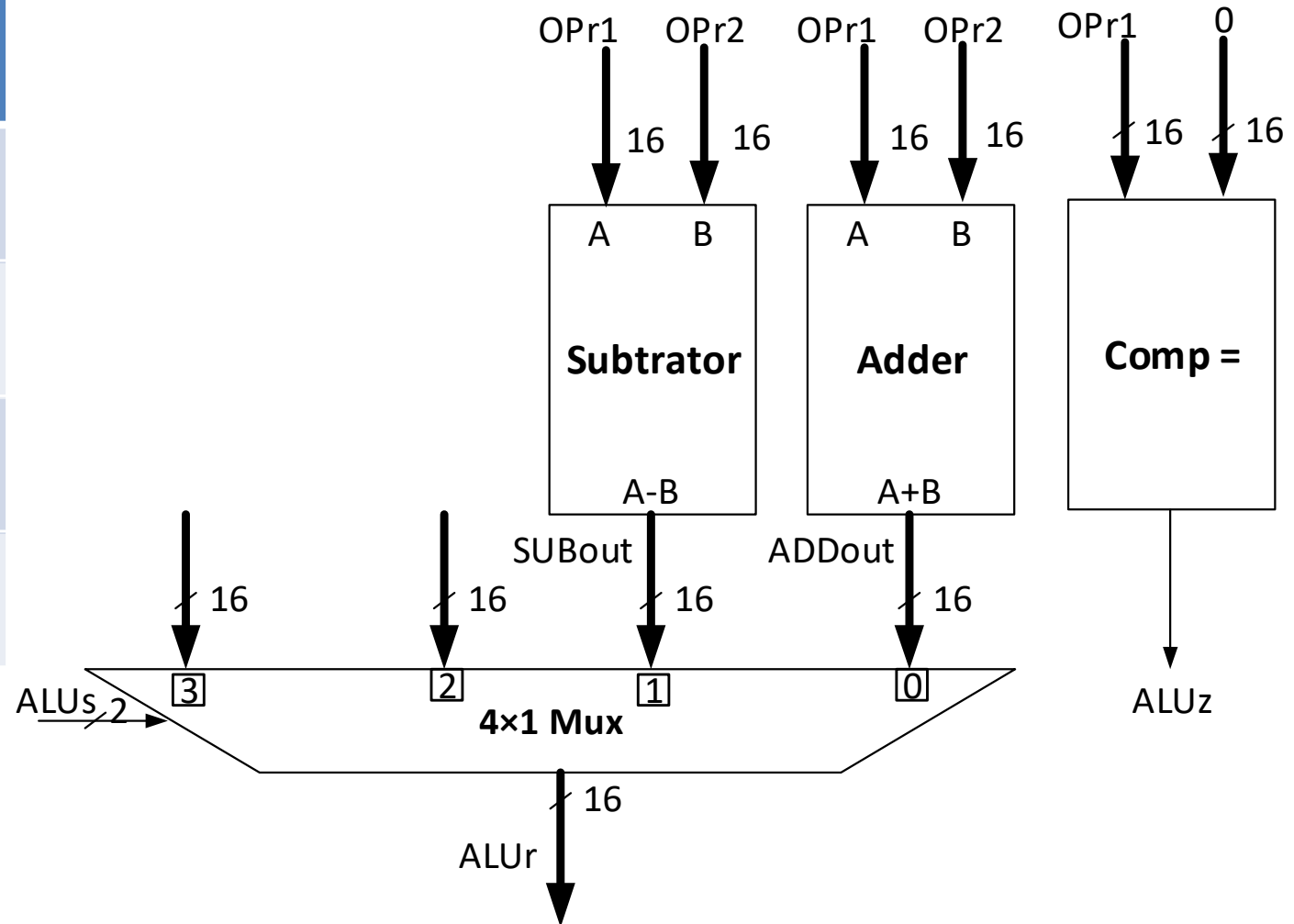


Architecture of a Simple Microprocessor

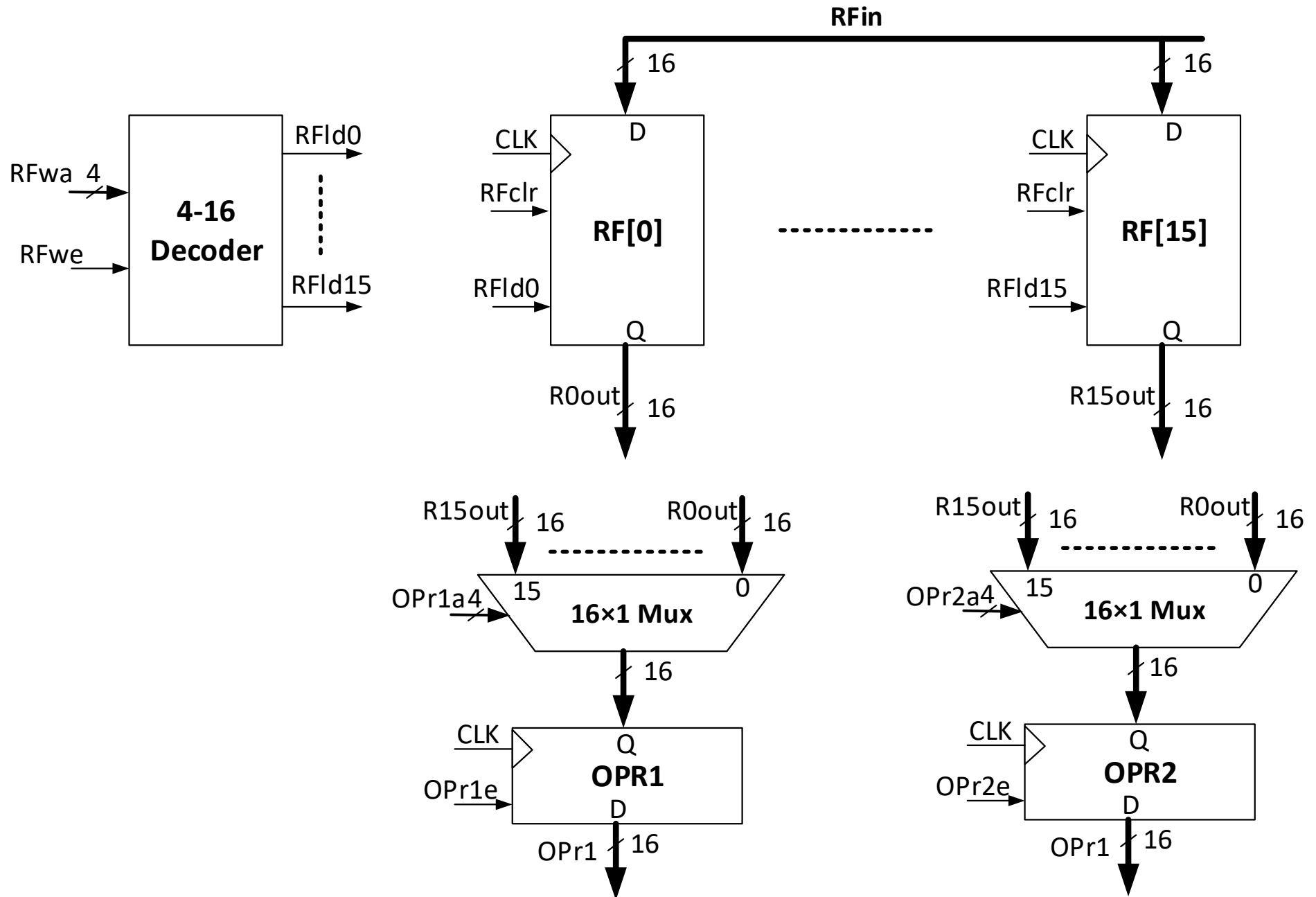

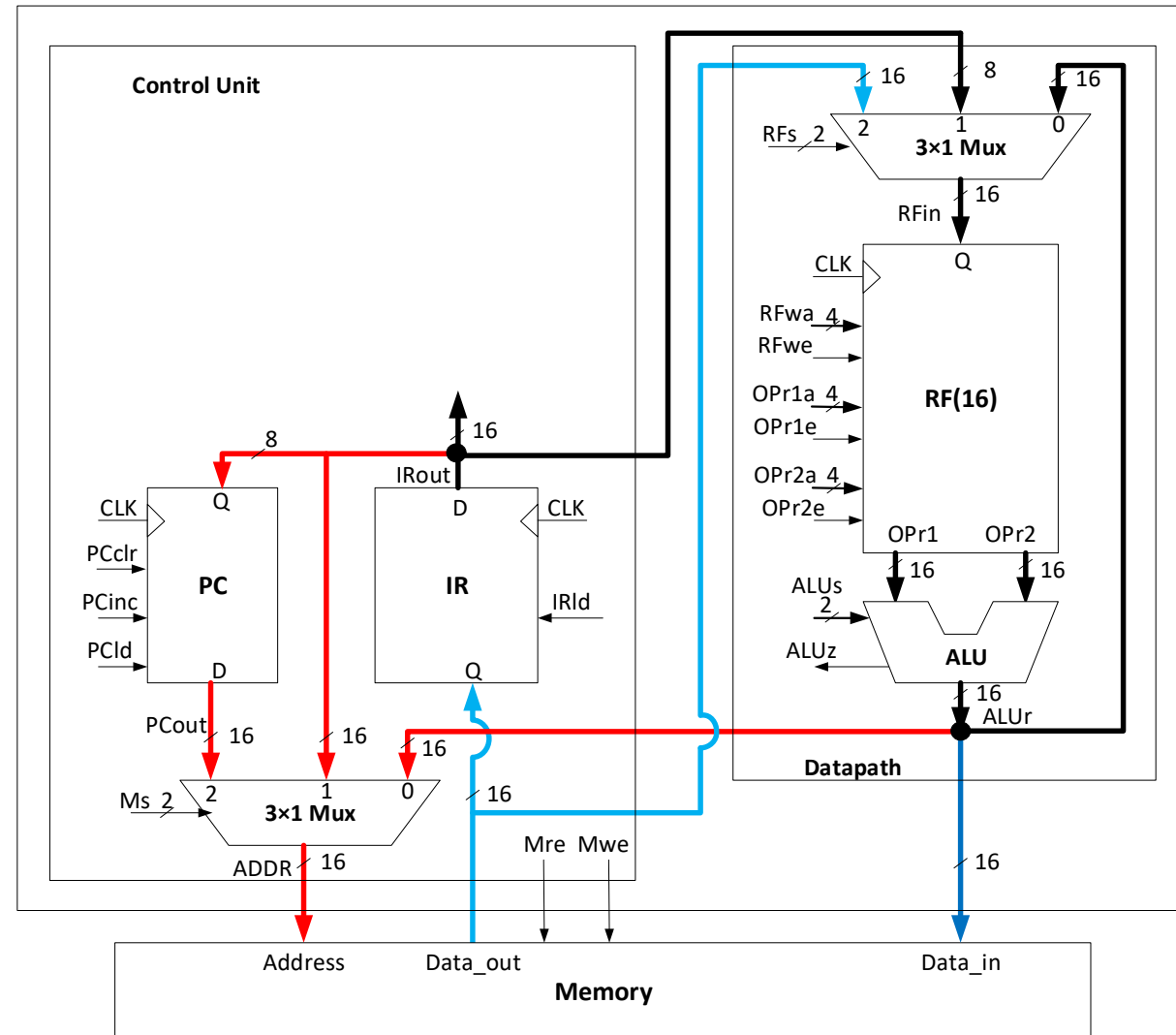


A Simple Microprocessor (here)

(e) Designing Controller

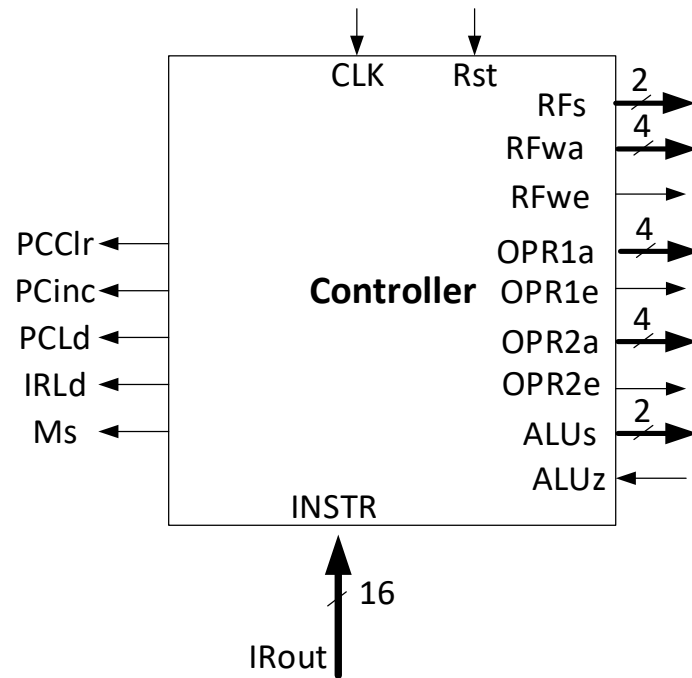


(d) Datapath

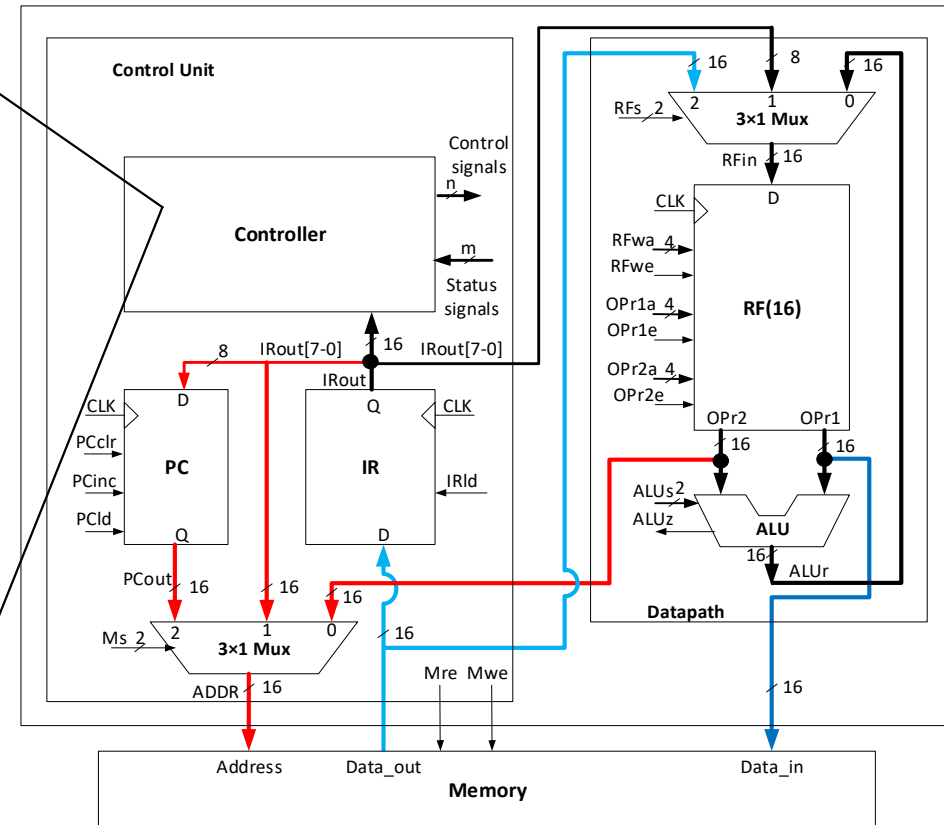


A Simple Microprocessor

(c) state diagram FSMD

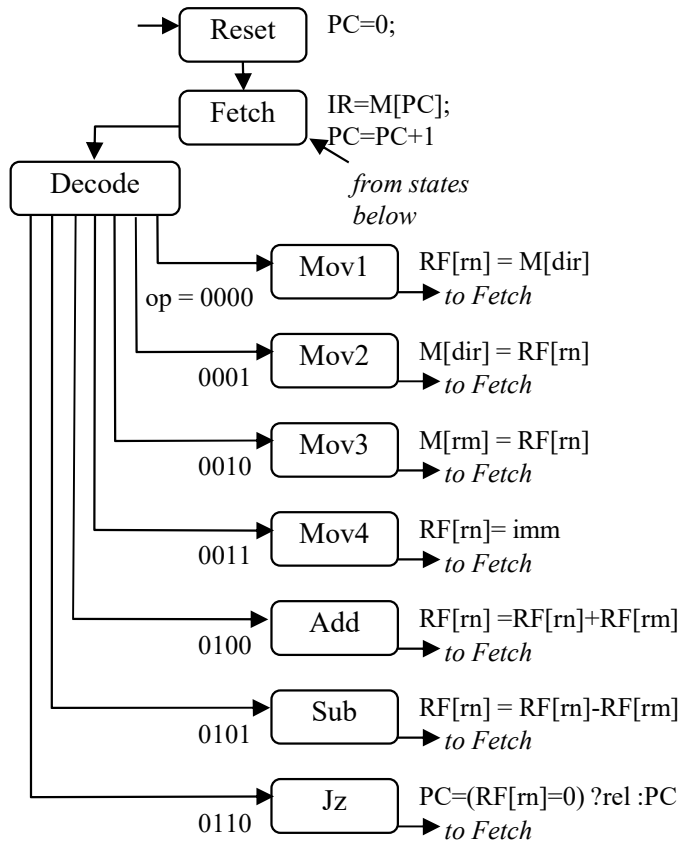


FSMD

(f) state diagram FSM


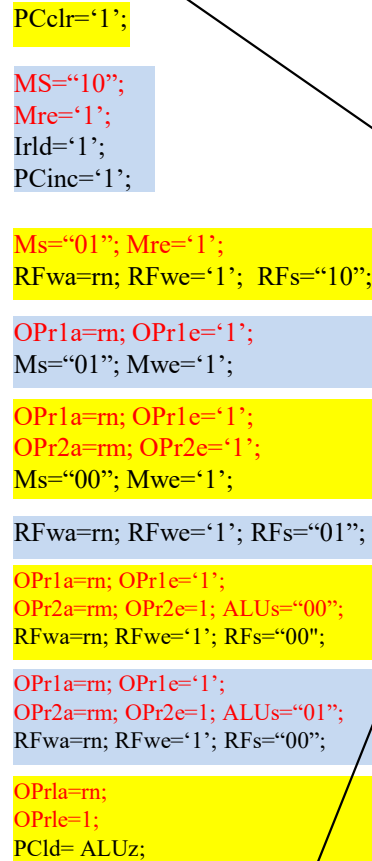


FSM operations that replace the FSMD operations after a datapath is created


(d) Datapath

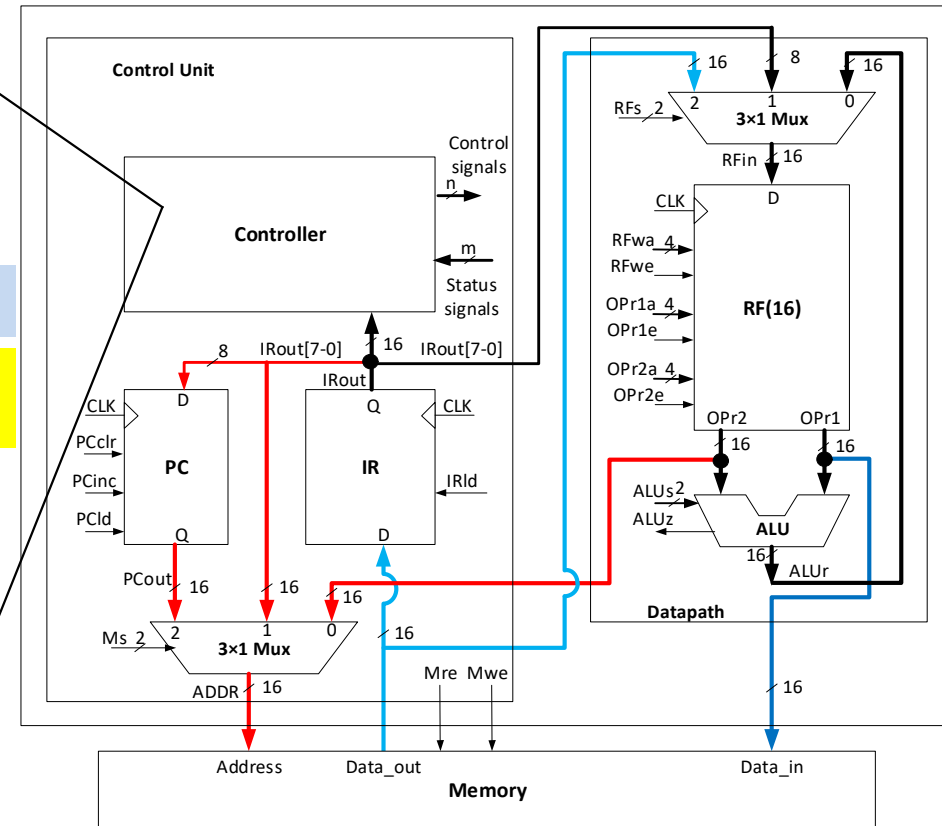

A Simple Microprocessor

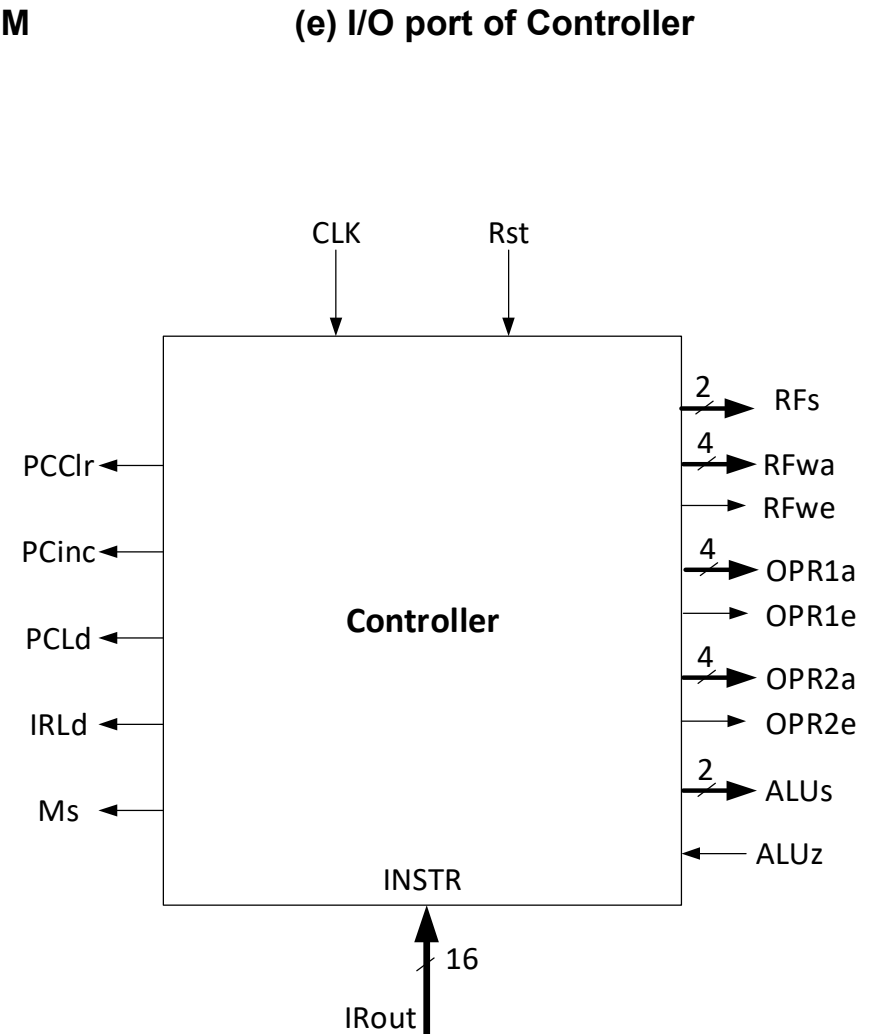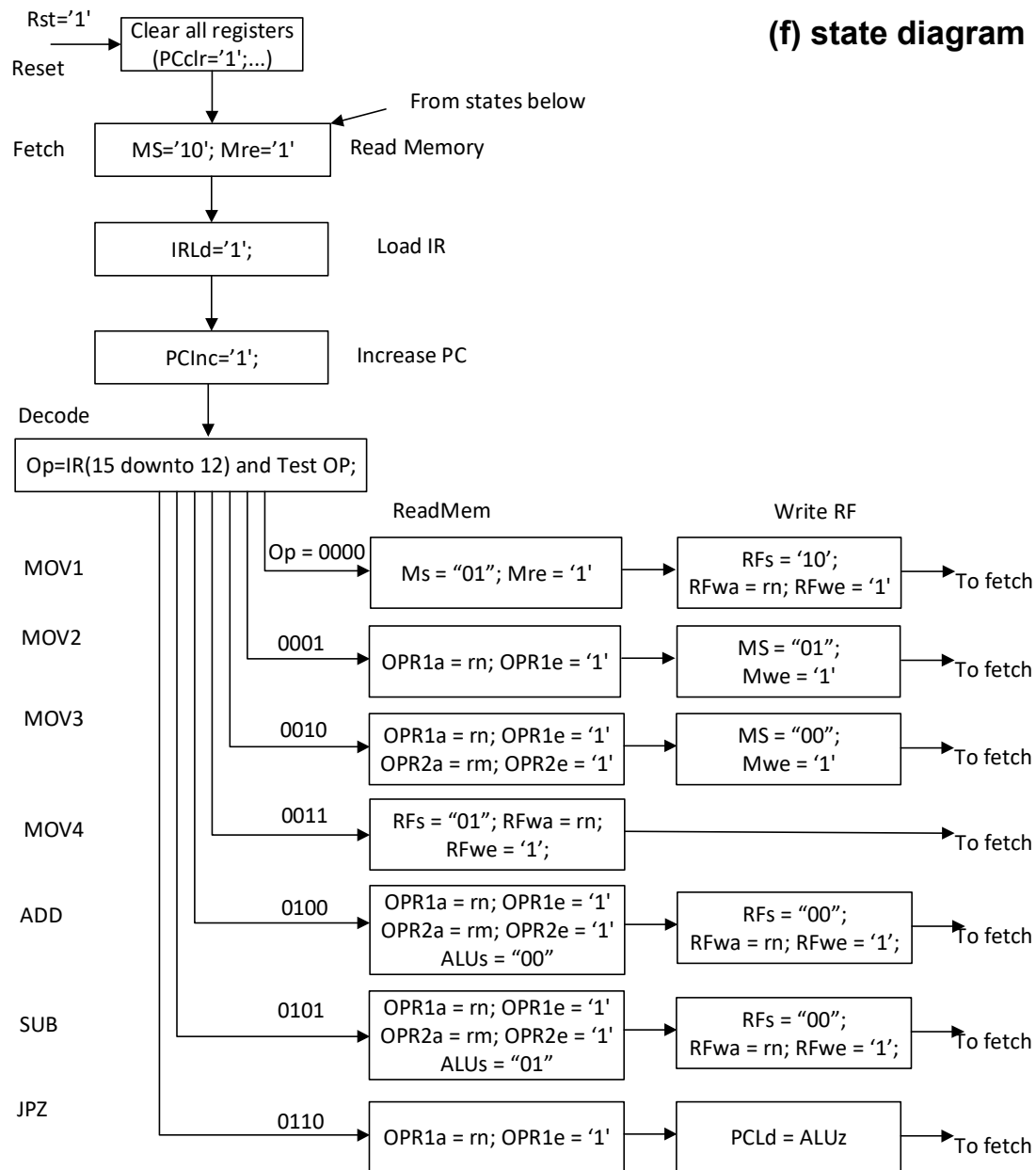


A Simple Microprocessor

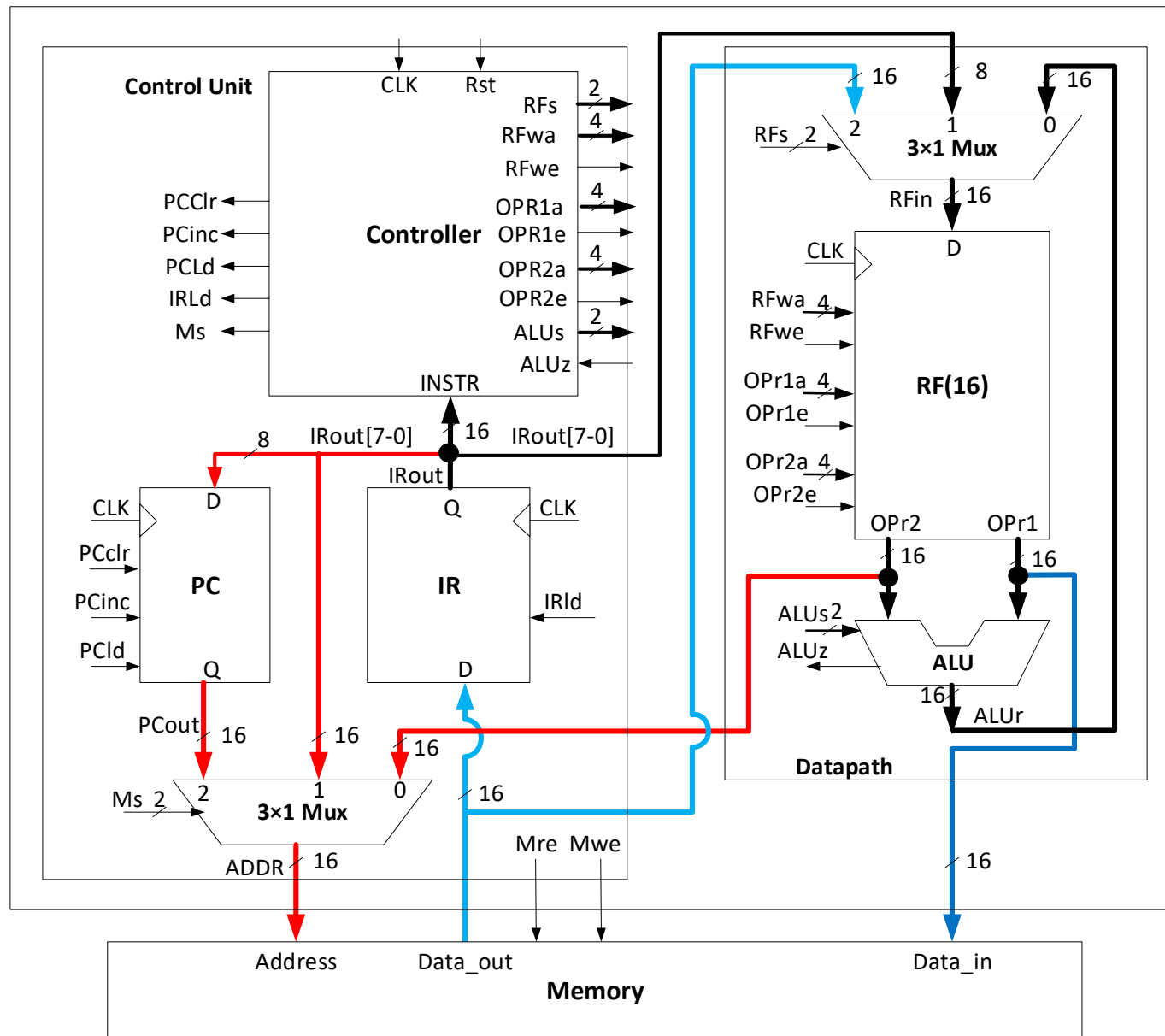

You just built a simple microprocessor!

Quiz

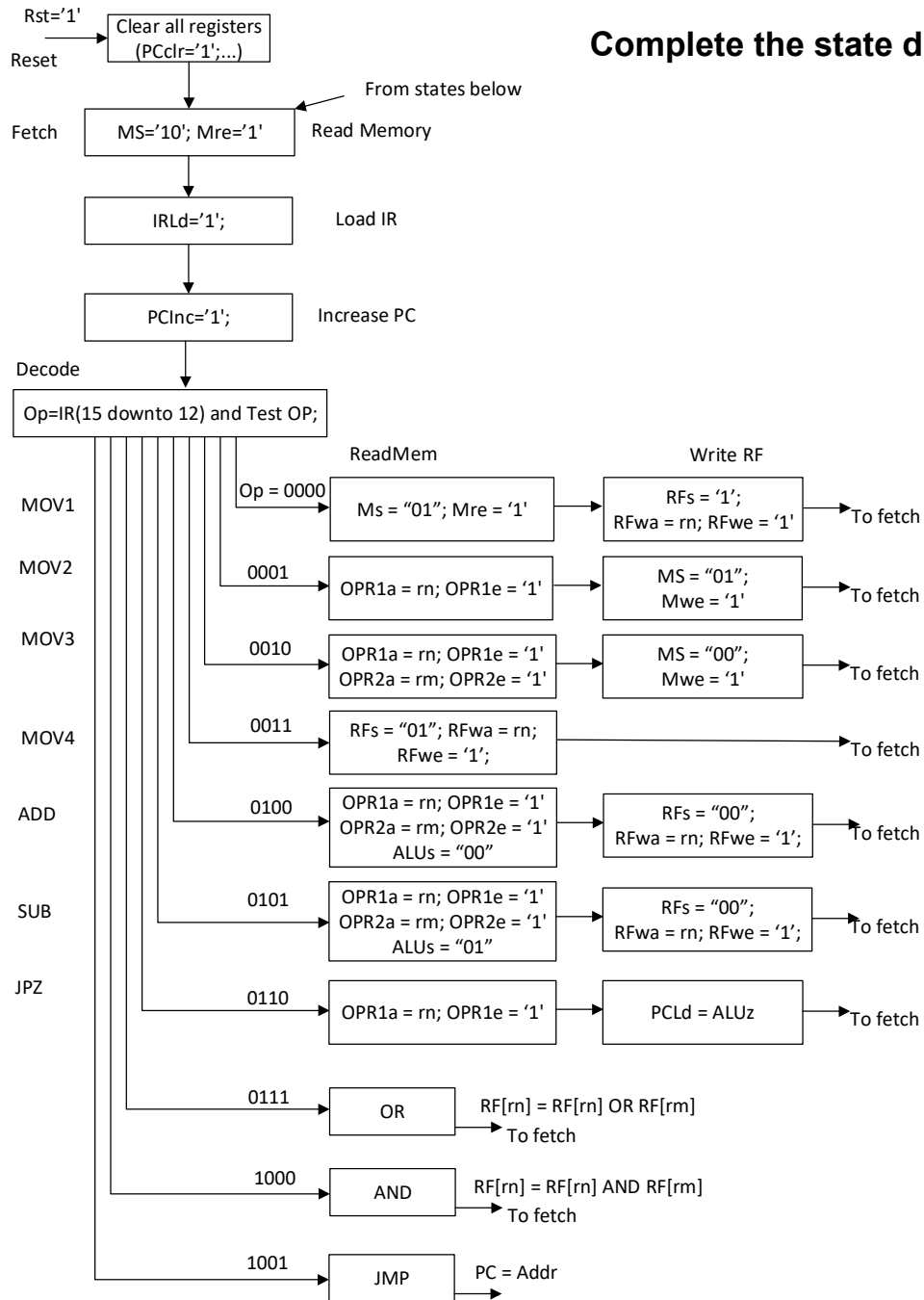Complete the state diagram FSM for instructions: OR, AND, JMP



RTL Modeling of Processor design in VHDL

- **Controller:** is behavior description of the FSM
- **Datapath:** structural description, including:
 - **Mux3to1:** choose one of three 16-bit inputs to connect to output port under the control of one select line.
 - **Register File:** 16 Registers, each takes a 16-bit input, a load signal, reset, and a clock signal.
 - **ALU:** adds or subtracts two 16-bit numbers,.
 - **PC Register:** 16 bits, holds the address of the next instruction.
 - **IR Register: 16 bits,** holds the next instruction
 - **Decoder4to16:** take a 4-bit input and generate a 16-bit output signal

Testbench for testing the Processor

- **Instruction/Data Memory Model:** behavior description
- **Data and Program for test:** stored in .mif file
- **Reset/Clock circuits:**

Summary

- General-purpose processors
 - Good performance, low NRE, flexible
- Structure includes Controller, datapath, and memory
- Many tools required for developing applications
 - Including compiler and debugger, instruction-set simulators, and in-circuit emulators
- Programmer's Model
 - Assembly Instructions, Registers, Addressing Models, ...
- Techniques for designing a general-purpose processor